

Boolean Algebra and Digital Logic

Hamza Osman İLHAN

hoilhan@yildiz.edu.tr

D-037

Objectives

- Understand the relationship between Boolean logic and digital computer circuits.
- Learn how to design simple logic circuits.
- Understand how digital circuits work together to form complex computer systems.

Introduction

- In the latter part of the nineteenth century, George Boole incensed philosophers and mathematicians alike when he suggested that logical thought could be represented through mathematical equations.
 - *How dare anyone suggest that human thought could be encapsulated and manipulated like an algebraic formula?*
- Computers, as we know them today, are implementations of Boole's *Laws of Thought*.
 - John Atanasoff and Claude Shannon were among the first to see this connection.

-
- In the middle of the twentieth century, computers were commonly known as “thinking machines” and “electronic brains.”
 - Many people were fearful of them.
 - Nowadays, we rarely ponder the relationship between electronic digital computers and human logic. Computers are accepted as part of our lives.
 - Many people, however, are still fearful of them.
 - In this chapter, you will learn the simplicity that constitutes the essence of the machine.

Boolean Algebra

- Boolean algebra is a mathematical system for the manipulation of variables that can have one of two values.
 - In formal logic, these values are “true” and “false.”
 - In digital systems, these values are “on” and “off,” 1 and 0, or “high” and “low.”
- Boolean expressions are created by performing operations on Boolean variables.
 - Common Boolean operators include AND, OR, and NOT.

-
- A Boolean operator can be completely described using a truth table.
 - The truth table for the Boolean operators AND and OR are shown at the right.
 - The AND operator is also known as a Boolean product. The OR operator is the Boolean sum.

X AND Y

X	Y	XY
0	0	0
0	1	0
1	0	0
1	1	1

X OR Y

X	Y	X+Y
0	0	0
0	1	1
1	0	1
1	1	1

-
- The truth table for the Boolean NOT operator is shown at the right.
 - The NOT operation is most often designated by an overbar. It is sometimes indicated by a prime mark (') or an “elbow” (\neg).

X	\bar{X}
0	1
1	0

-
- A Boolean function has:
 - At least one Boolean variable,
 - At least one Boolean operator, and
 - At least one input from the set $\{0,1\}$.
 - It produces an output that is also a member of the set $\{0,1\}$.

- The truth table for the Boolean function:

$$F(x, y, z) = x\bar{z} + y$$

is shown at the right.

- To make evaluation of the Boolean function easier, the truth table contains extra (shaded) columns to hold evaluations of subparts of the function.

$$F(x, y, z) = x\bar{z} + y$$

x	y	z	\bar{z}	$x\bar{z}$	$x\bar{z} + y$
0	0	0	1	0	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	0	0	1

- As with common arithmetic, Boolean operations have rules of precedence.
- The NOT operator has highest priority, followed by AND and then OR.
- This is how we chose the (shaded) function subparts in our table.

$$F(x, y, z) = x\bar{z} + y$$

x	y	z	\bar{z}	$x\bar{z}$	$x\bar{z} + y$
0	0	0	1	0	0
0	0	1	0	0	0
0	1	0	1	0	1
0	1	1	0	0	1
1	0	0	1	1	1
1	0	1	0	0	0
1	1	0	1	1	1
1	1	1	0	0	1

-
- Digital computers contain circuits that implement Boolean functions.
 - The simpler that we can make a Boolean function, the smaller the circuit that will result.
 - Simpler circuits are cheaper to build, consume less power, and run faster than complex circuits.
 - With this in mind, we always want to reduce our Boolean functions to their simplest form.
 - There are a number of Boolean identities that help us to do this.

-
- Most Boolean identities have an AND (product) form as well as an OR (sum) form. We give our identities using both forms. Our first group is rather intuitive:

Identity Name	AND Form	OR Form
Identity Law	$1x = x$	$0 + x = x$
Null Law	$0x = 0$	$1 + x = 1$
Idempotent Law	$xx = x$	$x + x = x$
Inverse Law	$x\bar{x} = 0$	$x + \bar{x} = 1$

-
- Our second group of Boolean identities should be familiar to you from your study of algebra:

Identity Name	AND Form	OR Form
Commutative Law	$xy = yx$	$x+y = y+x$
Associative Law	$(xy)z = x(yz)$	$(x+y)+z = x+(y+z)$
Distributive Law	$x+yz = (x+y)(x+z)$	$x(y+z) = xy+xz$

- Our last group of Boolean identities are perhaps the most useful.
- If you have studied set theory or formal logic, these laws are also familiar to you.

Identity Name	AND Form	OR Form
Absorption Law	$x(x+y) = x$	$x + xy = x$
DeMorgan's Law	$\overline{(xy)} = \bar{x} + \bar{y}$	$\overline{(x+y)} = \bar{x}\bar{y}$
Double Complement Law	$\overline{(\bar{x})} = x$	

- We can use Boolean identities to simplify the function:

as follows:

$$F(X, Y, Z) = (X + Y) (X + \bar{Y}) \overline{(XZ)}$$

$$\begin{aligned} & (X + Y) (X + \bar{Y}) \overline{(XZ)} \\ & (X + Y) (X + \bar{Y}) (\bar{X} + Z) \\ & (XX + X\bar{Y} + XY + Y\bar{Y}) (\bar{X} + Z) \\ & ((X + Y\bar{Y}) + X(Y + \bar{Y})) (\bar{X} + Z) \\ & ((X + 0) + X(1)) (\bar{X} + Z) \\ & X(\bar{X} + Z) \\ & X\bar{X} + XZ \\ & 0 + XZ \\ & XZ \end{aligned}$$

Idempotent Law (Rewriting)
 DeMorgan's Law
 Distributive Law
 Commutative & Distributive Laws
 Inverse Law
 Idempotent Law
 Distributive Law
 Inverse Law
 Idempotent Law

-
- Sometimes it is more economical to build a circuit using the complement of a function (and complementing its result) than it is to implement the function directly.
 - DeMorgan's law provides an easy way of finding the complement of a Boolean function.
 - Recall DeMorgan's law states:

$$\overline{(xy)} = \bar{x} + \bar{y} \quad \text{and} \quad \overline{(x+y)} = \bar{x}\bar{y}$$

- DeMorgan's law can be extended to any number of variables.
- Replace each variable by its complement and change all ANDs to ORs and all ORs to ANDs.
- Thus, we find the the complement of:

is:

$$F(X, Y, Z) = (XY) + (\bar{X}Z) + (Y\bar{Z})$$

$$\bar{F}(X, Y, Z) = \overline{(XY) + (\bar{X}Z) + (Y\bar{Z})}$$

$$= \overline{(XY)} \overline{(\bar{X}Z)} \overline{(Y\bar{Z})}$$

$$= (\bar{X} + \bar{Y})(X + \bar{Z})(\bar{Y} + Z)$$

-
- Through our exercises in simplifying Boolean expressions, we see that there are numerous ways of stating the same Boolean expression.
 - These “synonymous” forms are *logically equivalent*.
 - Logically equivalent expressions have identical truth tables.
 - In order to eliminate as much confusion as possible, designers express Boolean functions in *standardized* or *canonical* form.

-
- There are two canonical forms for Boolean expressions: sum-of-products and product-of-sums.
 - Recall the Boolean product is the AND operation and the Boolean sum is the OR operation.
 - In the sum-of-products form, ANDed variables are ORed together.
 - For example:
 - In the product-of-sums form, ORed variables are ANDed together.
 - For example:

$$F(x, y, z) = xy + xz + yz$$

$$F(x, y, z) = (x+y)(x+z)(y+z)$$

-
- It is easy to convert a function to sum-of-products form using its truth table.
 - We are interested in the values of the variables that make the function true (=1).
 - Using the truth table, we list the values of the variables that result in a true function value.
 - Each group of variables is then ORed together.

$$F(x, y, z) = x\bar{z} + y$$

x	y	z	$x\bar{z} + y$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- The sum-of-products form for our function is:

$$F(x, y, z) = \bar{x}\bar{y}\bar{z} + \bar{x}y\bar{z} + x\bar{y}\bar{z} + x\bar{y}z + x\bar{y}z + xyz$$

We note that this function is not in simplest terms. Our aim is only to rewrite our function in canonical sum-of-products form.


$$F(x, y, z) = x\bar{z} + y$$

x	y	z	$x\bar{z} + y$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Logic Gates

- We have looked at Boolean functions in abstract terms.
- In this section, we see that Boolean functions are implemented in digital computer circuits called gates.
- A gate is an electronic device that produces a result based on two or more input values.
 - In reality, gates consist of one to six transistors, but digital designers think of them as a single unit.
 - Integrated circuits contain collections of gates suited to a particular purpose.

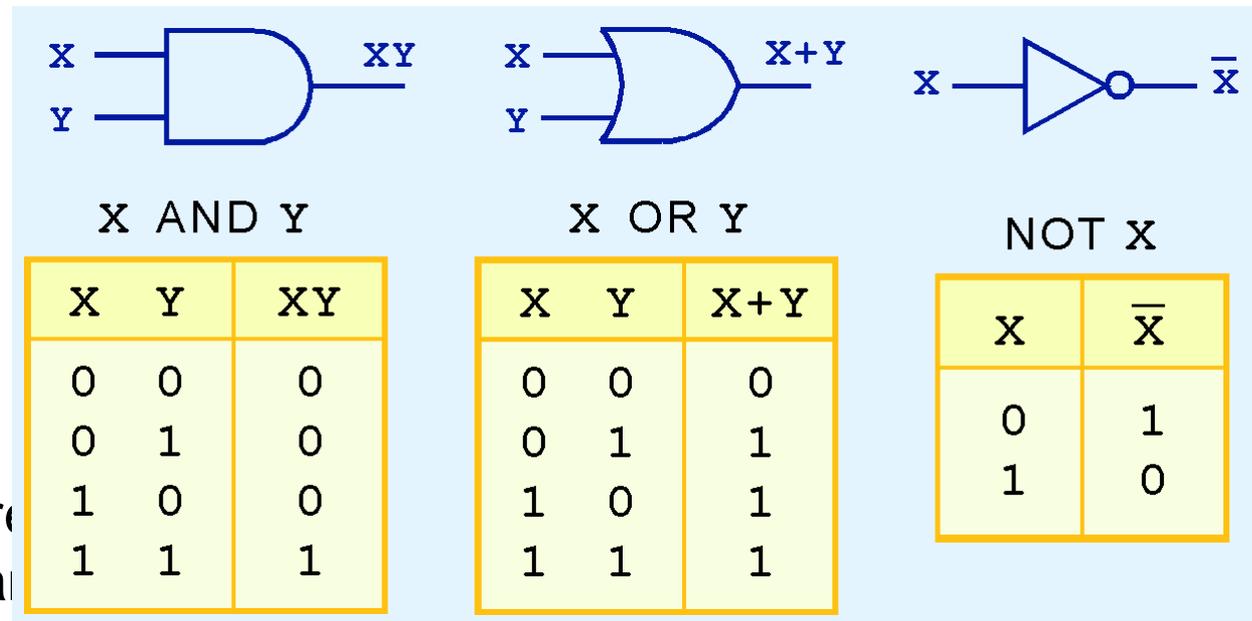
- The three simplest gates are the AND, OR, and NOT gates.



- They correspond to the operations, as you can see.

operations,

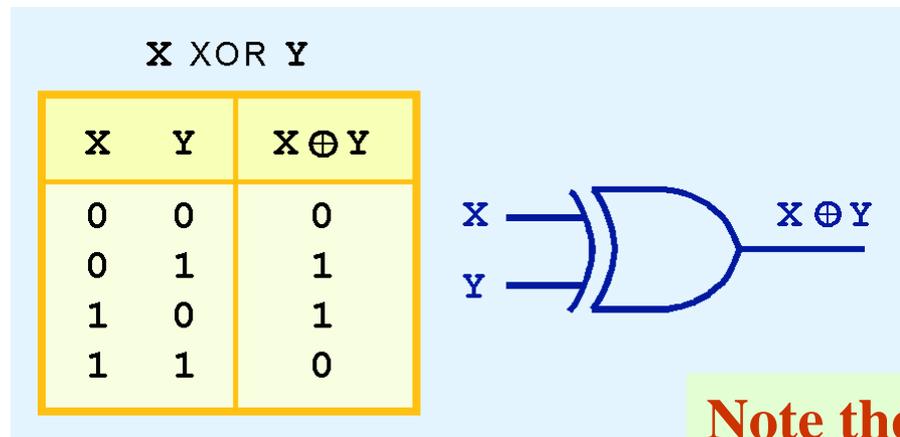-
- Another very useful gate is the exclusive OR (XOR) gate.
 - The output of the XOR operation is true only when the values of the inputs differ.




Note the special symbol \oplus for the XOR operation.

- NAND and NOR are two very important gates. Their symbols and truth tables are shown at the right.



X NAND Y

X	Y	X NAND Y
0	0	1
0	1	1
1	0	1
1	1	0

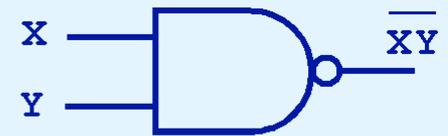


X NOR Y


X	Y	X NOR Y
0	0	1
0	1	0
1	0	0
1	1	0

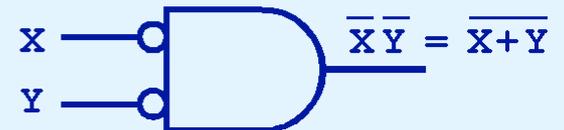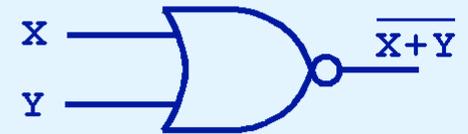

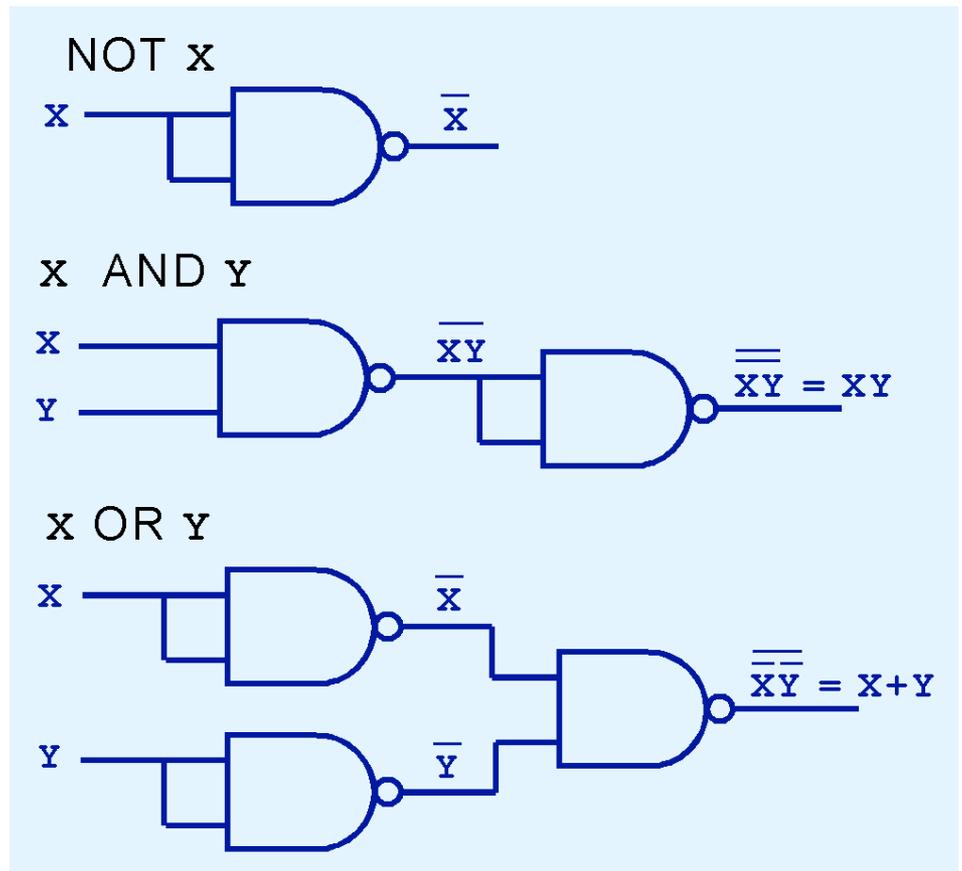- NAND and NOR are known as *universal gates* because they are inexpensive to manufacture and any Boolean function can be constructed using only NAND or only NOR gates.



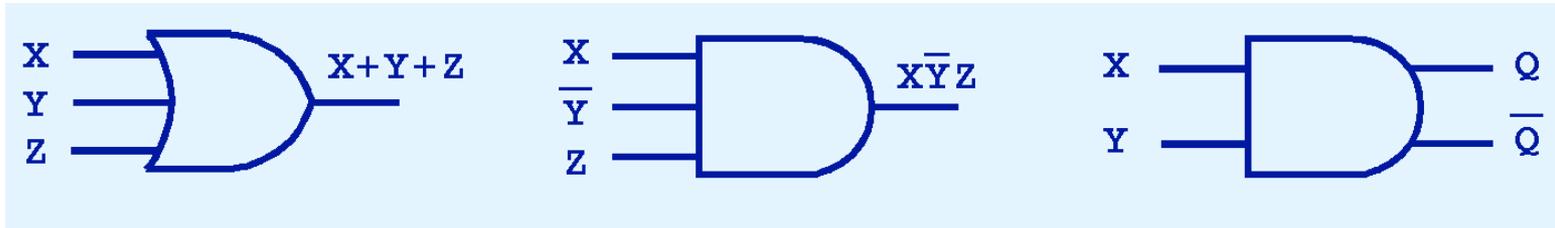
-
- Gates can have multiple inputs and more than one output.
 - A second output can be provided for the complement of the operation.
 - We'll see more of this later.



Digital Components

- The main thing to remember is that combinations of gates implement Boolean functions.
- The circuit below implements the Boolean function:

$$F(X, Y, Z) = X + \bar{Y}Z$$

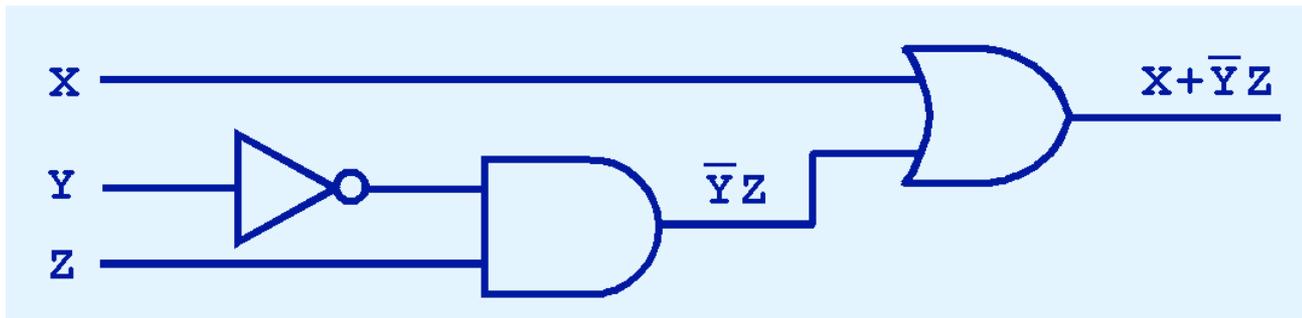

We simplify our Boolean expressions so that we can create simpler circuits.

-
- We have designed a circuit that implements the Boolean function:

$$F(X, Y, Z) = X + \bar{Y}Z$$


- This circuit is an example of a *combinational logic* circuit.
- Combinational logic circuits produce a specified output (almost) at the instant when input values are applied.
 - In a later section, we will explore circuits where this is not the case.

Combinational Circuits

- Combinational logic circuits give us many useful devices.
- One of the simplest is the *half adder*, which finds the sum of two bits.
- We can gain some insight as to the construction of a half adder by looking at its truth table, shown at the right.

Inputs		Outputs	
X	Y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

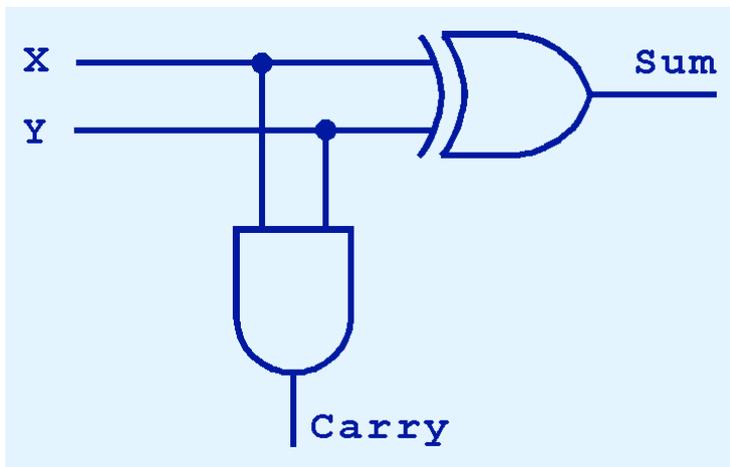- As we see, the sum can be found using the XOR operation and the carry using the AND operation.




Inputs		Outputs	
X	Y	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

-
- We can change our half adder into a full adder by including gates for processing the carry bit.
 - The truth table for a full adder is shown at the right.


Inputs			Outputs	
X	Y	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

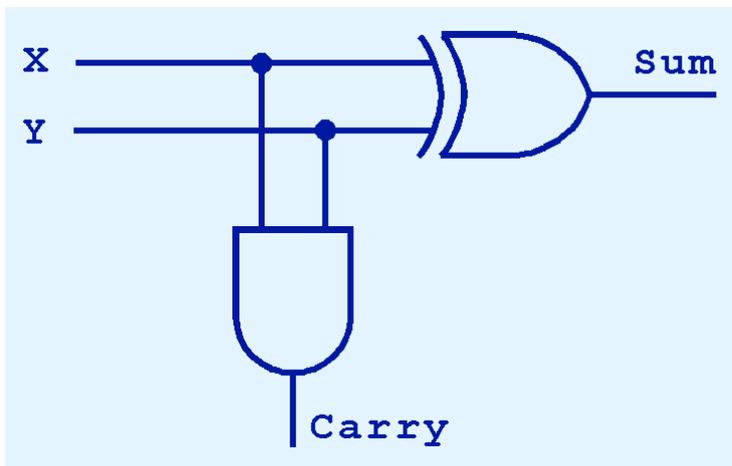- How can we change the half adder shown below to make it a full adder?




Inputs			Outputs	
X	Y	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

- Here's our completed full adder.

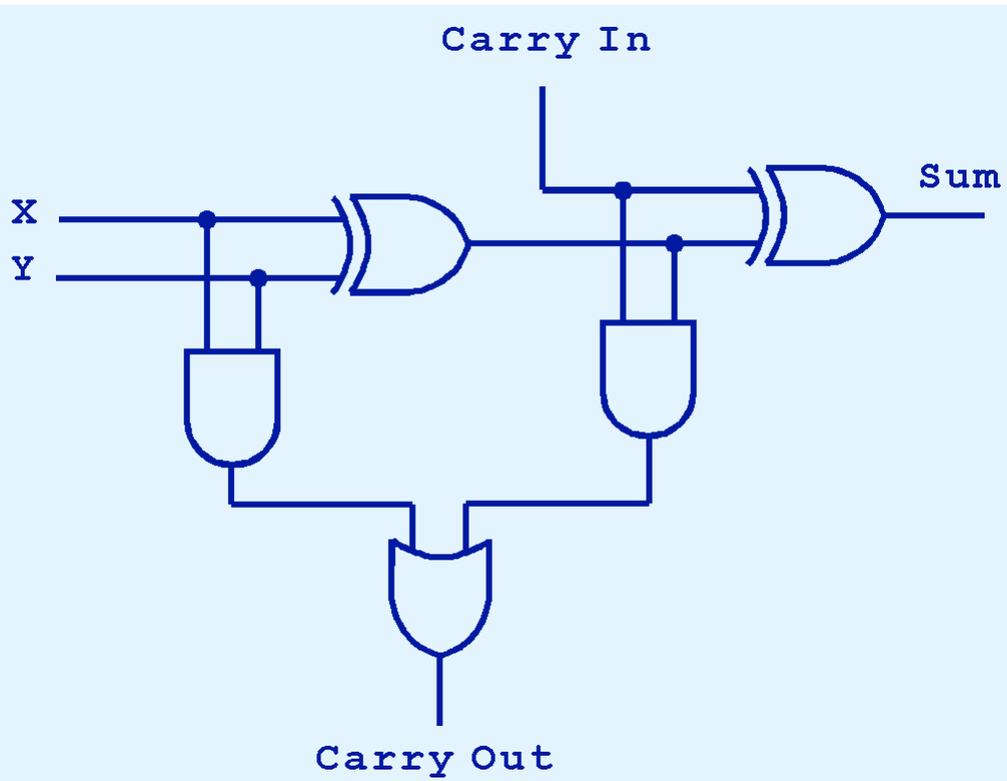

Inputs			Outputs	
X	Y	Carry In	Sum	Carry Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

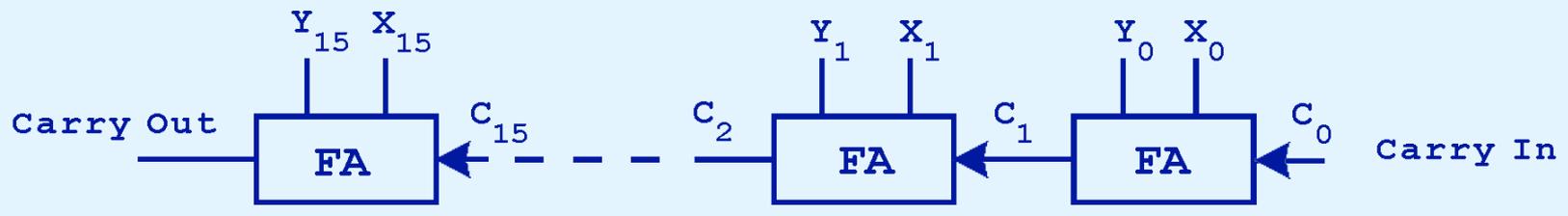-
- Just as we combined half adders to make a full adder, full adders can be connected in series.
 - The carry bit “ripples” from one adder to the next; hence, this configuration is called a *ripple-carry adder*.




Today's systems employ more efficient adders.

-
- Decoders are another important type of combinational circuit.
 - Among other things, they are useful in selecting a memory location according a binary value placed on the address lines of a memory bus.
 - Address decoders with n inputs can select any of 2^n locations.

This is a block diagram for a decoder.




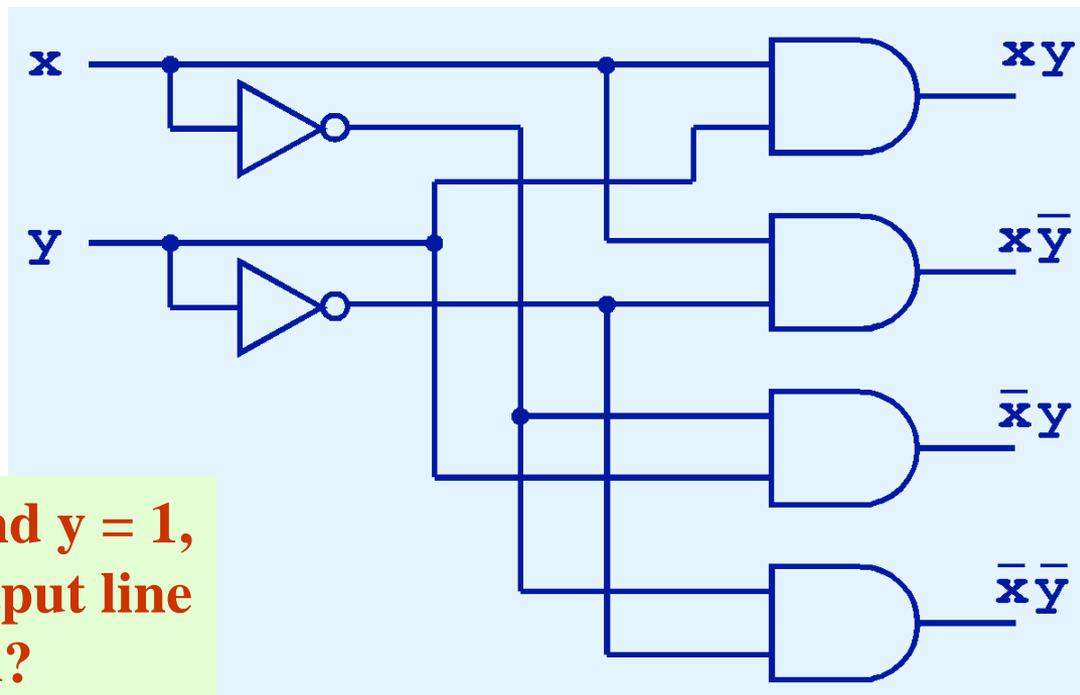- This is what a 2-to-4 decoder looks like on the inside.




**If $x = 0$ and $y = 1$,
which output line
is enabled?**

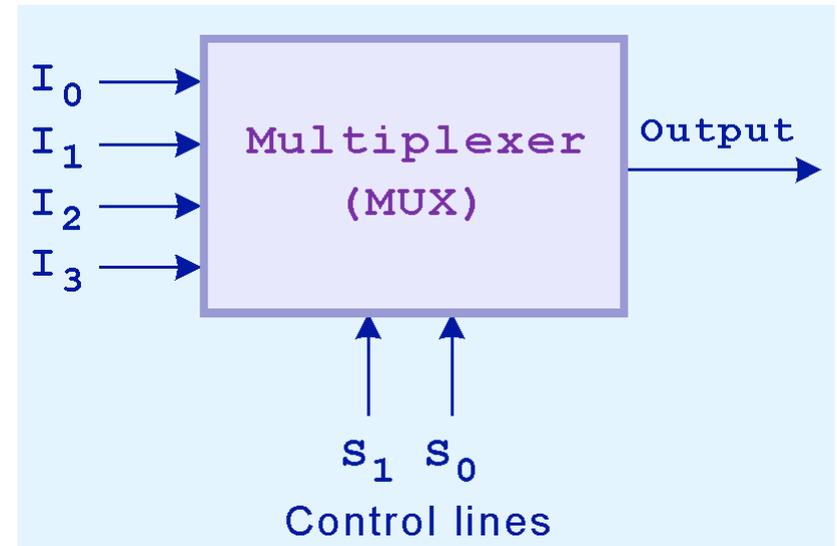-
- A multiplexer does just the opposite of a decoder.
 - It selects a single output from several inputs.
 - The particular input chosen for output is determined by the value of the multiplexer's control lines.
 - To be able to select among n inputs, $\log_2 n$ control lines are needed.



This is a block diagram for a multiplexer.

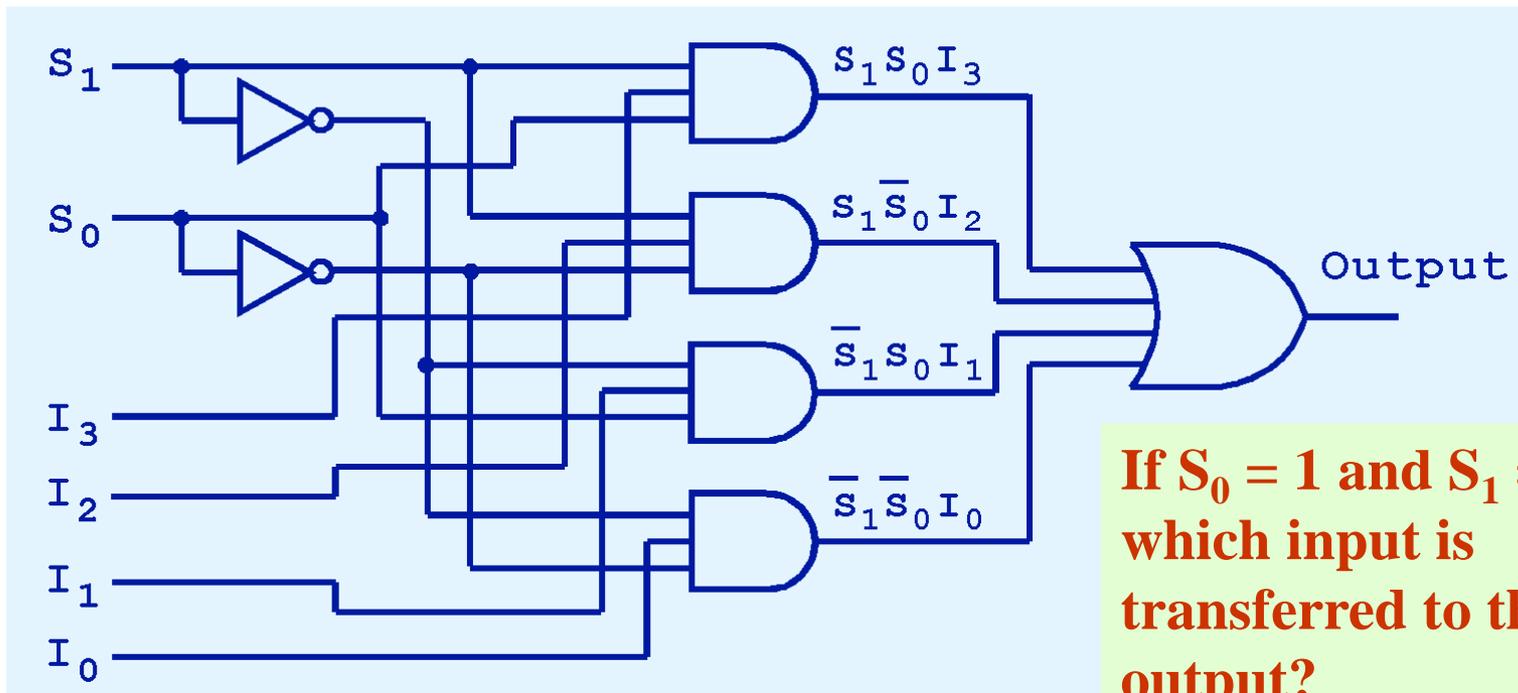- This is what a 4-to-1 multiplexer looks like on the inside.




**If $S_0 = 1$ and $S_1 = 0$,
which input is
transferred to the
output?**


Sequential Circuits

- Combinational logic circuits are perfect for situations when we require the immediate application of a Boolean function to a set of inputs.
- There are other times, however, when we need a circuit to change its value with consideration to its current state as well as its inputs.
 - These circuits have to “remember” their current state.
- *Sequential logic circuits* provide this functionality for us.

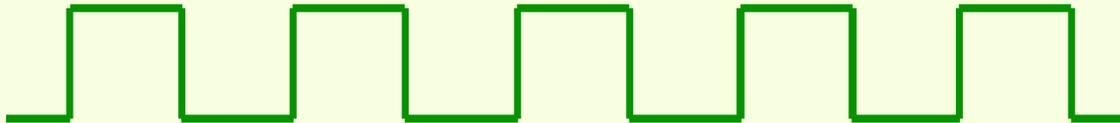
-
- As the name implies, sequential logic circuits require a means by which events can be sequenced.
 - State changes are controlled by clocks.
 - A “clock” is a special circuit that sends electrical pulses through a circuit.
 - Clocks produce electrical waveforms such as the one shown below.



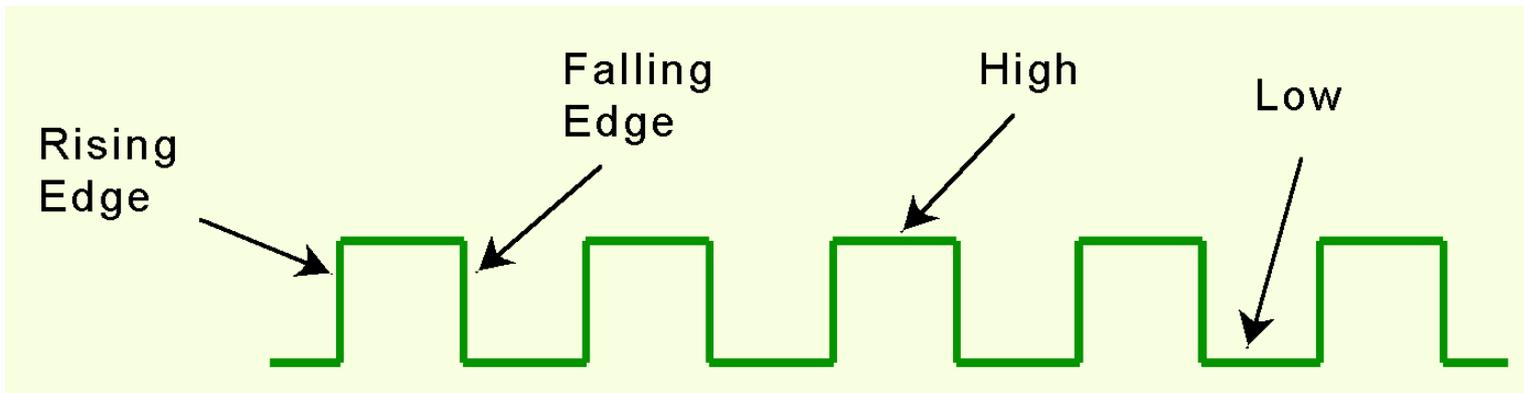
-
- State changes occur in sequential circuits only when the clock ticks.
 - Circuits can change state on the rising edge, falling edge, or when the clock pulse reaches its highest voltage.




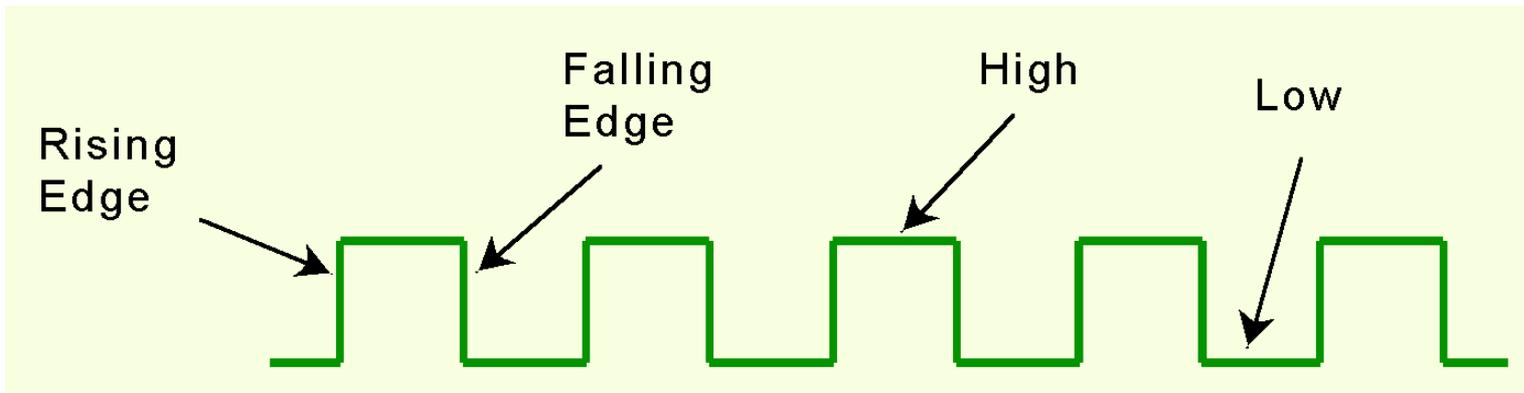
-
- Circuits that change state on the rising edge, or falling edge of the clock pulse are called *edge-triggered*.
 - *Level-triggered circuits* change state when the clock voltage reaches its highest or lowest level.



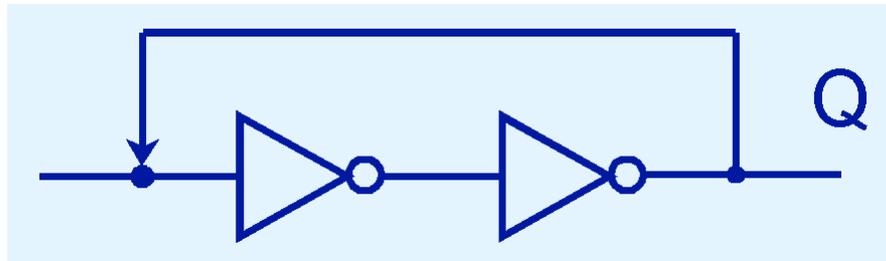
-
- To retain their state values, sequential circuits rely on *feedback*.
 - Feedback in digital circuits occurs when an output is looped back to the input.
 - A simple example of this concept is shown below.
 - If Q is 0 it will always be 0, if it is 1, it will always be 1. Why?



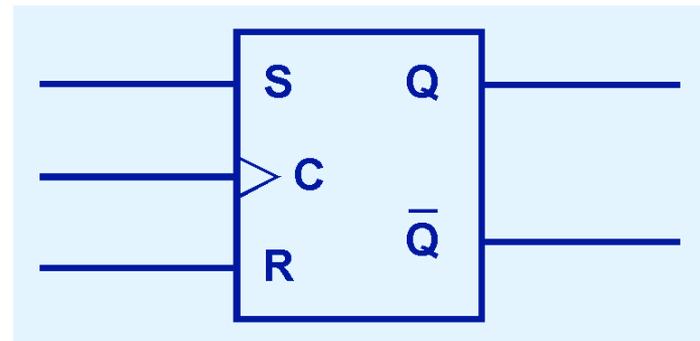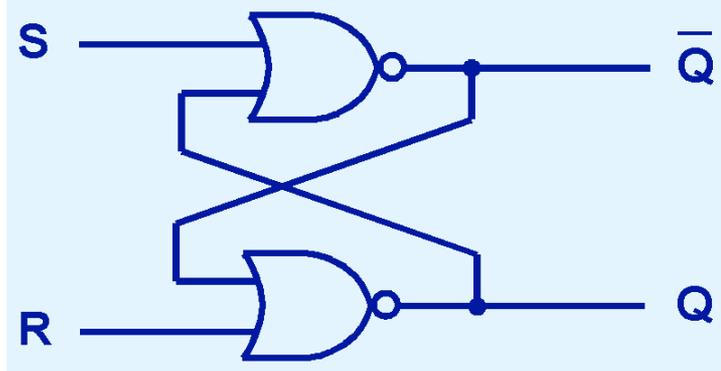-
- You can see how feedback works by examining the most basic sequential logic components, the SR flip-flop.
 - The “SR” stands for set/reset.
 - The internals of an SR flip-flop are shown below, along with its block diagram.



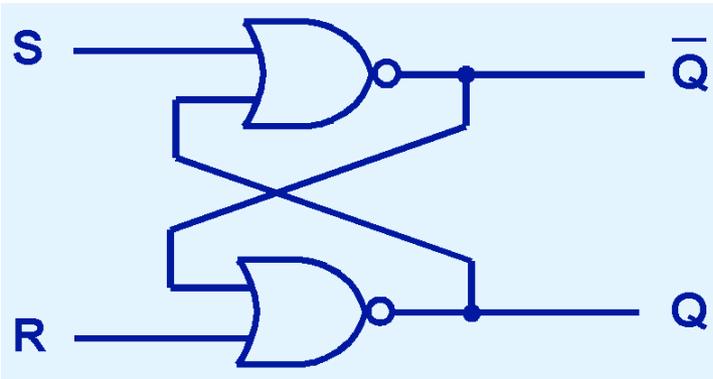-
- The behavior of an SR flip-flop is described by a characteristic table.
 - $Q(t)$ means the value of the output at time t . $Q(t+1)$ is the value of Q after the next clock pulse.




S	R	$Q(t+1)$
0	0	$Q(t)$ (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	undefined


- The SR flip-flop actually has three inputs: S, R, and its current output, Q.
- Thus, we can construct a truth table for this circuit, as shown at the right.
- Notice the two undefined values. When both S and R are 1, the SR flip-flop is unstable.

		Present State		Next State
S	R	Q (t)	Q (t+1)	
0	0	0	0	
0	0	1	1	
0	1	0	0	
0	1	1	0	
1	0	0	1	
1	0	1	1	
1	1	0	undefined	
1	1	1	undefined	

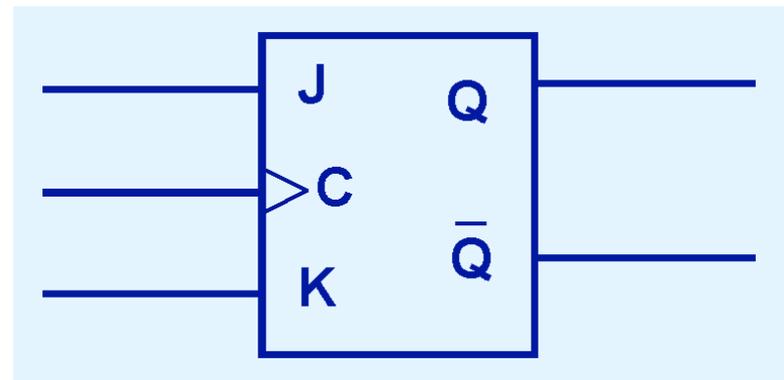-
- If we can be sure that the inputs to an SR flip-flop will never both be 1, we will never have an unstable circuit. This may not always be the case.
 - The SR flip-flop can be modified to provide a stable state when both inputs are 1.
 - This modified flip-flop is called a JK flip-flop, shown at the right.
 - The “JK” is in honor of Jack Kilby.




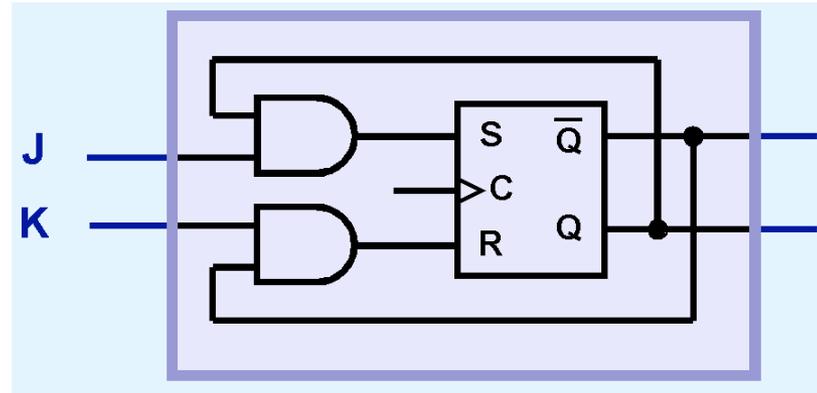- At the right, we see how an SR flip-flop can be modified to create a JK flip-flop.
- The characteristic table indicates that the flip-flop is stable for all inputs.




J	K	$Q(t+1)$
0	0	$Q(t)$ (no change)
0	1	0 (reset to 0)
1	0	1 (set to 1)
1	1	$\bar{Q}(t)$

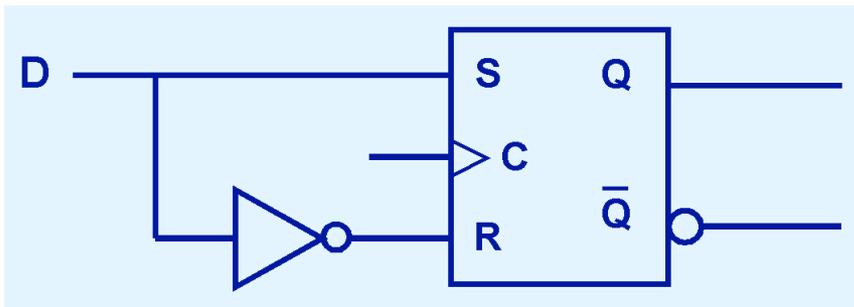-
- Another modification of the SR flip-flop is the D flip-flop, shown below with its characteristic table.
 - You will notice that the output of the flip-flop remains the same during subsequent clock pulses. The output changes only when the value of D changes.



D	$Q(t+1)$
0	0
1	1

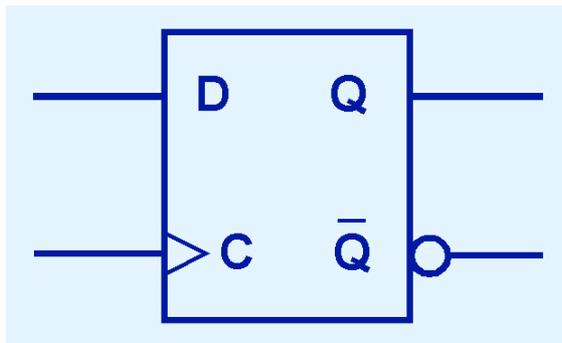-
- The D flip-flop is the fundamental circuit of computer memory.
 - D flip-flops are usually illustrated using the block diagram shown below.
 - The next slide shows how these circuits are combined to create a register.




D	$Q(t+1)$
0	0
1	1


- This illustration shows a 4-bit register consisting of D flip-flops. You will usually see its block diagram (below) instead.



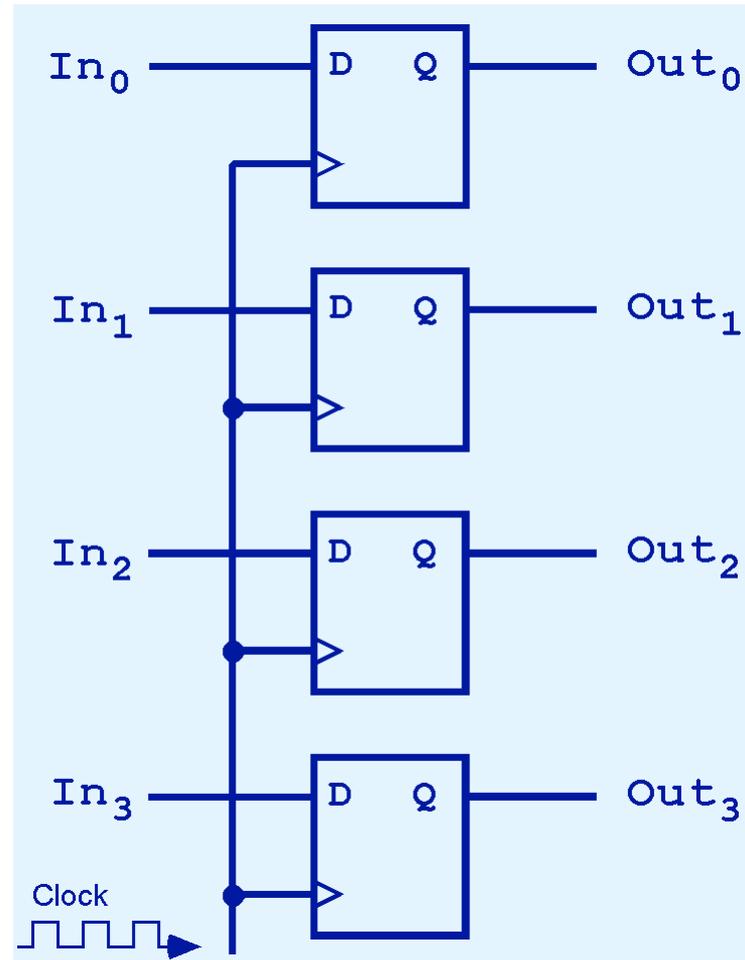A larger memory configuration is in your text.



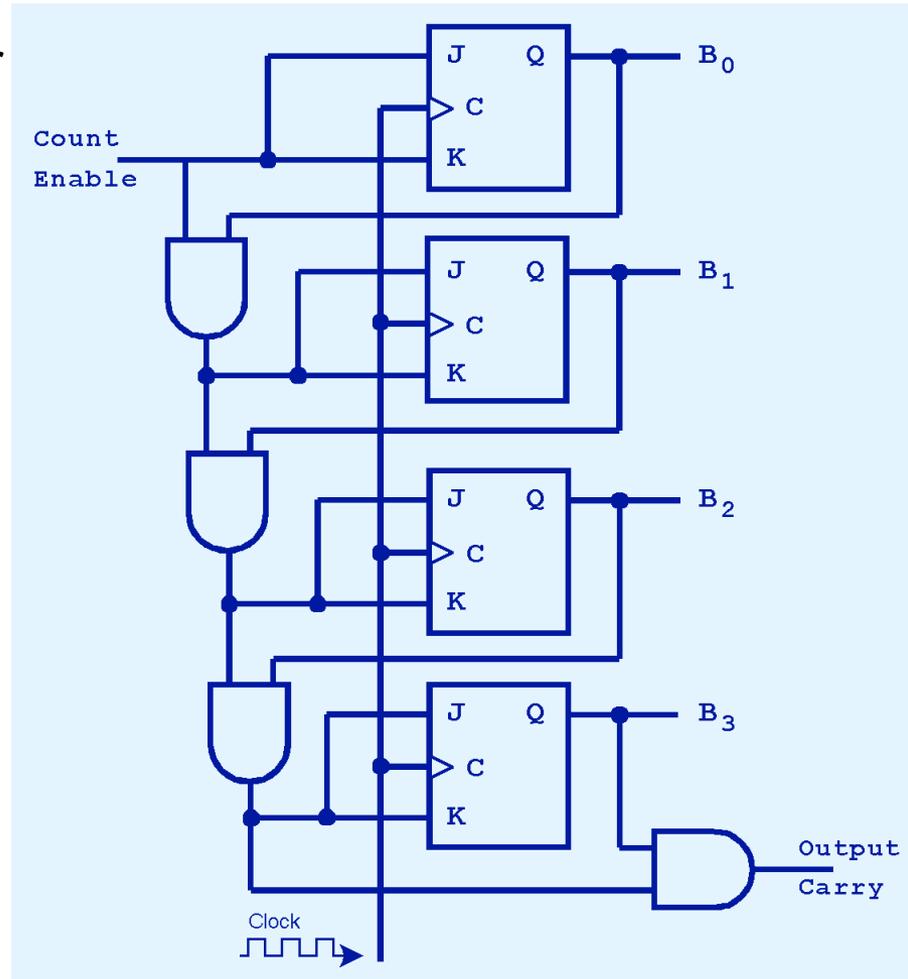- A binary counter is another example of a sequential circuit.
- The low-order bit is complemented at each clock pulse.
- Whenever it changes from 0 to 1, the next bit is complemented, and so on through the other flip-flops.



Designing Circuits

- We have seen digital circuits from two points of view: digital analysis and digital synthesis.
 - *Digital analysis* explores the relationship between a circuit's inputs and its outputs.
 - *Digital synthesis* creates logic diagrams using the values specified in a truth table.
- Digital systems designers must also be mindful of the physical behaviors of circuits to include minute propagation delays that occur between the time when a circuit's inputs are energized and when the output is accurate and stable.

-
- Digital designers rely on specialized software to create efficient circuits.
 - Thus, software is an enabler for the construction of better hardware.
 - Of course, software is in reality a collection of algorithms that could just as well be implemented in hardware.
 - Recall the Principle of Equivalence of Hardware and Software.

-
- When we need to implement a simple, specialized algorithm and its execution speed must be as fast as possible, a hardware solution is often preferred.
 - This is the idea behind *embedded systems*, which are small special-purpose computers that we find in many everyday things.
 - Embedded systems require special programming that demands an understanding of the operation of digital circuits, the basics of which you have learned in this chapter.