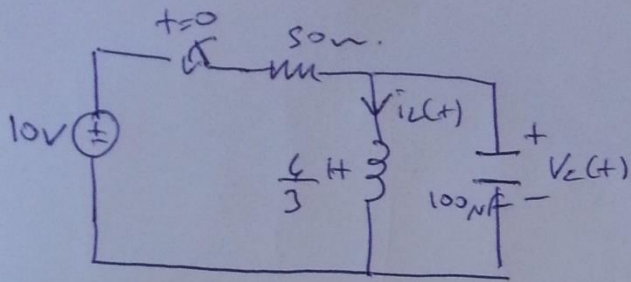


ex1



The circuit has no initial energy storage.
 Find $i_L(t)$.
 ↓
 inductor current.

Solution

This is a parallel RLC circuit.

$$\alpha = \frac{1}{2RC} \quad , \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\alpha = \frac{1}{2 \times 50 \times 100 \times 10^{-6}} = 100 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{\frac{4}{3} \times 100 \times 10^{-6}}} \approx 86.60 \text{ rad/sec.}$$


$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \approx -50$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \approx -150$$

$\alpha > \omega_0 \Rightarrow$ this is an overdamped circuit.


$$\text{so } i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + A_3$$

when $t \rightarrow \infty$, we have.

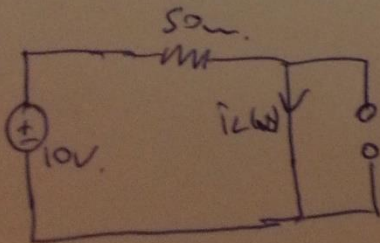

$$i_L(\infty) = \frac{10V}{50m} = 0.2A = \underline{\underline{A_3}}$$

for $t = 0^+$, we have.

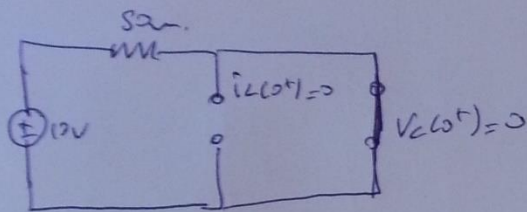

$$i_L(0^-) = i_L(0^+) = 0$$

$$V_C(0^-) = V_C(0^+) = 0$$

⇒ The first equation, for $t = 0^+$

$$i_L(0^+) = 0 \Rightarrow 0 = A_1 e^0 + A_2 e^0 + 0.2.$$

$$\boxed{A_1 + A_2 = -0.2}$$

The second equation, for $t = 0^+$

$$V_L = L \frac{di_L}{dt} \Rightarrow \frac{di_L(0^+)}{dt} = \frac{V_L(0^+)}{L}$$

$$V_L(0^+) = V_C(0^+) = 0$$

the voltage across inductor. The voltage across capacitor.

$$\frac{di_L(t)}{dt} = \frac{d(A_1 e^{s_1 t} + A_2 e^{s_2 t} + A_3)}{dt}$$

$$\frac{di_L(0^+)}{dt} = \frac{0}{\frac{4}{3} \text{H}} = 0 = A_1 s_1 e^0 + A_2 s_2 e^0$$

$$\Rightarrow -50A_1 - 150A_2 = 0$$

$$\boxed{-A_1 - 3A_2 = 0} \rightarrow \text{second Equ}$$

$$\Rightarrow A_1 + A_2 = -0.2$$

$$+ -A_1 - 3A_2 = 0$$

$$-2A_2 = -0.2$$

$$\boxed{A_2 = 0.1}$$


$$\boxed{A_1 = -0.3}$$

⇒

$$(i_L(t) = -0.3e^{-50t} + 0.1e^{-150t} + 0.2) + 70$$

②


Ex 2

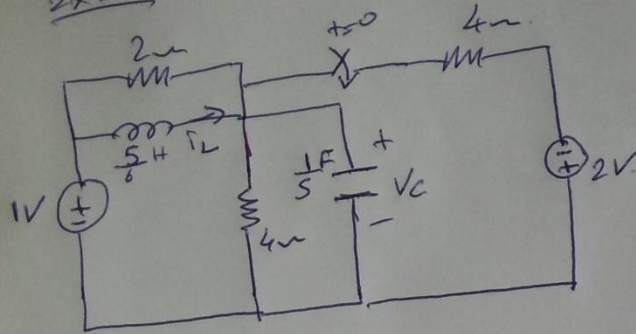

Find $V_C(t)$.

Solution


Before the switching, (for $t=0^-$)

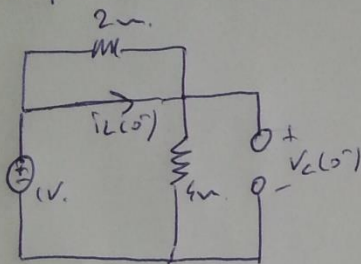

$$i_L(0^-) = \frac{1V}{4\Omega} = 0.25A$$

$$V_C(0^-) = 1V.$$

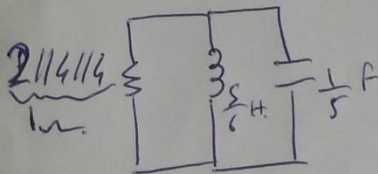\Rightarrow the zero input circuit (to find the natural response part)



\Rightarrow we can find α , ω_0 and the roots (s_1, s_2) from this circuit

\Rightarrow this is a parallel RLC circuit.


$$\alpha = \frac{1}{2RC} = 2.5 s^{-1}, \quad \omega_0 = \frac{1}{\sqrt{LC}} = 2.5 \text{ rad/s}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -2, \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -3$$

$\alpha > \omega_0$, so the circuit is overdamped.


$$V_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + A_3 \quad t > 0$$

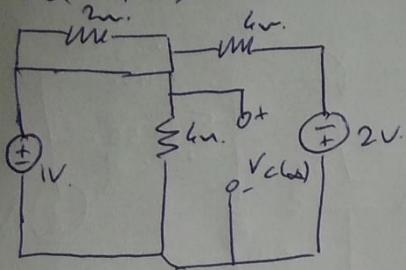When $t \rightarrow \infty$ (to find forced response)



$V_c(\infty) = 1V$. (parallel to 1V source)

at $t = 0^+$

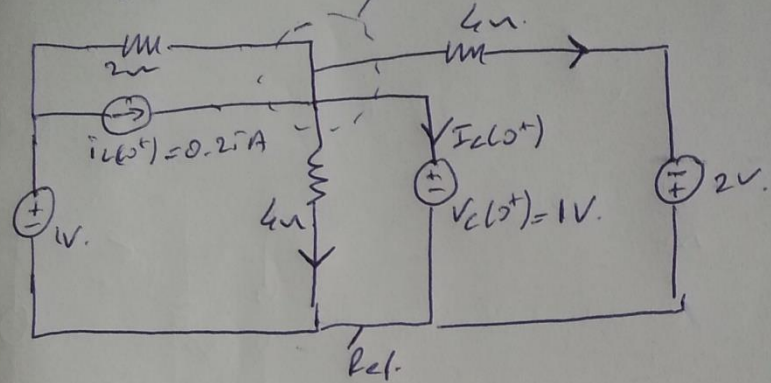

First Eq.

for $t = 0^+ \Rightarrow V_c(0^+) = 1V = A_1 e^0 + A_2 e^0 + 1$ $\nearrow A_3$
 $\Rightarrow \boxed{A_1 + A_2 = 0}$ \rightarrow first Eq.

Second Eq.

KCL $\Rightarrow 0.25 = \frac{1}{4} + \frac{(1 - (-2))}{4} + I_c(0^+)$

$\Rightarrow I_c(0^+) = -\frac{3}{4} = -0.75A$

\Rightarrow we know that

$I_c = C \frac{dV_c}{dt} \Rightarrow \frac{dV_c(0^+)}{dt} = \frac{I_c(0^+)}{C}$

$\Rightarrow \frac{-0.75}{\frac{1}{5}} = \frac{dV_c(0^+)}{dt} \Rightarrow \frac{dV_c(0^+)}{dt} = -3.75$

$\Rightarrow \frac{dV_c(t)}{dt} = \frac{d(A_1 e^{-2t} + A_2 e^{-3t} + A_3)}{dt} = -2A_1 e^{-2t} - 3A_2 e^{-3t} + 0 \Rightarrow$ for $t = 0^+$
 $\boxed{-2A_1 - 3A_2 = -3.75} \rightarrow$ second Eq.


$$\begin{array}{r} 2A_1 + A_2 = 0 \\ + -2A_1 - 3A_2 = -3.75 \\ \hline \end{array}$$

$$-A_2 = -3.75$$

$$\boxed{\begin{array}{l} A_2 = 3.75 \\ A_1 = -3.75 \end{array}}$$

$$\text{then } v_c(t) = (-3.75e^{-2t} + 3.75e^{-3t} + 1) \quad \underline{\underline{+ > 0}}$$


Ex 3

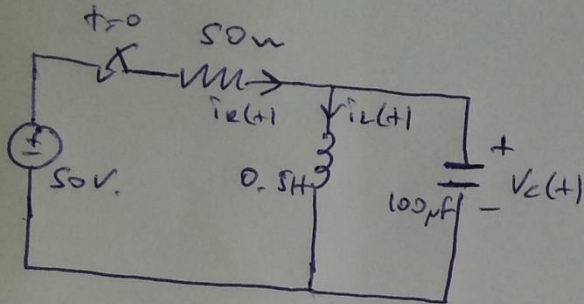

$i_L(0^-) = 2A$
 $V_C(0^-) = 0V$
 Find $i_R(t)$

Solution

Zero input circuit

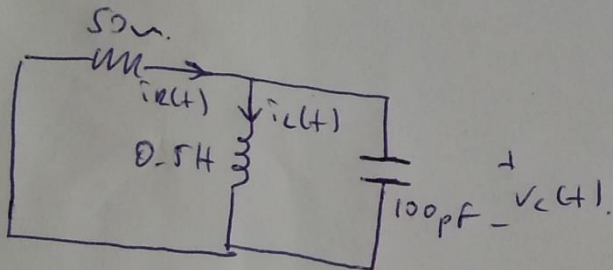

⇒ This is a parallel RLC circuit.


$\Rightarrow \alpha = \frac{1}{2RC} = 100 \text{ s}^{-1}$, $\omega_0 = \frac{1}{\sqrt{LC}} = 141.4 \text{ rad/s}$.

$\omega_0 > \alpha \Rightarrow$ so this circuit is overdamped.


$i_R(t) = e^{-\alpha t} [A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)] + A_3$

⇒ In order to find A_3 , we need to find $i_R(\omega)$.

when $t \rightarrow \infty$

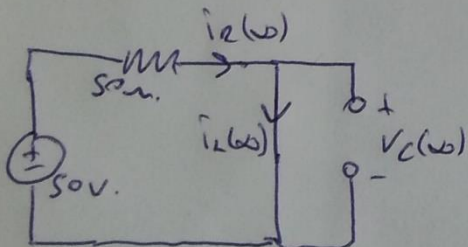

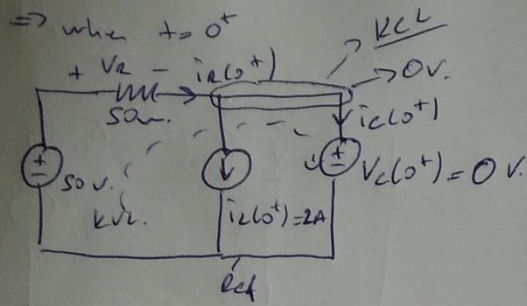$i_R(\omega) = \frac{50V}{50\Omega} = 1V = A_3$



$$i_R(t) = \frac{(50 - 0)V}{50 \Omega} = 1A$$

The first equation, when $t=0^+$

$$i_R(t) = 1A = e^0 [\underbrace{A_1 \cos 0}_1 + \underbrace{A_2 \sin 0}_0] + \underbrace{A_3}_{1A}$$

$$\Rightarrow 1A = A_1 + 1 \Rightarrow \boxed{A_1 = 0}$$

The second equation, (we need to find the derivative of $i_R(t)$)

$$I_C = C \frac{dV_C}{dt} \Rightarrow \frac{dV_C}{dt} = \frac{I_C}{C}$$

when we apply KCL, for $t=0^+$

$$\frac{50 - 0}{50} = 2A + i_C(t) \Rightarrow \boxed{i_C(t) = -1A}$$

$$\Rightarrow \frac{dV_C(t)}{dt} = \frac{-1}{100 \times 10^{-6}} = -10000$$

⇒ if we write $V_C(t)$ in terms of $i_R(t)$.

$$KVL \Rightarrow -50 + V_R(t) + V_C(t) = 0$$

$$V_C(t) = 50 - V_R(t) \Rightarrow V_C(t) = \boxed{50 - i_R(t) \times 50}$$

↳ if we use this equation instead of $V_C(t)$.

(2)

$$\frac{d(V_c(t^+))}{dt} = -10000$$

$$\Rightarrow \frac{d(50 - 50 i_R(t^+))}{dt} = -10000$$

$$\Rightarrow -50 \frac{d i_R(t^+)}{dt} = -10000$$

$$\frac{d i_R(t^+)}{dt} = \frac{+10000}{-50} = -200$$

the second equation,

for $t=0^+$

$$-x e^{-x t} [A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t)] + e^{-x t} [A_1 \omega_d \sin(\omega_d t) + A_2 \omega_d \cos(\omega_d t)]$$

$$\Rightarrow -100 e^{-100 t} [A_2 \sin(\omega_d t)] + e^{-100 t} [A_2 \omega_d \cos(\omega_d t)]$$

for $t \rightarrow 0$,

$$-100 e^0 [A_2 \sin 0] + e^0 [A_2 \omega_d \cos 0] = 200$$

$$\omega_d = \sqrt{\omega_0^2 - x^2} \approx 100 \text{ rad/sec.}$$

\Rightarrow

$$A_2 100 = 200$$

$$A_2 = \frac{200}{100} = 2$$

So the final formula of $i_R(t)$.

$$e^{-100 t} [2 \sin(100 t)] + 1 = i_R(t) \quad \text{for } t > 0$$

$$i_R(t) = 2 e^{-100 t} \sin(100 t) + 1 \quad \text{for } t > 0$$