

# BME2301 - Circuit Theory

## The Instructors:

Dr. Görkem SERBES (C317)

[gserbes@yildiz.edu.tr](mailto:gserbes@yildiz.edu.tr)

<https://avesis.yildiz.edu.tr/gserbes/>

## Lab Assistants:

Nihat AKKAN

[nakkan@yildiz.edu.tr](mailto:nakkan@yildiz.edu.tr)

<https://avesis.yildiz.edu.tr/nakkan>

# Objectives of the Lecture

- Present Kirchhoff's Current and Voltage Laws.
- Demonstrate how these laws can be used to find currents and voltages in a circuit.
- Explain how these laws can be used in conjunction with Ohm's Law.

**Important Note : Laboratory Sections of the course will start in the 3rd week. Follow Nihat Akkan's Avesis Web Page.**

# Resistivity, $\rho$

- Resistivity is a material property
  - Dependent on the number of free or mobile charges (usually electrons) in the material.
    - In a metal, this is the number of electrons from the outer shell that are ionized and become part of the ‘sea of electrons’
  - Dependent on the mobility of the charges
    - Mobility is related to the velocity of the charges.
    - It is a function of the material, the frequency and magnitude of the voltage applied to make the charges move, and temperature.


# Resistivity of Common Materials at Room Temperature (300K)

Material	Resistivity ( $\Omega\text{-cm}$ )	Usage
Silver	$1.64 \times 10^{-8}$	Conductor
Copper	$1.72 \times 10^{-8}$	Conductor
Aluminum	$2.8 \times 10^{-8}$	Conductor
Gold	$2.45 \times 10^{-8}$	Conductor
Carbon (Graphite)	$4 \times 10^{-5}$	Conductor
Germanium	0.47	Semiconductor
Silicon	640	Semiconductor
Paper	$10^{10}$	Insulator
Mica	$5 \times 10^{11}$	Insulator
Glass	$10^{12}$	Insulator
Teflon	$3 \times 10^{12}$	Insulator

# Resistance, R

- Resistance takes into account the physical dimensions of the material

$$R = \rho \frac{L}{A}$$

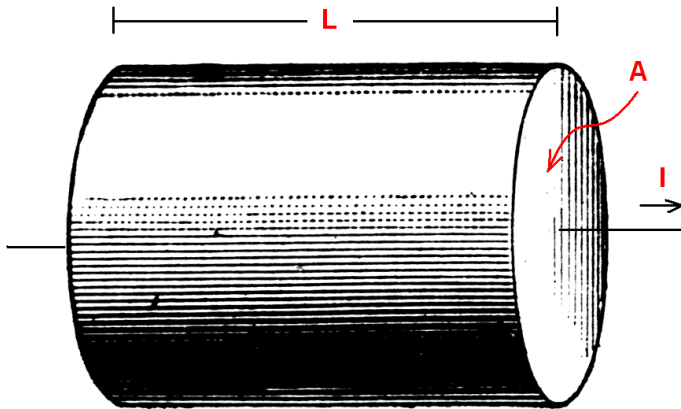

— where:

- L is the length along which the carriers are moving
- A is the cross sectional area that the free charges move through.

# Ohm's Law


- Voltage drop across a resistor is proportional to the current flowing through the resistor

$$V = iR$$

Units:  $V = A\Omega$

where  $A = C/s$

# Short Circuit

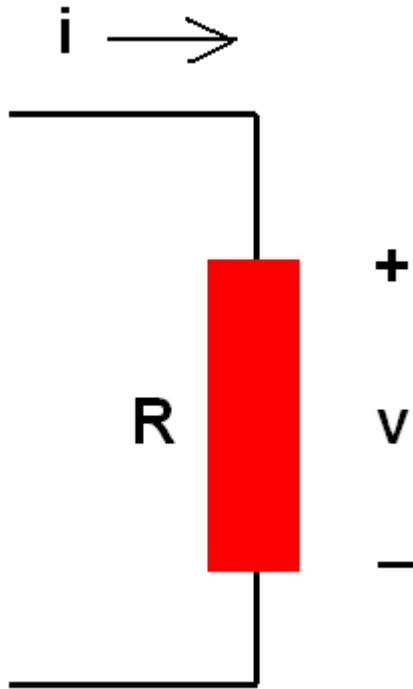

- If the resistor is a perfect conductor (or a short circuit)


$$R = 0 \, \Omega,$$

- then

$$v = iR = 0 \, \text{V}$$

- no matter how much current is flowing through the resistor

# Open Circuit

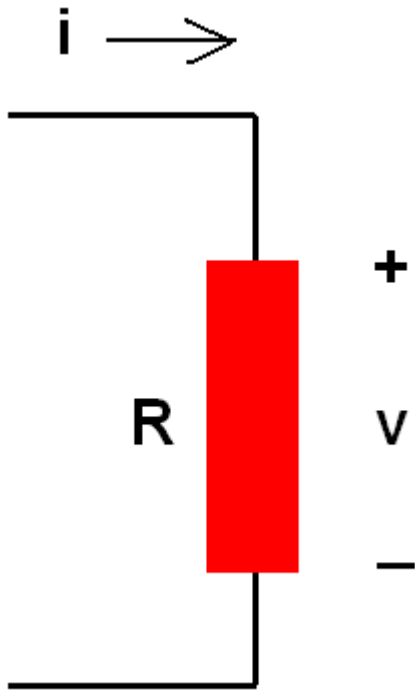

- If the resistor is a perfect insulator,  $R = \infty \Omega$

- then

$$i = \lim_{R \rightarrow \infty} \frac{v}{R} = 0$$

- no matter how much voltage is applied to (or dropped across) the resistor.



# Conductance, G

- Conductance is the reciprocal of resistance

$$G = R^{-1} = i/v$$

– Unit for conductance is S (siemens) or (mhos,  $\Omega^{-1}$ )

$$G = A\sigma/L$$

where  $\sigma$  is conductivity,

which is the inverse of resistivity,  $\rho$

# Power Dissipated by a Resistor

$$p = iv = i(iR) = i^2R$$

$$p = iv = (v/R)v = v^2/R$$

$$p = iv = i(i/G) = i^2/G$$

$$p = iv = (vG)v = v^2G$$

# Power (con't)

- Since  $R$  and  $G$  are always real positive numbers
  - Power dissipated by a resistor is always positive
- The power consumed by the resistor is not linear with respect to either the current flowing through the resistor or the voltage dropped across the resistor
  - This power is released as heat. Thus, resistors get hot as they absorb power (or dissipate power) from the circuit.

# Short and Open Circuits

- There is no power dissipated in a short circuit.


$$p_{sc} = v^2 R = (0\text{V})^2 (0\Omega) = 0\text{W}$$

- There is no power dissipated in an open circuit.


$$p_{oc} = i^2 / R = (0\text{A})^2 / (\infty\Omega) = 0\text{W}$$
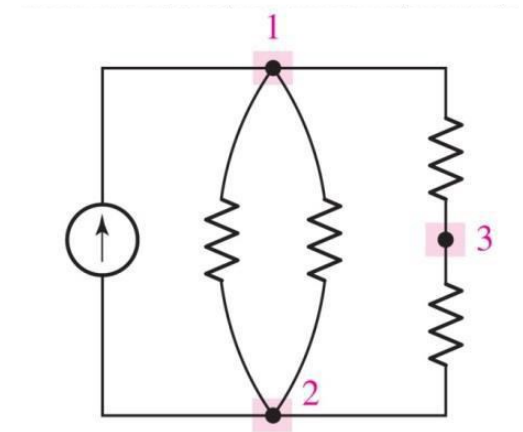
# Circuit Terminology

- Node
  - point at which 2+ elements have a common connection
    - e.g., node 1, node 2, node 3
- Path
  - a route through a network, through nodes that never repeat
    - e.g.,  $1 \rightarrow 3 \rightarrow 2$ ,  $1 \rightarrow 2 \rightarrow 3$
- Loop
  - a path that starts & ends on the same node
    - e.g.,  $3 \rightarrow 1 \rightarrow 2 \rightarrow 3$
- Branch
  - a single path in a network; contains one element and the nodes at the 2 ends
    - e.g.,  $1 \rightarrow 2$ ,  $1 \rightarrow 3$ ,  $3 \rightarrow 2$




(a)

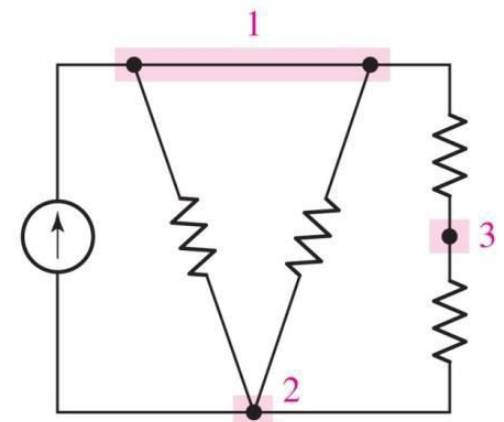

(b)
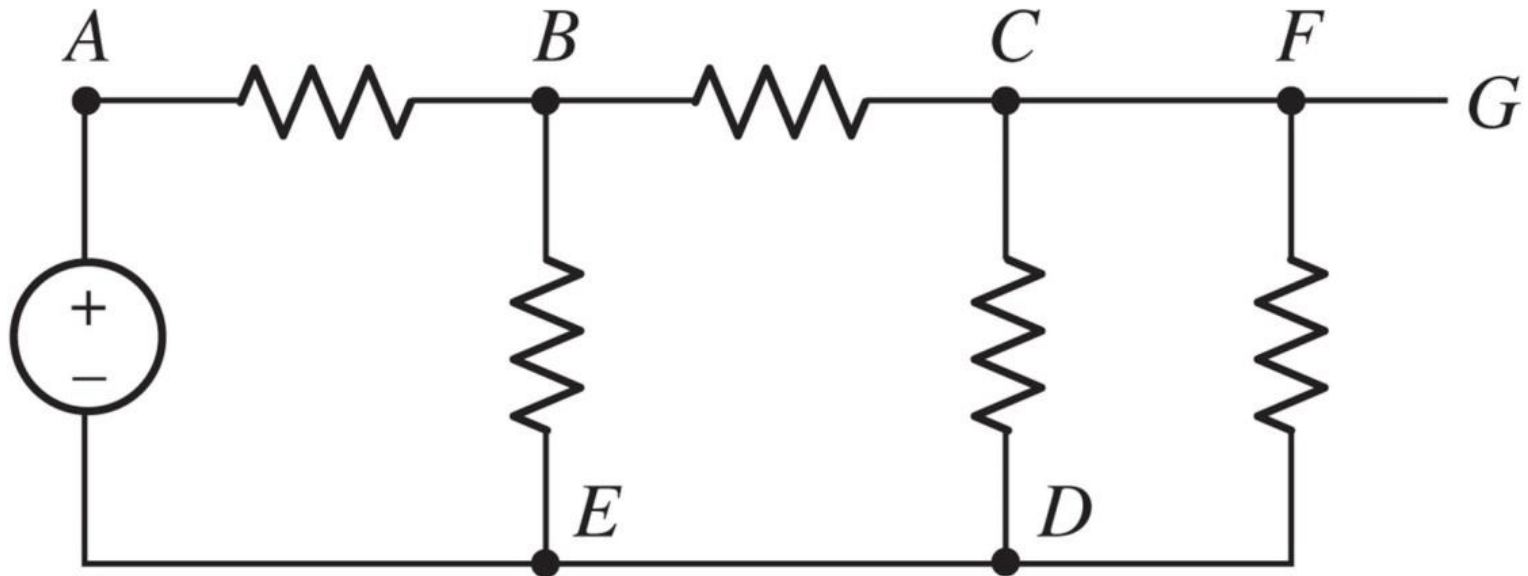
# Exercise

- For the circuit below:
  - Count the number of circuit elements.
  - If we move from  $B$  to  $C$  to  $D$ , have we formed a path and/or a loop?
  - If we move from  $E$  to  $D$  to  $C$  to  $B$  to  $E$ , have we formed a path and/or a loop?



# Kirchhoff's Current Law (KCL)

- Gustav Robert Kirchhoff: German university professor, born while Ohm was experimenting
- Based upon conservation of charge

$$\sum_{n=1}^N i_n = 0$$

Where N is the total number of branches connected to a node.


– the algebraic sum of the charge within a system can not change.

– the algebraic sum of the currents entering any node is zero.

$$\sum_{\text{node}} i_{\text{enter}} = \sum_{\text{node}} i_{\text{leave}}$$

$$i_A + i_B - i_C - i_D = 0$$

$$-i_A - i_B + i_C + i_D = 0$$

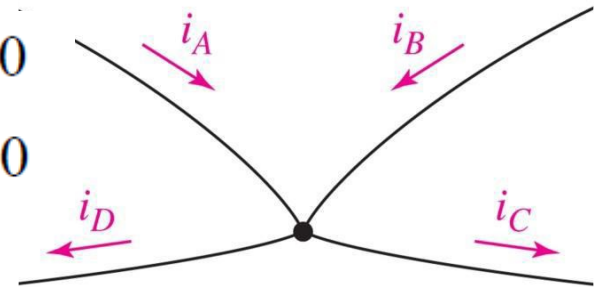


# Kirchhoff's Voltage Law (KVL)

- Based upon conservation of energy
  - the algebraic sum of voltages dropped across components around a loop is zero.
  - The energy required to move a charge from point A to point B must have a value independent of the path chosen.

$$\sum_{m=1}^M V = 0$$

Where M is the total number of branches in the loop.
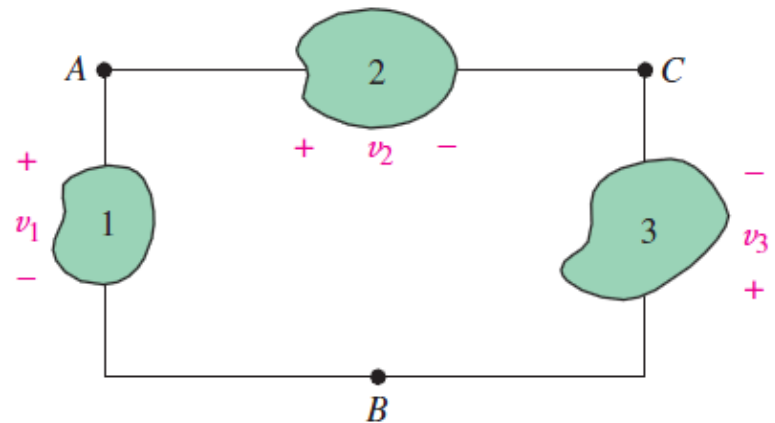
$$\sum V_{\text{drops}} = \sum V_{\text{rises}}$$





$$-v_1 + v_2 - v_3 = 0$$

$$v_1 - v_2 + v_3 = 0$$


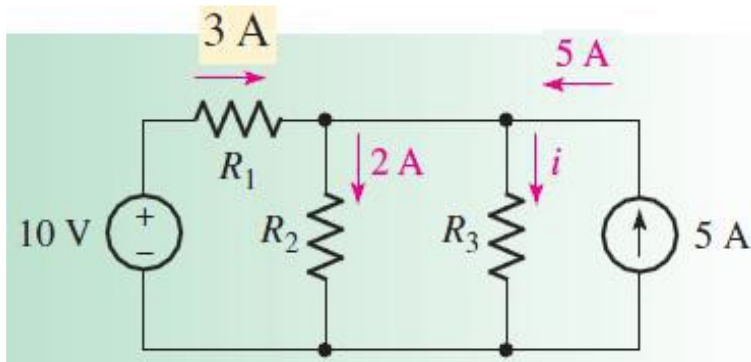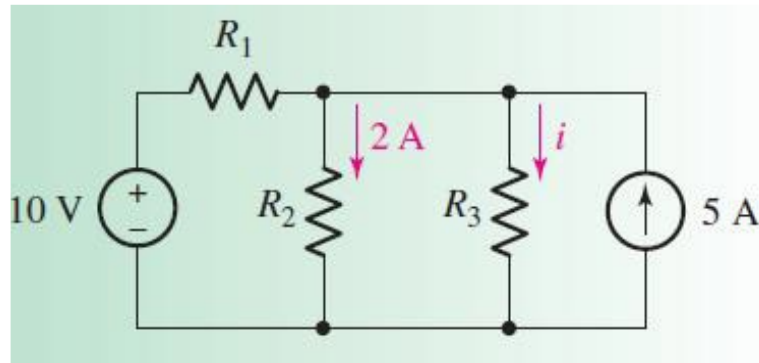
# Example-01

- For the circuit, compute the current through  $R_3$  if it is known that the voltage source supplies a current of 3 A.
- Use KCL



$$3 - 2 - i + 5 = 0$$

$$i = 3 - 2 + 5 = 6 \text{ A}$$

# Example-02

- Referring to the single node below, compute:

*a.*  $i_B$ , given  $i_A = 1$  A,  $i_D = -2$  A,  $i_C = 3$  A, and  $i_E = 4$  A

*b.*  $i_E$ , given  $i_A = -1$  A,  $i_B = -1$  A,  $i_C = -1$  A, and  $i_D = -1$  A

- Use KCL


$$i_A + i_B - i_C - i_D - i_E = 0$$

*a.*  $i_B = -i_A + i_C + i_D + i_E$

$$i_B = -1 + 3 - 2 + 4 = 4 \text{ A}$$


*b.*  $i_E = i_A + i_B - i_C - i_D$

$$i_E = -1 - 1 + 1 + 1 = 0 \text{ A}$$

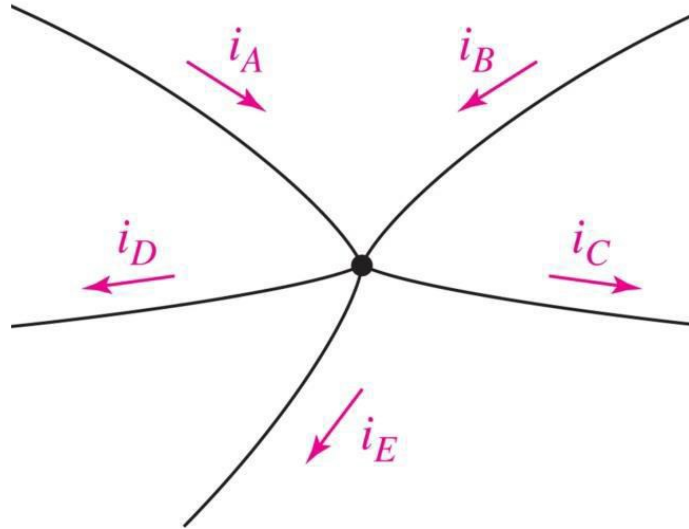
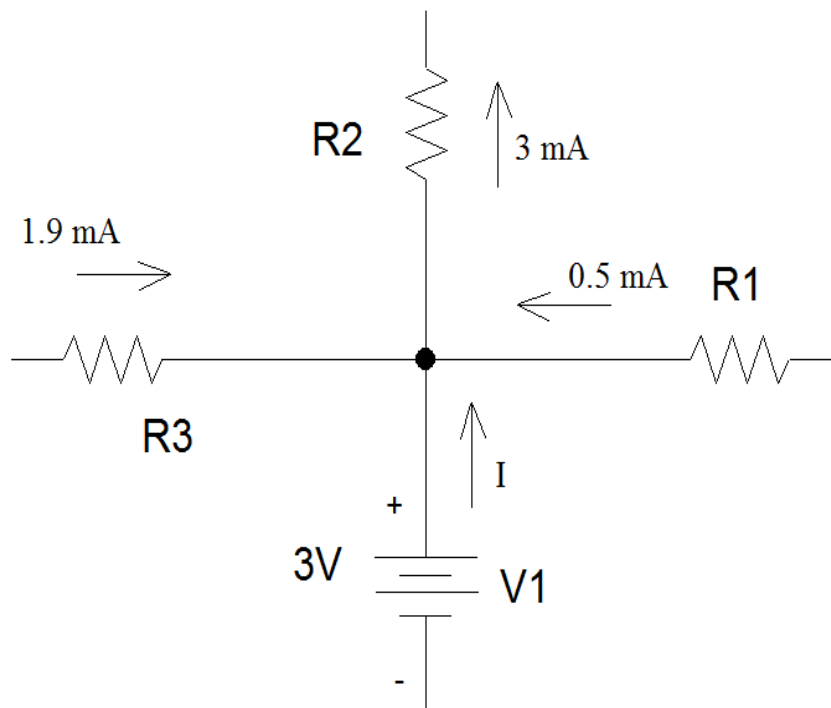
# Example-03

- Determine  $I$ , the current flowing out of the voltage source.



– Use KCL

- $1.9 \text{ mA} + 0.5 \text{ mA} + I$  are entering the node.
- $3 \text{ mA}$  is leaving the node.

$$1.9 \text{ mA} + 0.5 \text{ mA} + I = 3 \text{ mA}$$


$$I = 3 \text{ mA} - (1.9 \text{ mA} + 0.5 \text{ mA})$$

$$I = 0.6 \text{ mA}$$

$V1$  is generating power.
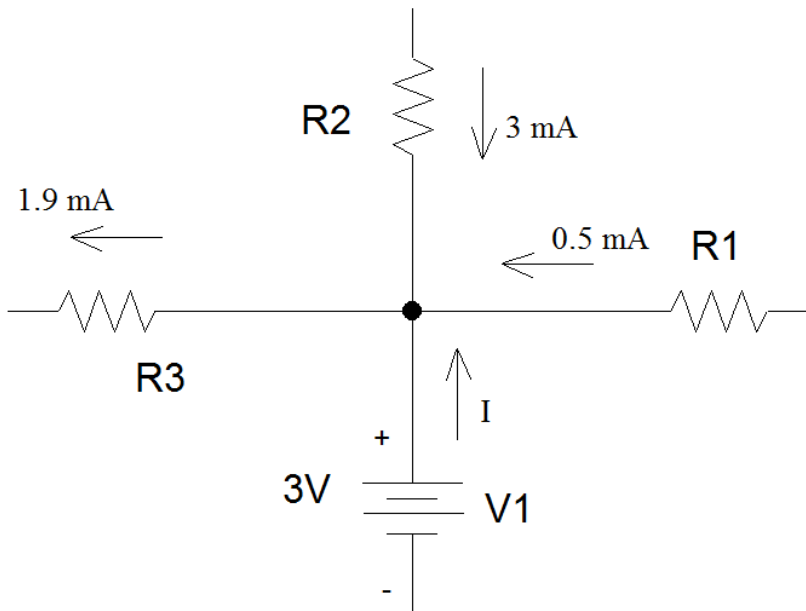
# Example-04

- Suppose the current through R2 was entering the node and the current through R3 was leaving the node.



– Use KCL

- 3 mA + 0.5 mA + I are entering the node.
- 1.9 mA is leaving the node.

$$3mA + 0.5mA + I = 1.9mA$$


$$I = 1.9mA - (3mA + 0.5mA)$$

$$I = -1.6mA$$

V1 is dissipating power.
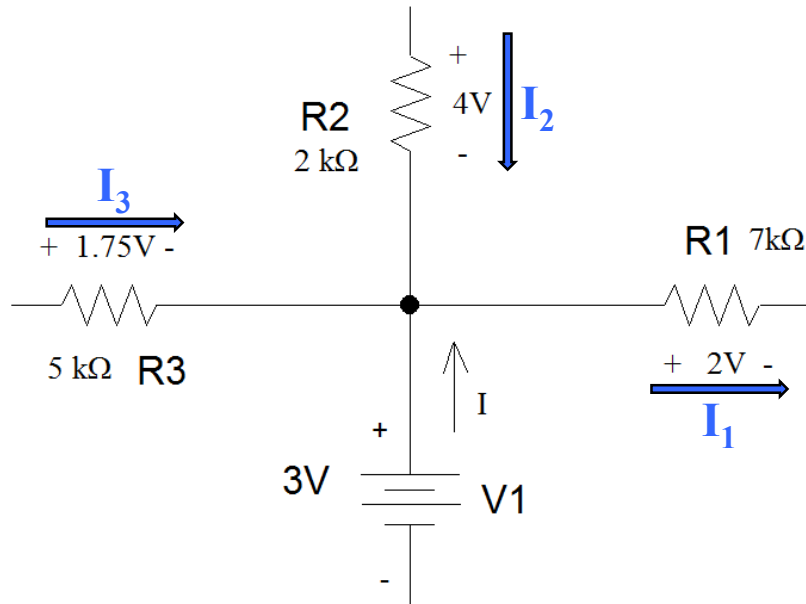
# Example-05

- If voltage drops are given instead of currents,



- you need to apply Ohm's Law to determine the current flowing through each of the resistors before you can find the current flowing out of the voltage supply.

- $I_1$  is leaving the node.
- $I_2$  is entering the node.
- $I_3$  is entering the node.
- $I$  is entering the node.

$$I_1 = 2V / 7k\Omega = 0.286mA$$

$$I_2 = 4V / 2k\Omega = 2mA$$

$$I_3 = 1.75V / 5k\Omega = 0.35mA$$



$$I_2 + I_3 + I = I_1$$

$$2mA + 0.35mA + I = 0.286mA$$

$$I = 0.286mA - 2.35mA = -2.06mA$$
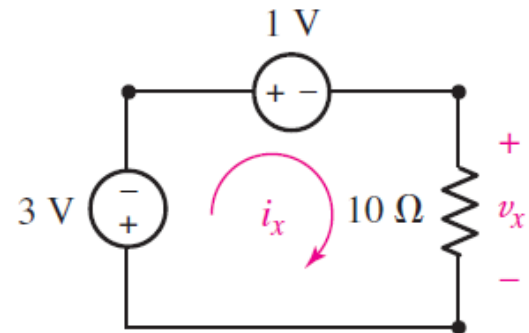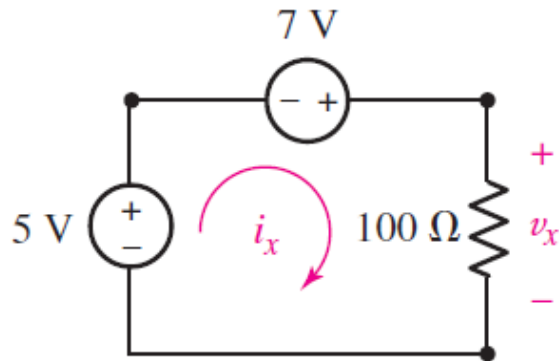
# Example-06

- For each of the circuits in the figure below, determine the voltage  $v_x$  and the current  $i_x$ .



– Applying KVL clockwise around the loop and Ohm's law

$$-5 - 7 + v_x = 0$$

$$v_x = 12 \text{ V}$$

$$i_x = \frac{v_x}{100} = \frac{12}{100} \text{ A} = 120 \text{ mA}$$

$$+ 3 + 1 + v_x = 0$$

$$v_x = \underline{-4 \text{ V}}$$


$$i_x = \frac{v_x}{10} = \underline{-400 \text{ mA}}$$

# Example-07

- For the circuit below, determine

a.  $v_{R2}$

b.  $v_x$

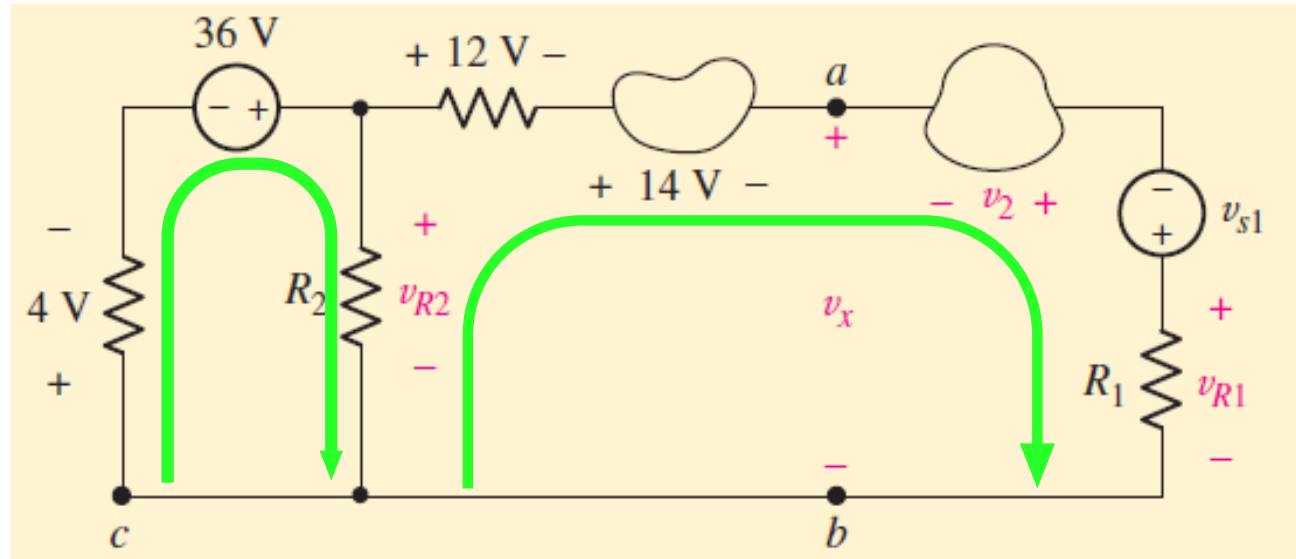

a.  $4 - 36 + v_{R2} = 0$

$v_{R2} = 32 \text{ V}$

b.  $-32 + 12 + 14 + v_x = 0$


$v_x = 6 \text{ V}$

# Example-08

- For the circuit below, determine

a.  $v_{R2}$

b.  $v_x$  if  $v_{R1} = 1$  V.

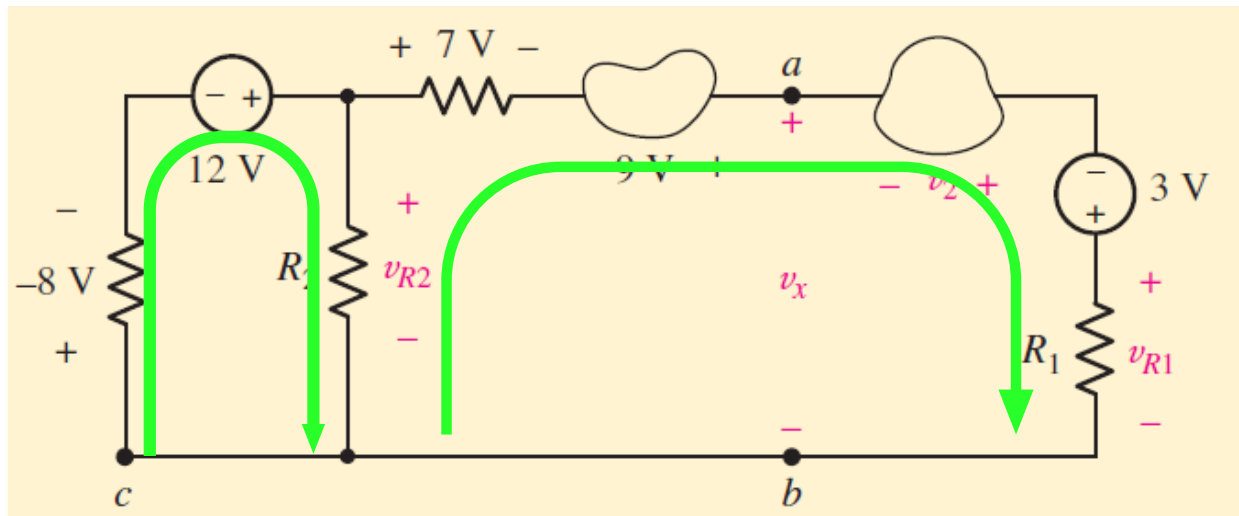

a. KVL yields  $-8 - 12 + v_{R2} = 0$        $v_{R2} = 20$  V


b. KVL yields  $-20 + 7 - 9 - v_2 - 3 + v_{R1}$

where  $v_{R1} = 1$  V. Thus,  $v_2 = -24$  V


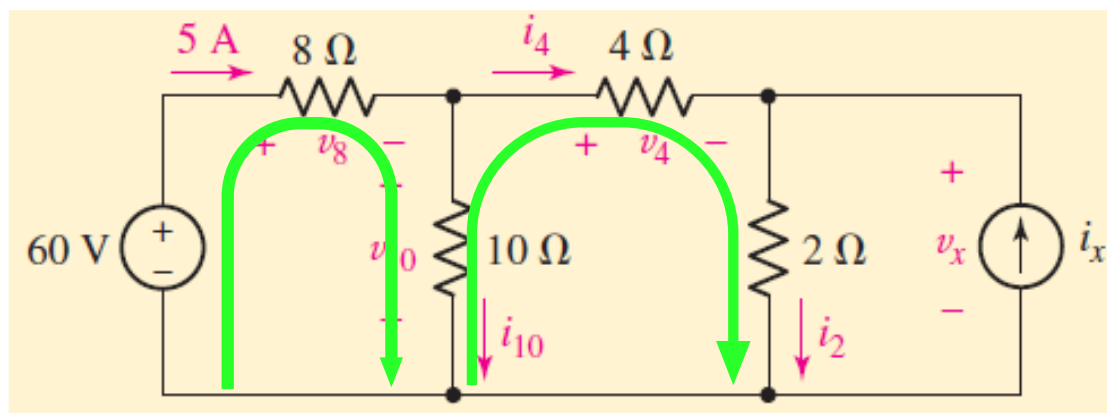
# Example-09

- For the circuit below, determine  $v_x$



$$-60 + v_8 + v_{10} = 0$$

$$v_{10} = 0 + 60 - 40 = 20 \text{ V}$$

$$-v_{10} + v_4 + v_x = 0$$

$$v_x = 20 - v_4$$


$$i_4 = 5 - i_{10} = 5 - \frac{v_{10}}{10} = 5 - \frac{20}{10} = 3$$

$$v_4 = (4)(3) = 12 \text{ V}$$

$$v_x = 20 - 12 = 8 \text{ V}$$
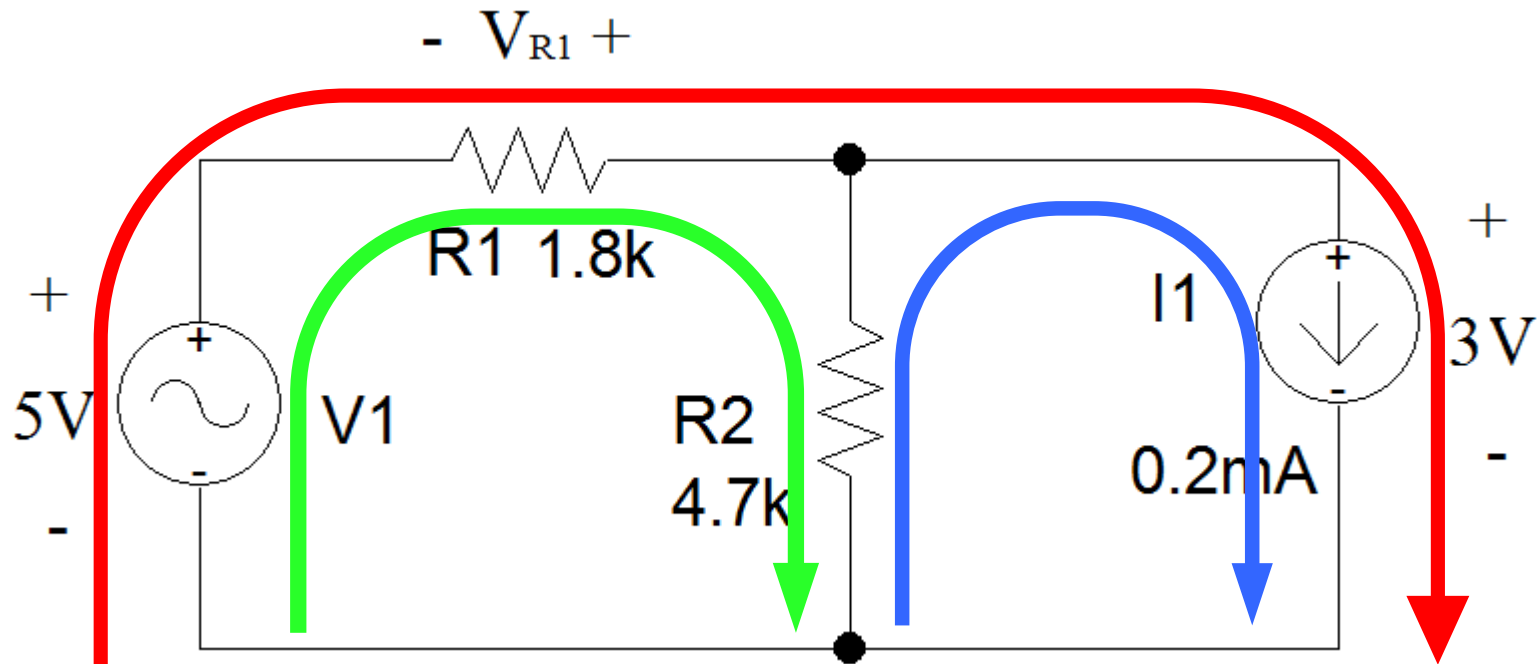
# Example-10...

- Find the voltage across R1.
  - Note that the polarity of the voltage has been assigned in the circuit schematic.




– First, define a loop that include R1.

# ...Example-10...

- If the red loop is considered

$$- V_{R1} +$$

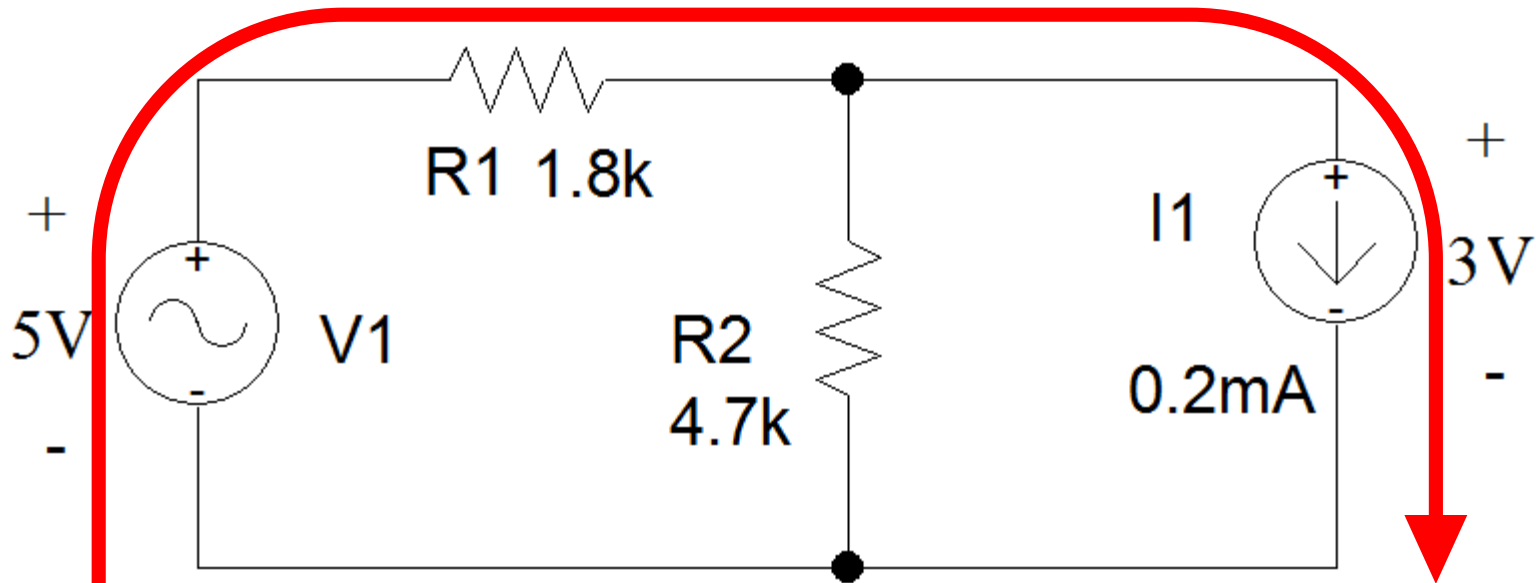


- By convention, voltage drops are added and voltage rises are subtracted in KVL.

$$-5 \text{ V} - V_{R1} + 3 \text{ V} = 0$$

$$V_{R1} = 2 \text{ V}$$
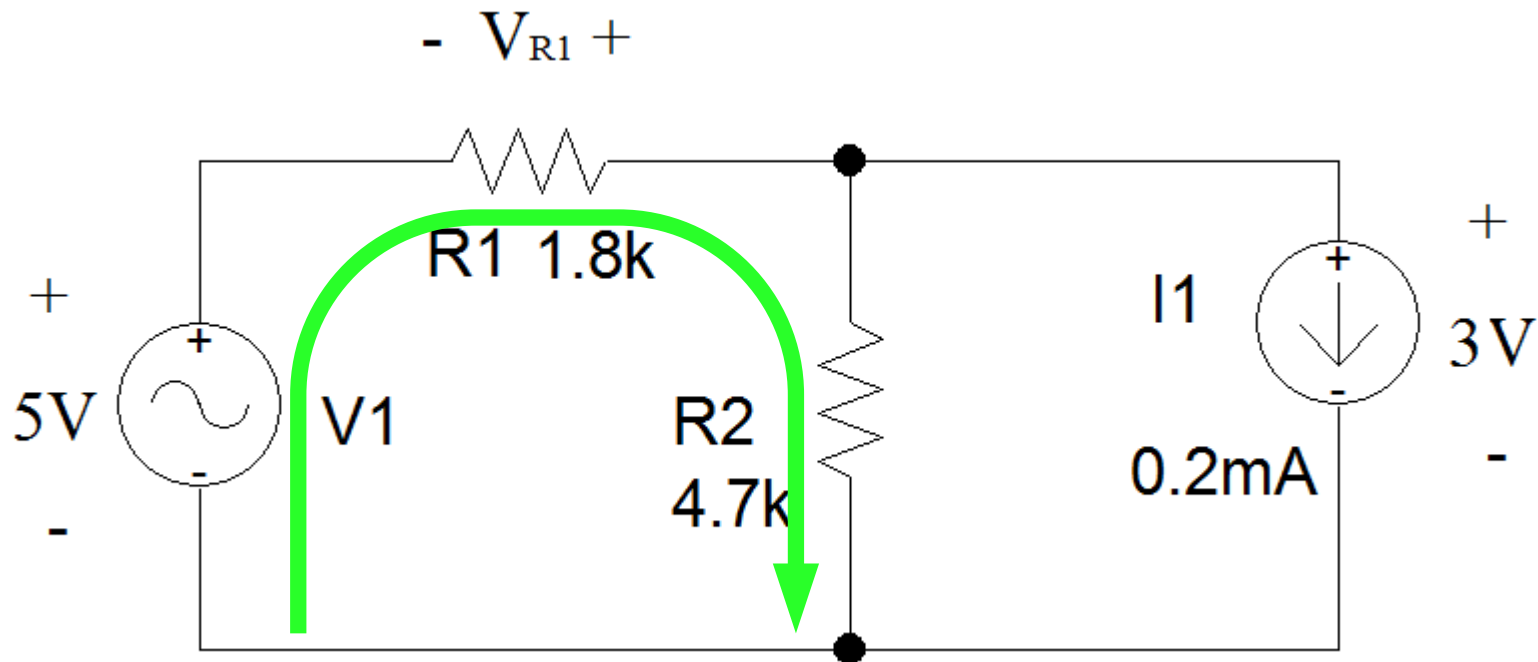
# ...Example-10

- Suppose you chose the green loop instead.
  - Since  $R_2$  is in parallel with  $I_1$ , the voltage drop across  $R_2$  is also 3V.




$$-5 \text{ V} - V_{R1} + 3 \text{ V} = 0$$

$$V_{R1} = 2 \text{ V}$$
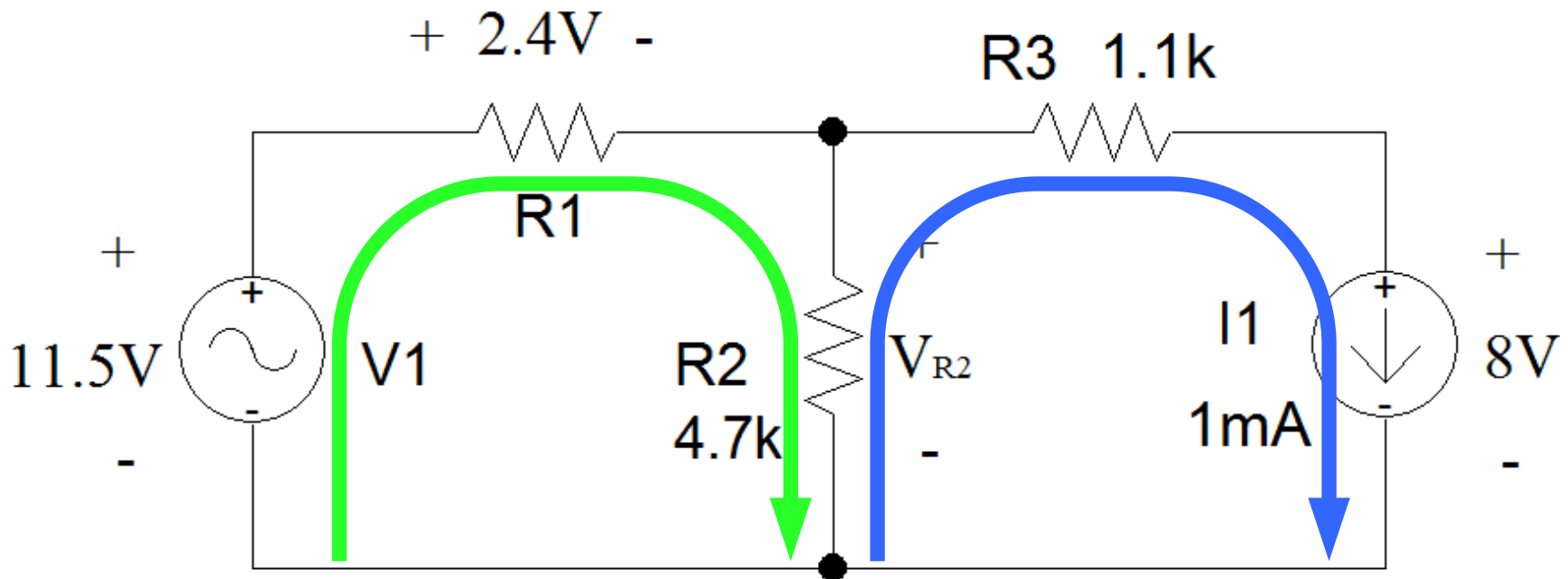
# Example-11...


- Find the voltage across  $R_2$  and the current flowing through it.



– First, draw a loop that includes  $R_2$ .

# ...Example-11...

- If the green loop is used:

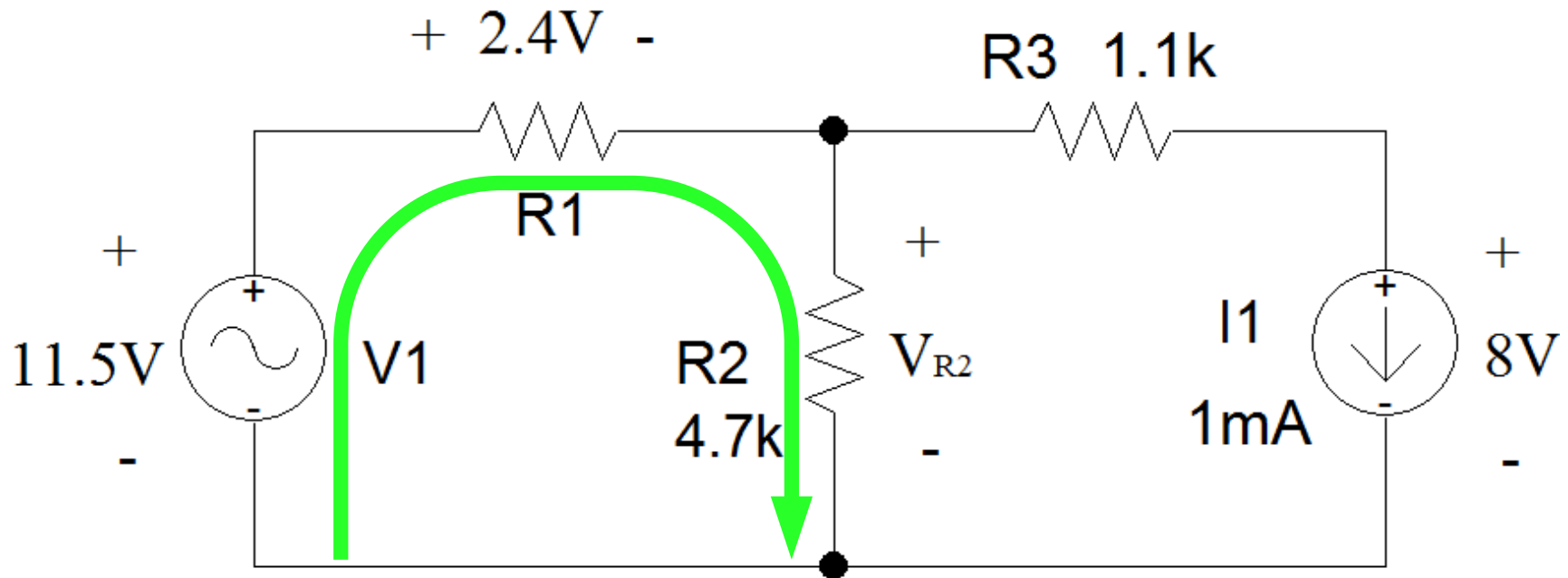


$$-11.5 \text{ V} + 2.4 \text{ V} + V_{R2} = 0$$

$$V_{R2} = 9.1 \text{ V}$$

# ...Example-11...

- If the blue loop is used:

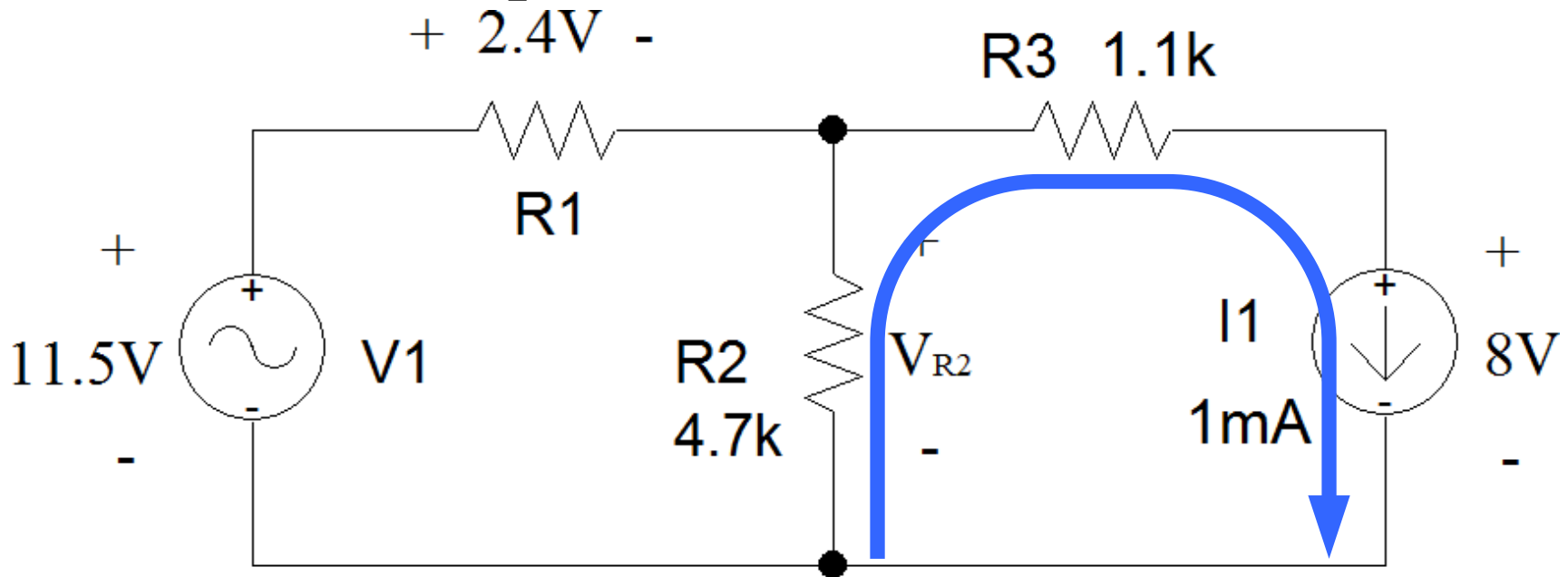


- First, find the voltage drop across R3

$$1 \text{ mA} \times 1.1 \text{ k}\Omega = 1 \times 10^{-3} \text{ A} \times 1.1 \times 10^3 \Omega = 1.1 \text{ V}$$

$$1.1 \text{ V} + 8 \text{ V} - V_{R2} = 0 \quad V_{R2} = 9.1 \text{ V}$$
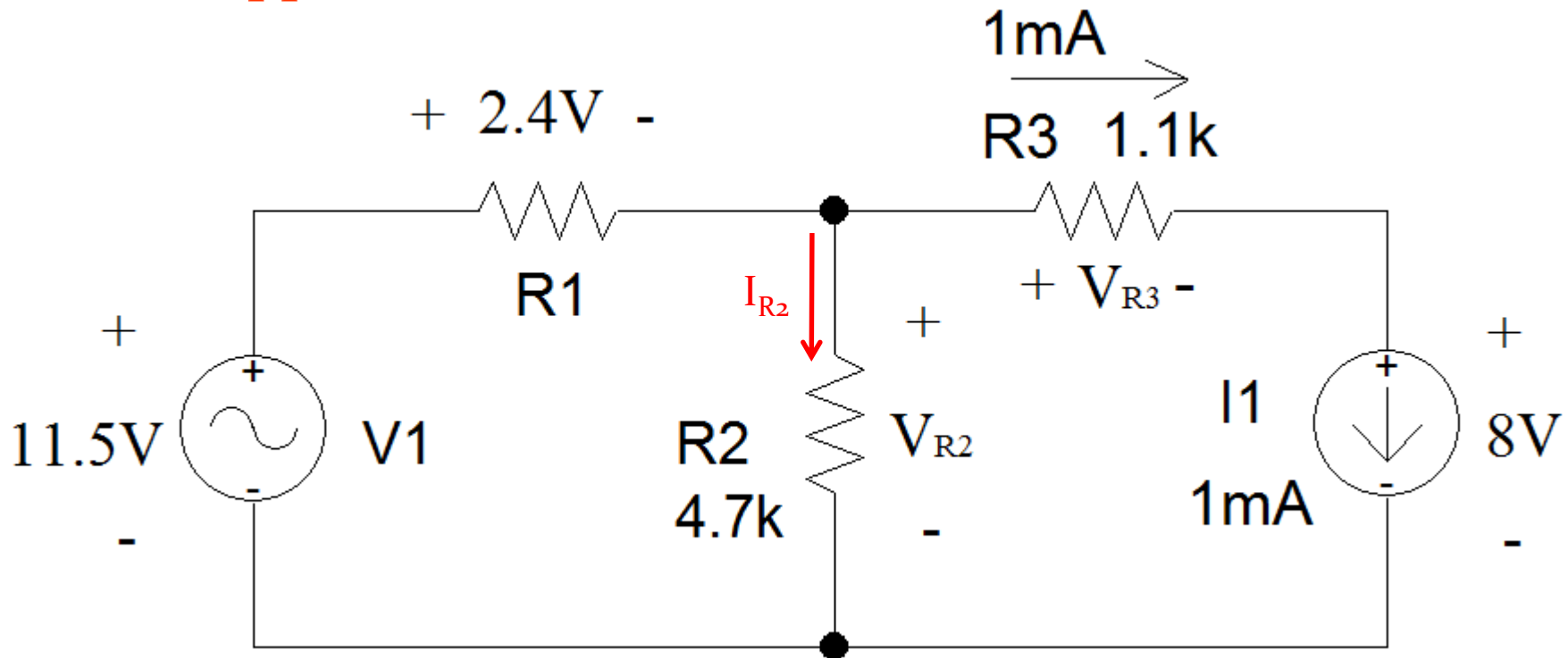
## ...Example-11

- Once the voltage across R2 is known, Ohm's Law is applied to determine the current.



$$I_{R2} = 9.1 \text{ V} / 4.7 \text{ k}\Omega = 9.1 \text{ V} / (4.7 \times 10^3 \Omega)$$

$$I_{R2} = 1.94 \times 10^{-3} \text{ A} = 1.94 \text{ mA}$$