
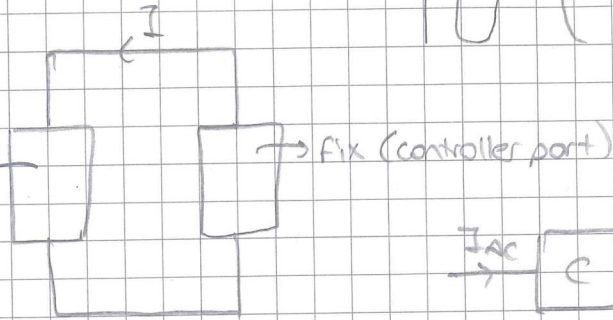


* BME 2301 - CIRCUIT THEORY *

(Dr. Gökrem Serbes / gserbes@yildiz.edu.tr)


Book: Engineering Circuit Analysis / W. Hyat

- 1- Introduction
- 2- Basic concepts
- 3- Voltage & Current Law (Kirchhoff)
- 4- Nodal & Mesh Analysis
- 5- Linearity & Superpositions
- 6- Thevenin & Norton Equivalents
- 7- The Operational Amplifier
- 8- Capacitors & Inductors
- 9- Basic RL and RC circuits
- 10- RLC circuits $\rightarrow$ uses in filter
- 11- AC analysis $\rightarrow$ frequency & period
- 12- The frequency response not fix
- 13- Laplace Transform
- 14- s-Domain Analysis

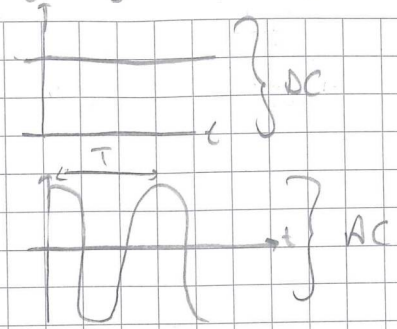

* Abstraction *


Lumped circuit $\rightarrow$ battery

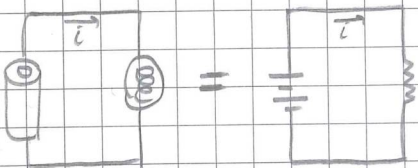

analog abstraction

digital abstraction (not continuous)

$\rightarrow$ Transistors:

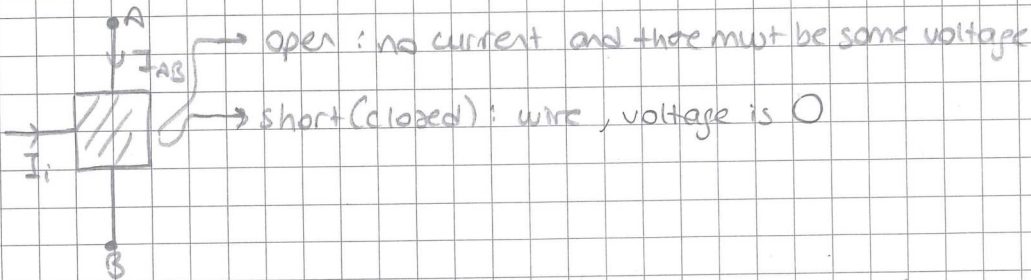

* if we can storage energy, so we have memory. $\rightarrow$ like counters

* if we have digital abstraction, we need to logic and we don't have memory.

$\rightarrow$ Circuit Types:

- ① Bread boards
- ② Printed Circuit boards (PCBs)
- ③ Integrated Circuit (ICS)

NOTE: from heart signals $\rightarrow$ ECG
muscles signals $\rightarrow$ EMG
brain signals $\rightarrow$ EEG
eyes signals $\rightarrow$ EOG


and these signals are continuous signals;
we filtered them and get rid of
the noises. They are analog abstractions.

unwanted parts in some signal


→ Linear vs Nonlinear:

A linear system is predictable and easy to work with


Homogeneity

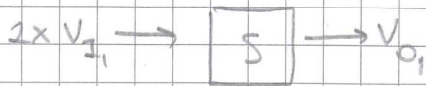

Additivity

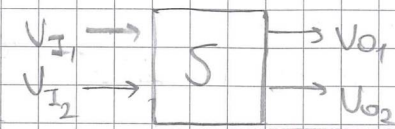
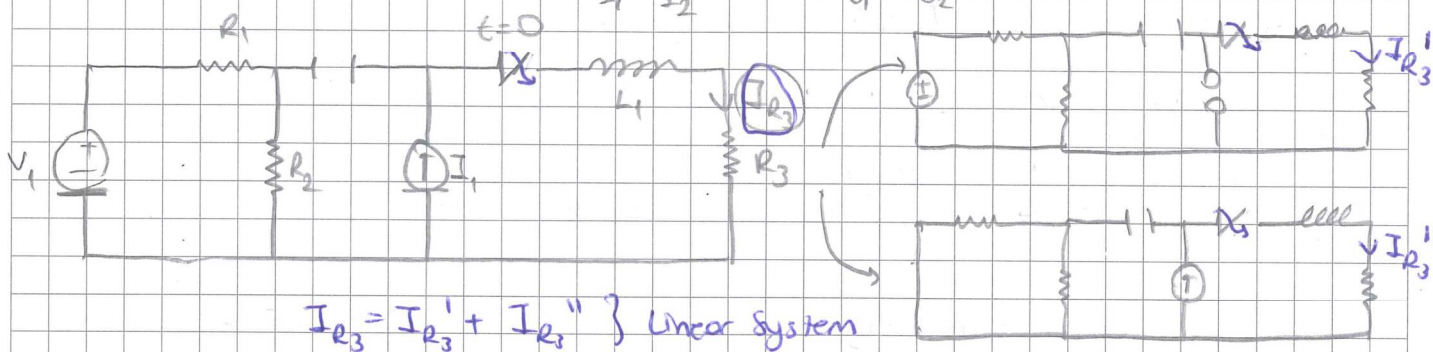
$$V_1 + V_2 \rightarrow V_{01} + V_{02}$$



- * Analysis a system is already given system and solve for a part in it but designing a system, you have a problem and you need to think and design a solution.

→ Electricity: high → low

- * Electricity flows from high voltage to low voltage.
- * Electricity flows in the opposite direction of electron flow.

→ Current is the movement of charge.


$$I = dq/dt$$

$$q(t) = \int_{t=0}^t I(\tau) d\tau + q(t_0)$$

→ Voltage is the energy required to move a unit charge through a element measured in volts (V).

$$V_{ab} = -V_{ba}$$

This element
voltage-current
element

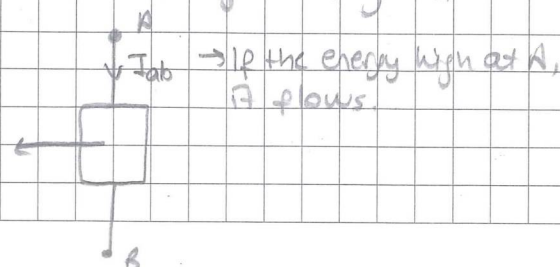

* Define a current → we need to know magnitude and direction.

* Define a voltage → we need to know magnitude and polarity.

Ex: @ $t = 1\text{ms}$ → positive movement

$$i(t) = \frac{dq(t)}{dt} = \frac{\Delta q}{\Delta t} = \frac{80\text{mC} - 0}{2\text{ms} - 0} = \frac{80\text{mC}}{2 \times 10^{-3}} = \underline{\underline{40\text{A}}}$$

@ $t = 6\text{ms}$

there is no change, $A = 0$

@ $t = 10\text{ms}$ → negative movement

$$i(t) = \frac{dq(t)}{dt} = \frac{\Delta q}{\Delta t} = \frac{0 - 80\text{mC}}{12\text{ms} - 8\text{ms}} = \frac{-80\text{mC}}{4\text{ms}} = \underline{\underline{-20\text{A}}}$$



→ Power is the rate of energy change in the circuit. $\Rightarrow P = V \cdot i$

* Passive Sign Convention:

① Positive: If the current enters from (+) side then the power absorbs energy.


$$P = (+)(V)(i)$$

② Negative: If the current enters from (-) side then the power supplies energy.

$$P = (-)(V)(i)$$

* Tellegen's Theorem → $\sum P = 0$ → because of energy conservation.

Ex:

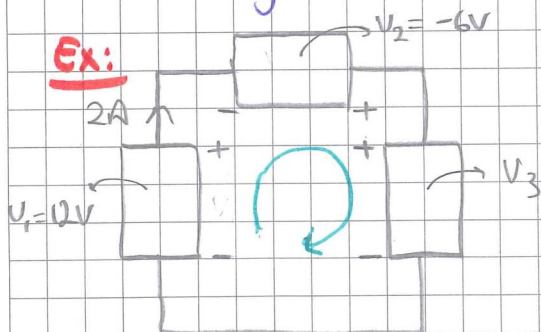

$$V_3 = ?$$

$$P_1 = (-)(12\text{V})(2\text{A}) = -24\text{W}$$

$$P_2 = (-)(-6\text{V})(2\text{A}) = 12\text{W}$$

$$P_3 = (+)(V_3)(2\text{A}) = 2V_3$$

by Tellegen's
 $\sum P = 0$

$$-24 + 12 + 2V_3 = 0$$

$$2V_3 = 12 \Rightarrow \underline{\underline{V_3 = 6\text{V}}}$$

Note:

derivate
 $P(t) \Rightarrow W(t)$
integrate

→ Circuit Components :

① Active elements → independent power sources

$\begin{array}{|c|} \hline \text{---} \\ \hline \text{---} \\ \hline \text{---} \\ \hline \end{array}, \oplus \rightarrow \text{voltage}$ $\textcircled{\uparrow} \rightarrow \text{current}$

→ dependent power sources

$\textcircled{\oplus} \rightarrow \text{voltage}$ $\textcircled{\uparrow} \rightarrow \text{current}$

② Passive elements → resistors (---)

→ capacitors ($\text{---} \text{---} \text{---}$)

→ inductors ($\text{---} \text{---} \text{---}$)


③ Measurement devices → ampermeters → voltmeters

④ Ground (reference point) ($\text{---} \text{---} \text{---}$)

⑤ electric wire (---)

⑥ switches ($\text{---} \text{---}$)

⑦ protective devices → fuse

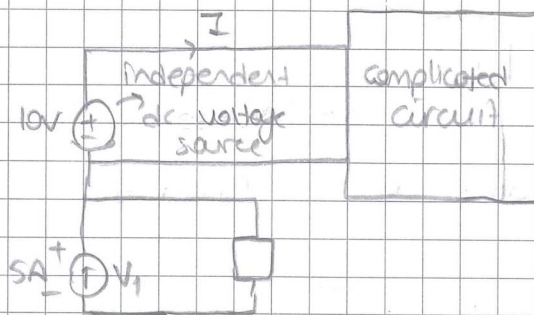


* Types of dependent power sources *

voltage controlled

- voltage source (VCVS)
- current source (VCCS)


current controlled

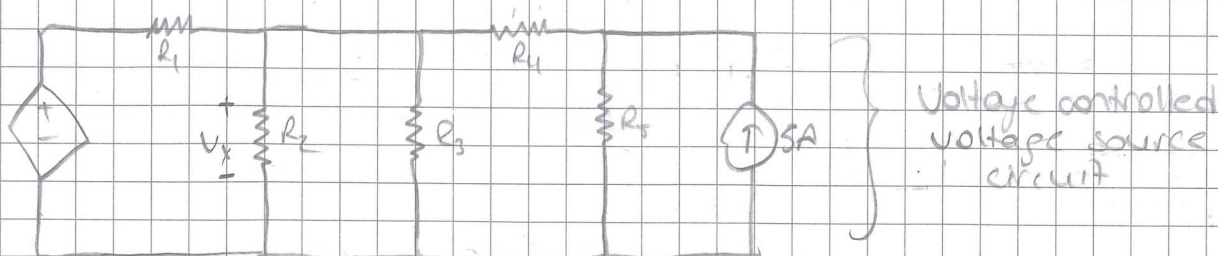- voltage source (CCVS)
- current source (CCCS)



* in control circuits we must use switches.

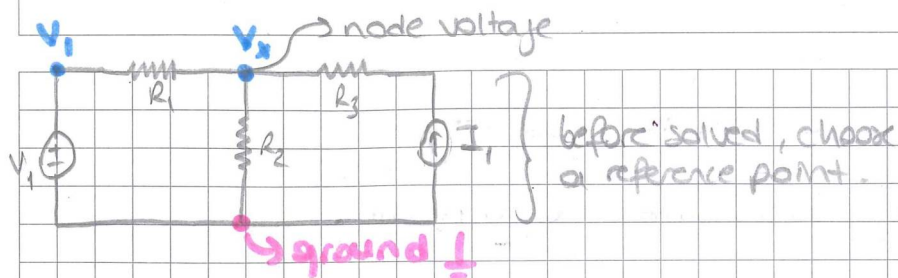in AC { $\rightarrow$ time differences between in two wave $\rightarrow$ phase difference (ϕ)



! The volt value at the two ends of the non current resistor is the same. !

* if we have two resistors (one of them is too big than the other) which are connect to each other parallels, their equivalent resistance value approximates to small one.

* Don't forget to choose reference point in the circuits. (in real life)


$\rightarrow$ Resistivity depends on mobility and points/width (ρ)

$$R = \rho \frac{L}{A} \quad V = I \cdot R$$

$\rightarrow$ Conductance (G) inverse of the resistivity. (conductivity (σ))


$$G = R^{-1} = \frac{I}{V} \quad G = \frac{A\sigma}{L}$$

* Short Circuit *

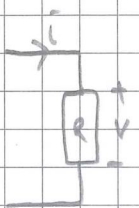


if the resistor is a perfect conductor then,
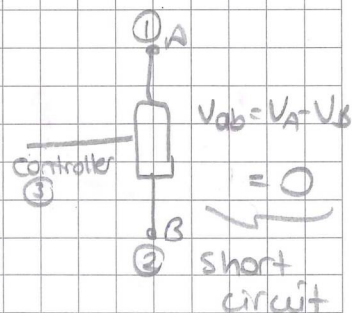
$$R = 0 \Omega \rightarrow V = 0 \text{ volts}$$



* Open Circuit *

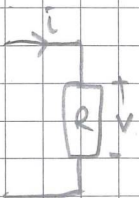


if the resistor is a perfect insulator then,

$$R = \infty \Omega \rightarrow i = \lim_{R \rightarrow \infty} \frac{V}{R} = 0 \quad \text{we may have voltage}$$

* there is no power dissipated in open & short circuits.

Ex:

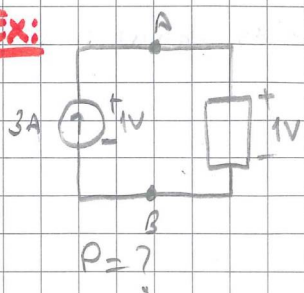

$$V_{AB} = 1V$$

$$P = (-)(1V)(3A)$$


$$V_{GS} = V_{AB} = 1V$$

across the current source

$$= -3 \text{ watts supplied power}$$

by the KVL

Ex:

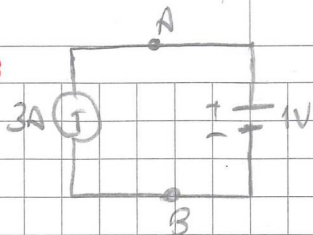


$$P_{CS} = (-)(3A)(1V) = -3 \text{ watt} \rightarrow \text{supplied power}$$

$$P_{VS} = (+)(3A)(1V) = 3 \text{ watt} \rightarrow \text{absorbed power}$$

→ in this source battery charged by current source.

Ex:

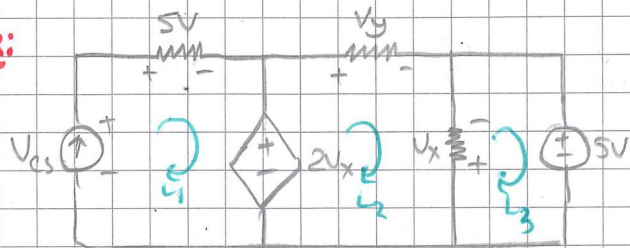

$$V_{cs}, V_x, V_y = ?$$

By the KVL / Tellegen's Theorem


$$\text{for } L_3 \Rightarrow +V_x + 5V = 0$$

$$V_x = -5V$$

$$\text{for } L_2 \Rightarrow -2V_x + V_y - V_x = 0$$


$$V_y = -15V$$

$$V_{cs} = -5V$$

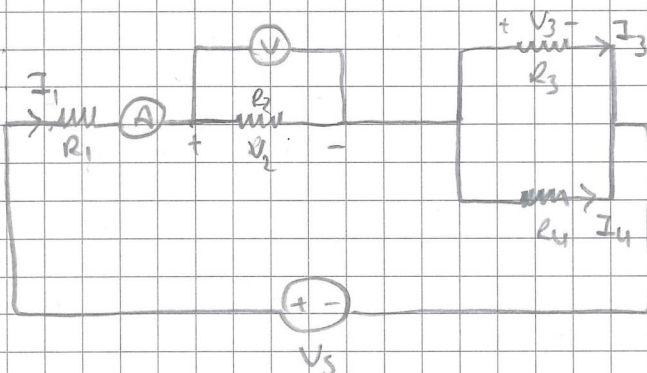

$$\text{ampermeter} \rightarrow R_m = 0$$
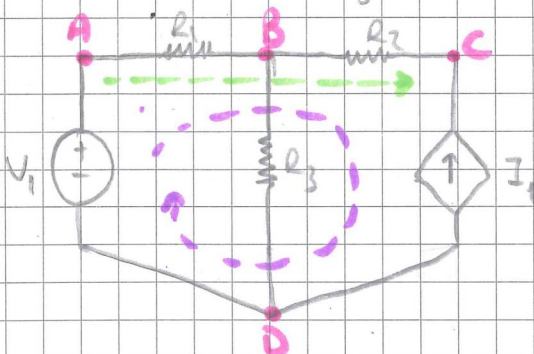
$$\text{voltmeter} \rightarrow R_m = \infty$$





A, B, C, D → nodes

ABC → path

ABCD → loop

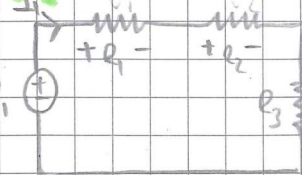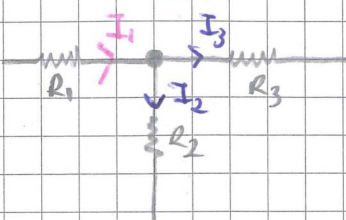*** Kirchhoff's Current Law (KCL) *** *** Kirchhoff's Voltage Law (KVL) ***



$$-V_1 = V_{R1} + V_{R2} + V_{R3}$$

$$V_1 + V_{R1} + V_{R2} + V_{R3} = 0$$


$$\sum_{\text{node}} i_{\text{enter}} = \sum_{\text{node}} i_{\text{leave}}$$

$$\Rightarrow \sum_{n=1}^N i_n = 0$$

$$\sum V_{\text{drops}} = \sum V_{\text{rises}}$$

$$\Rightarrow \sum_{m=1}^N V_m = 0$$


Ex:

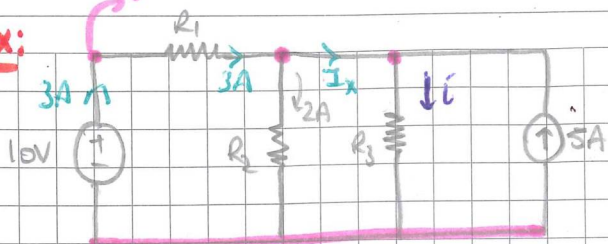

Voltage source supplies a current of 3A
so, $i = ?$

By the KCL $\Rightarrow 3A = I_x + 2A$, $I_x + 5A = i$
 $I_x = 1A$, $i = 6A$

Ex:

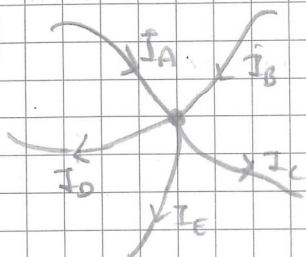


$I_A = 1A$, $I_C = 3A$, $I_D = 2A$, $I_E = 4A \rightarrow I_B = ?$

$I_A + I_B = I_D + I_E + I_C$

$I_B = I_D + I_E + I_C - I_A \Rightarrow I_B = 4A$

Ex:

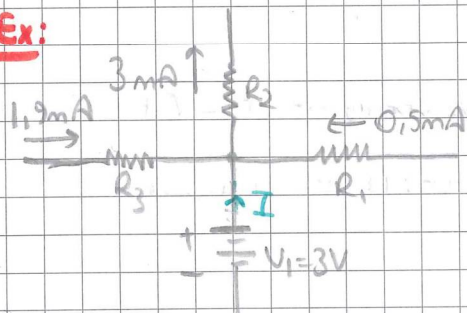


$I = ?$, $P_2 = ?$

$I + 1.9mA + 0.5mA = 3mA$ $\Leftarrow$ KCL

$I = 0.6mA$

$P_2 = (-)(0.6mA)(3V) = -1.8mW$ supplying

Ex:

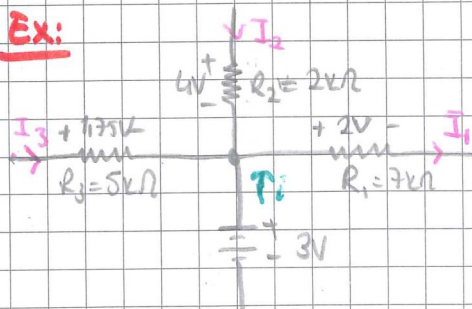


$i = ?$

$I_3 + I_2 - I_1 + i = 0$

$-\left(\frac{1.75V}{5k} + \frac{4V}{2k} - \frac{2V}{7k}\right) = i$

$i = -2.0643mA$

Ex:

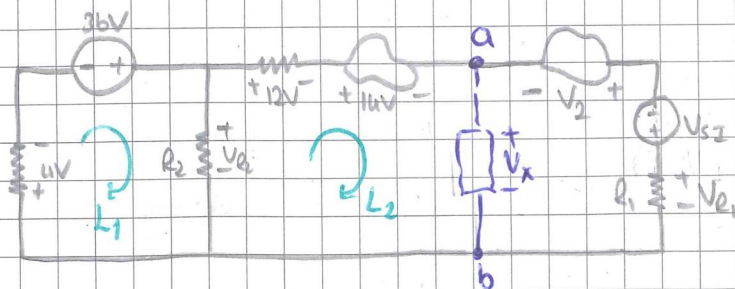


$V_{R2} = ?$, $V_{ab} = ?$

KVL $\Rightarrow 4V - 36V + V_2 = 0$
 L_1

$V_{R2} = 32V$

$-32V + 12V + 14V + V_x = 0$ $\Leftarrow$ KVL
 L_2

$V_x = 6V$

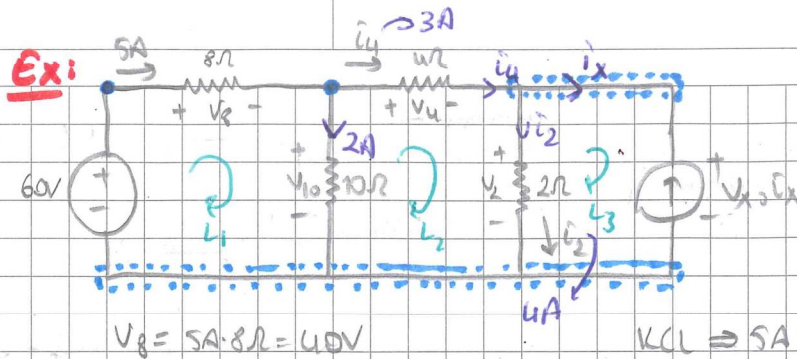

$$V_8 = 5A \cdot 8\Omega = 40V$$

$$KVL \rightarrow L_1 \Rightarrow -60 + 40 + V_{10} = 0$$

$$V_{10} = 20V$$

$$V_{10} = i_{10} \cdot 10\Omega \Rightarrow i_{10} = 2A$$

$$KCL \Rightarrow 5A = i_4 + i_{10}$$

$$i_4 = 3A$$

$$V_4 = 3A \cdot 4\Omega = 12V$$

$$KVL \rightarrow L_2 \Rightarrow -8V + V_x = 0$$

$$\boxed{V_x = 8V}$$


$$KVL \rightarrow L_2 \Rightarrow -V_{10} + V_4 + V_2 = 0$$

$$-20 + 12 + V_2 = 0$$

$$V_2 = 8V$$

$$KCL \Rightarrow i_4 - i_2 + i_x = 0$$

$$i_x = 1A$$

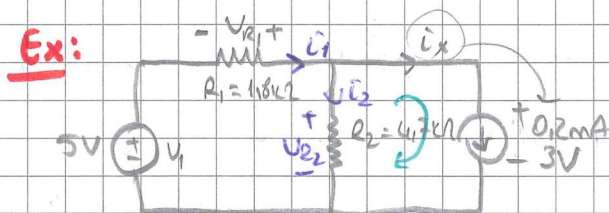

$$L_1 \Rightarrow -V_2 + 3V = 0$$

$$V_2 = 3V \Rightarrow i_2 = \frac{3V}{4.7k\Omega} = 0.638mA$$


$$i_1 = i_x + i_2$$

$$i_1 = 0.2mA + 0.638mA = 0.838mA$$

$$V_{R1} = (-)(0.838mA)(1.8k\Omega)$$

$$\boxed{V_{R1} = -1.5V}$$


comes from current entered (-) side

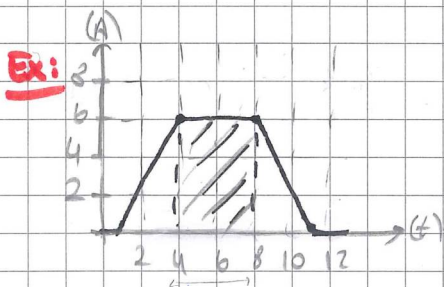

What is the net charge that passes through the element between $t=4$ and $t=8$?

$$Q = \int i(t) dt \rightarrow \text{we should look the area}$$
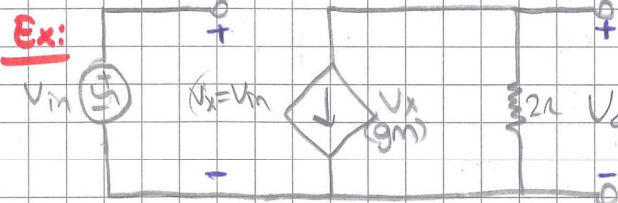
$$= \int_4^8 i(t) dt = 4s \cdot 6A = \underline{\underline{24C}}$$



$$V_{in} = 3 \sin(\omega t) mV$$

$$g_m = 10 A/V$$


$$V_{out} = ?$$

$$V_{out} = (-)(2\Omega)(g_m)(V_x) = (-)(2\Omega)(10A/V)(3 \sin(\omega t) mV)$$

enters from negative side

$$\underline{\underline{V_{out} = -60 \sin(\omega t) mV}}$$


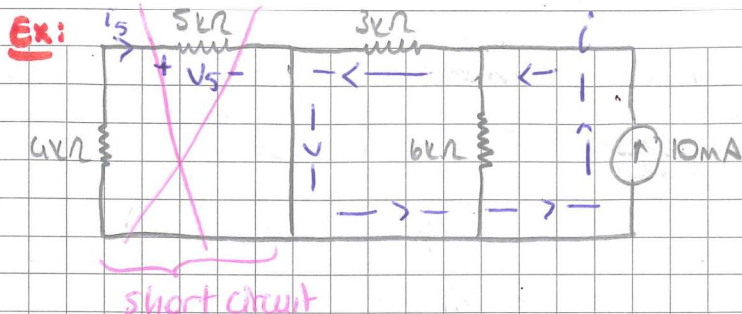
* open circuit here, between $t - R_x = \infty$



Determine the power absorbed by the 5kΩ resistor.

$$P_{5k\Omega} = (-5)(V_5)(I_5) = \underline{0 \text{ watts}}$$

because the short circuit

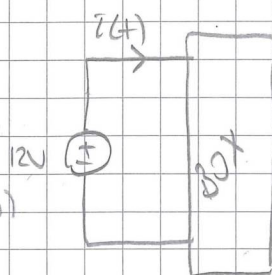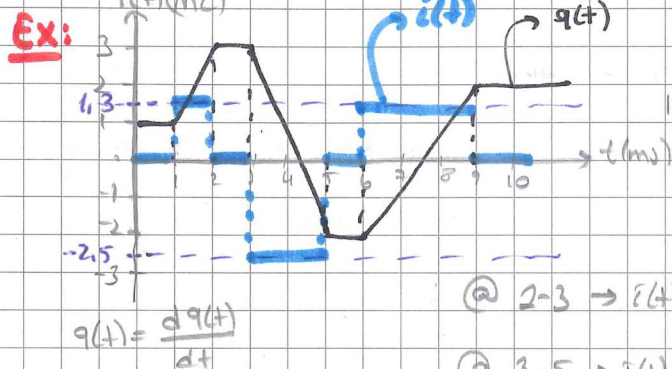

The charge that enters the Box is shown. Calculate and sketch the current flowing by the box between 0-10ms.

$$i(t) = \frac{dq(t)}{dt}$$

@ 0-1 $\rightarrow i(t) = 0$

@ 1-2 $\rightarrow i(t) = \frac{\Delta q}{\Delta t} = 2A$

@ 2-3 $\rightarrow i(t) = 0$


@ 3-5 $\rightarrow i(t) = \frac{(-2.5)-0}{2} = -2.5A$

@ 5-6 $\rightarrow i(t) = 0$

@ 6-9 $\rightarrow i(t) = \frac{2-0}{3} = 1.33A$

@ 9-10 $\rightarrow i(t) = 0$

* — is the sketch of solution

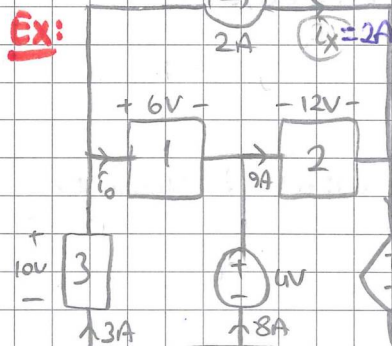

find the i_0 by the Tellegen's Theorem.

$$P_1 = (6V)(i_0) = 6i_0W$$

$$P_2 = (-)(12V)(9A) = -108W$$

$$P_3 = (-)(10V)(3A) = -30W$$


$$P_{4V} = (-)(4V)(8A) = -32W$$

$$P_{2A} = (-)(6V)(2A) = -12W$$

$$P_{dep} = (+)(16V)(11A) = 176W$$

The total sum must be zero by Tellegen's theorem,
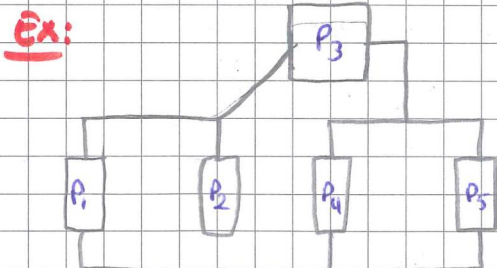
$$6i_0 = 6 \Rightarrow \underline{i_0 = 1A}$$



$$P_1 = 50W$$

$$P_2 = 40W$$

$$P_3 = -10W$$

$$P_4 = 5W$$


$$P_5 = ?$$

+ Tellegen's #

$$50W + 40W - 10W + 5W + P_5 = 0$$

$$\underline{P_5 = 15W}$$

Ex:

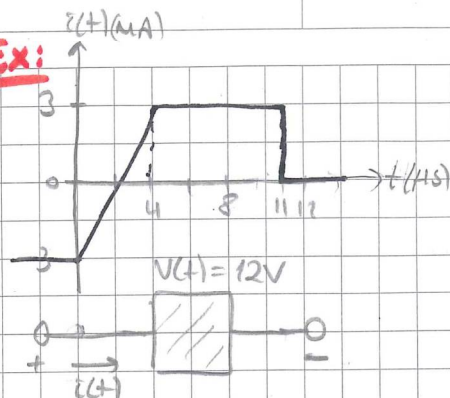

under the area

a) Compute the net charge between $t = 2\mu\text{s}$ and $t = 11\mu\text{s}$

$$i(t) = \frac{dq(t)}{dt}$$

$$q = \int_2^{11} i(t) dt = \frac{(2\mu\text{s})(3\text{mA})}{2} + (7\mu\text{s})(3\text{mA})$$

$$= \underline{\underline{24\text{ nC}}}$$

b) When does the element absorbed & supplied electrical energy?


$$P(t) = i(t) \cdot V(t) \rightarrow t @ 0 - 2\mu\text{s} \Rightarrow P = (-) \rightarrow \text{supplied}$$

$$@ 2 - 11\mu\text{s} \Rightarrow P = (+) \rightarrow \text{absorbed}$$

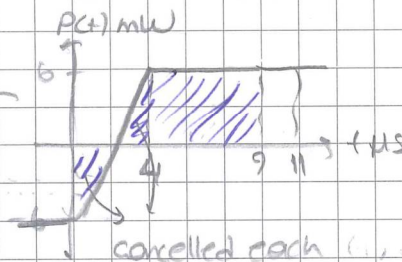
c) Compute the net energy absorbed by the element between $t = 0\mu\text{s}$ and $t = 9\mu\text{s}$

$$W = \int P(t) dt = \int_0^9 P(t) dt$$

$$= (5\mu\text{s})(6\text{mW}) = \underline{\underline{30\mu\text{Joule}}}$$



Ex:

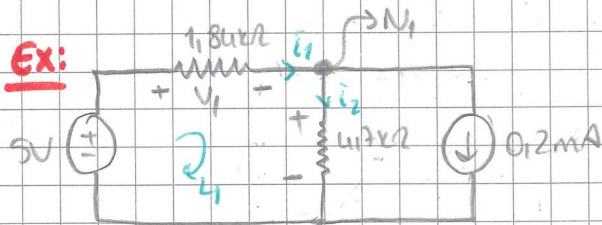

$$V_1 = ?$$

$$\text{KVL @ } L_1 \Rightarrow -5\text{V} + (1.8\text{k}) (i_1) + (4.7\text{k}) (i_2) = 0$$

$$\text{KCL @ } N_1 \Rightarrow i_1 - i_2 - 0.2\text{mA} = 0$$

$$1800i_1 + 4700i_2 = 5\text{V}$$

$$i_1 - i_2 = 0.2\text{mA}$$

$$\begin{bmatrix} 1800 & 4700 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 0.2 \times 10^{-3} \end{bmatrix}$$

a b c

We solved these matrices on matlab

$$(\vec{a}^T * \vec{a}) + \vec{b} = \vec{a}^T * \vec{c}$$


$$\vec{b} = \vec{a}^T * \vec{c}$$

$$i_1 = 0.918\text{mA}$$


$$i_2 = 0.718\text{mA}$$

$$V_1 = (+)(0.918\text{mA})(1.8\text{k}\Omega)$$
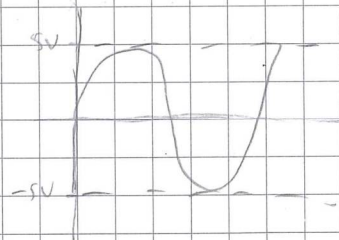
$$\underline{\underline{V_1 = +1.65\text{V}}}$$



* The Single-Loop Circuit *

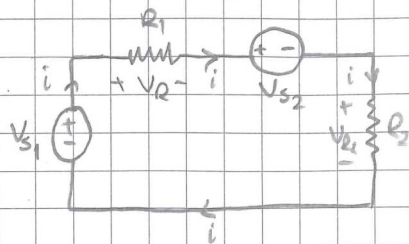

$$-V_{s1} + V_{R1} + V_{s2} + V_{R2} = 0$$


$$V_{R1} = R_1 i \text{ and } V_{R2} = R_2 i$$

$$-V_{s1} + R_1 i + V_{s2} + R_2 i = 0$$

$$i = \frac{V_{s1} - V_{s2}}{R_1 + R_2}$$

- ① Analysis is the assumption of reference directions for unknown currents.
- ② Analysis is a choice of the voltage reference for each of the resistors.
- ③ Application of KVL to the only closed path.

Ex:

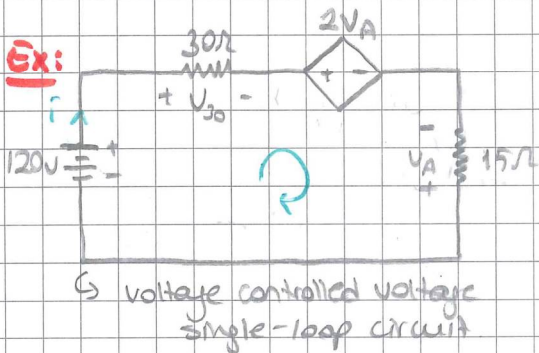

Compute the power absorbed in each element of the circuit.

$$1 - \text{KVL} \Rightarrow -120V + V_{30} + 2V_A - V_A = 0$$

$$V_{30} + V_A = 120V$$


$$2 - V_{30} = (i) \cdot 30\Omega \quad \left. \begin{array}{l} 30i - 15i = 120V \\ V_A = -(i) \cdot 15\Omega \end{array} \right\} \quad \underline{i = 8A}$$

$$V_A = -(i) \cdot 15\Omega$$

$$\begin{aligned} 3 - P_{120V} &= (-)(8)(120) = -960W \\ P_{30\Omega} &= i^2 R = (64)(30) = 1920W \\ P_{2V_A} &= (+)(8)(-24) = -1920W \\ P_{15\Omega} &= i^2 R = (64)(15) = 960W \end{aligned}$$

$$\underline{P_T = 0W}$$

Ex:

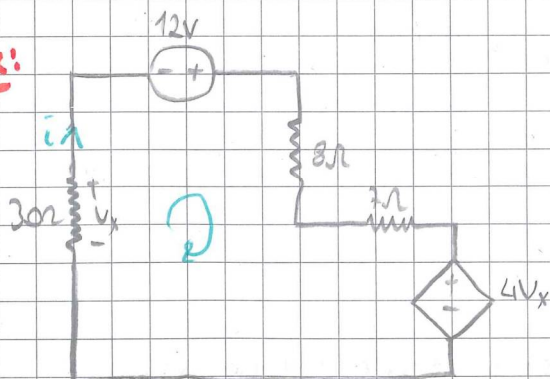

$$P_T = ?$$

$$-V_x = 12V + (8+2)i + 4V_x = 0$$

$$-V_x = \frac{15V_x}{20} + 4V_x = 12$$

$$V_x = \frac{24}{5} \text{ Volts}$$

$$\hookrightarrow i = -\frac{4}{25} A$$

$$V_x = (-)(20\Omega) \cdot i$$

$$i = -V_x / 20$$

$$P_{30\Omega} = 760mW$$

$$P_{12V} = 1.92W$$


$$P_{8\Omega} = 204.8mW$$

$$P_{2\Omega} = 179.2mW$$

$$P_{4V_x} = -3.072W$$

$$\underline{P_T = 0W}$$

* The Single-Node-Pair Circuit *

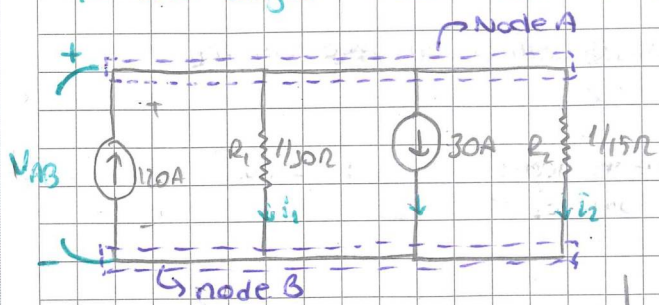

Find the voltage, current and power associated with each element.

$$\text{KCL @ node A} \rightarrow 120 - i_1 - i_2 - 30 = 0$$

$$i_1 + i_2 = 90\text{A}$$

$$30V_{AB} + 15V_{AB} = 90$$

$$i_1 = \frac{V_{AB}}{1/30} = 60\text{A}$$

$$V_{AB} = 2\text{V}$$

$$i_2 = \frac{V_{AB}}{1/15} = 30\text{A}$$

Current sources live $120 - 30 = 90\text{A}$

$$P_{120A} = (-)(2)(120\text{A}) = -240\text{W}$$


$$P_{30A} = (+)(2\text{V})(30\text{A}) = 60\text{W}$$

$$P_{R1} = 60^2 \cdot 1/30 = 120\text{W}$$

$$P_{R2} = 30^2 \cdot 1/15 = 60\text{W}$$


$$P_T = 0\text{W}$$

* Series Circuits *

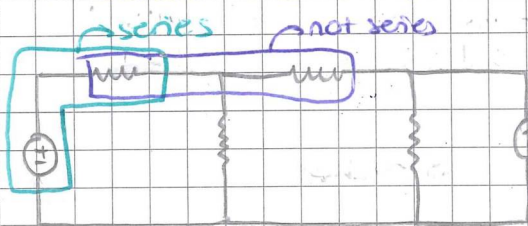


→ all elements in a circuit (loop) that carry the same current.

* Parallel Circuits *

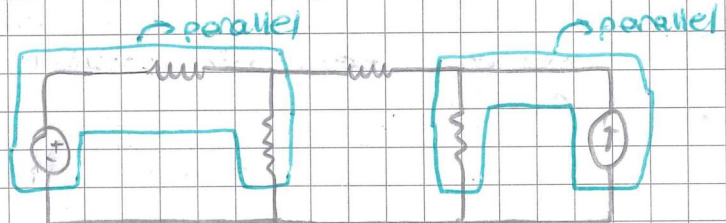

→ all elements in a circuit (loop) that have a common voltage across them.

Ex:

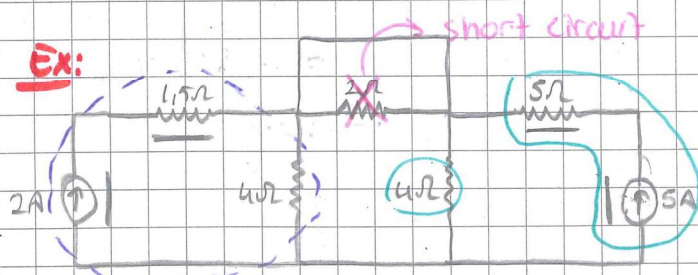


write the parallels & series elements.

2A & 1.5 ohm } individual series
5A & 5 ohm }

5A & 5 ohm parallel with 4 ohm
2A & 1.5 ohm parallel with 4 ohm

groups.


NOTE: ①

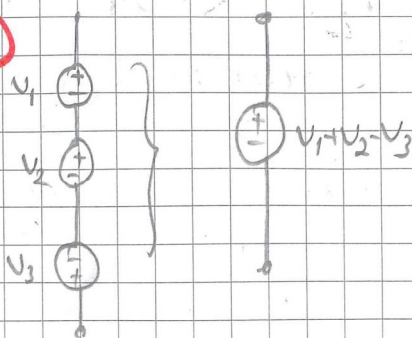

→ We can replace voltage source in series with a single equivalent source.

$$\sum V_n = V_{\text{equivalent}}$$

②

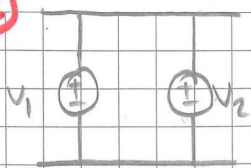


→ unless $V_1 = V_2 = \dots$ this circuit is not valid for real sources

→ All real voltage source have internal resistance and are usually not exactly equal.

→ Current will flow from the higher source to the lower source until equilibrium is reached.

③

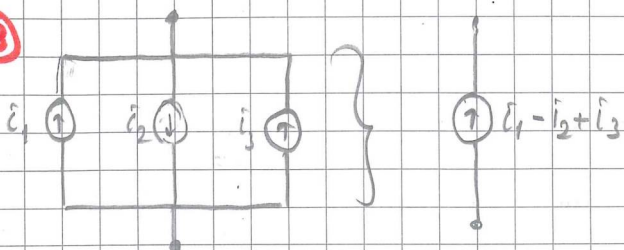

→ we can replace current sources in parallel with a single equivalent source.

$$\sum i_n = i_{\text{equivalent}}$$

④

→ in series resistance are added $\sum R_n = R_1 + R_2 + \dots + R_n = R_{\text{equivalent}}$

→ in parallel resistance $\sum 1/R_n = 1/R_1 + 1/R_2 + \dots + 1/R_n = 1/R_{\text{equivalent}}$


→ $R_1 || R_2 || R_3$ parallel symbol

⑤

→ if G is used instead of R ; in series → the reciprocal of the equivalent conductance is equal to the sum of the reciprocal of each of the conductors in series.

$$1/G_{\text{eq}} = 1/G_1 + 1/G_2 \rightarrow \text{inverse } R \quad G \rightarrow \text{mho}$$

Ex:

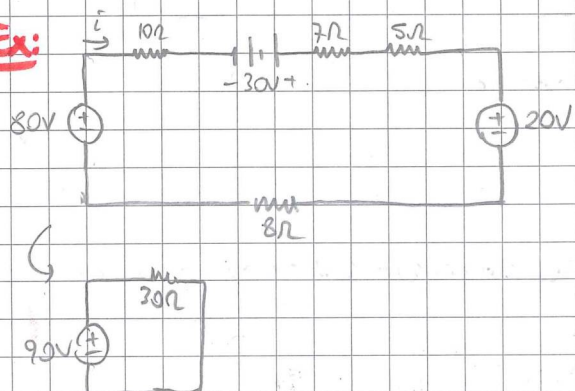


$$i = ? , P_{80V} = ?$$

$$80V \uparrow \quad -30V \downarrow \quad 20V \uparrow \quad \} \quad 90V = V_{\text{Total}}$$

$$R_{\text{eq}} = 10 + 7 + 5 + 8 = 30\Omega \rightarrow i = \frac{90V}{30} = 3A$$

$$P_{80V} = -(80)(3A) = -240W \text{ delivered}$$

Ex:

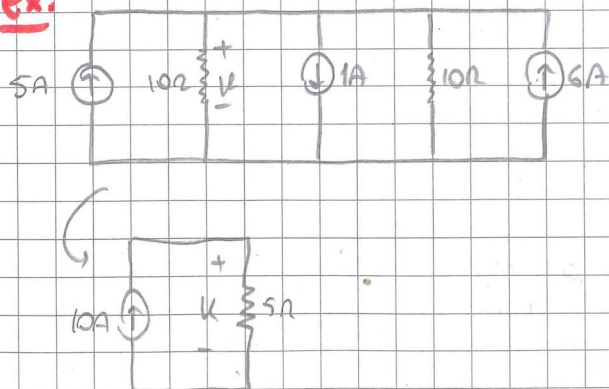

Determine V in this circuit by first combining the three current sources, then the two 10 ohm resistors.

$$\frac{1}{R_{\text{eq}}} = \frac{1}{10} + \frac{1}{10} \Rightarrow R_{\text{eq}} = 5\Omega$$


$$I_{\text{Total}} = 5 - 1 + 6 = 10A$$

$$V_T = (10A)(5\Omega) = 50V$$

* As you increase the number of resistors in series; R_{eq} increase.

* As you increase the number of resistors in parallel; R_{eq} decrease.

Ex:

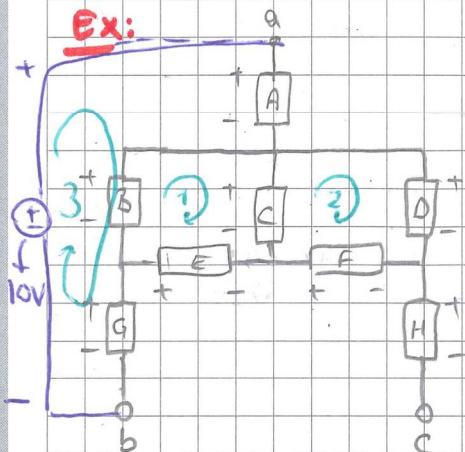

For the diagram above the following voltages are specified;

$$V_A = -2V, V_D = 2V, V_E = 3V, V_G = 4V, V_H = 2V, V_{ab} = 10V$$

Find the value of V_c in volts.


$$\text{KVL @ loop 1} \rightarrow -V_B + V_c - V_E = 0 \rightarrow V_c = V_B + V_E$$

$$\text{@ loop 2} \rightarrow -V_c + V_D - V_F = 0 \rightarrow V_c = V_D - V_F$$

$$\text{@ loop 3} \rightarrow -10V + V_A + V_B + V_G = 0 \rightarrow V_B = 8V$$

$$V_c = V_B + V_E \Rightarrow V_c = 8V + 3V = \underline{11V}$$

Ex:

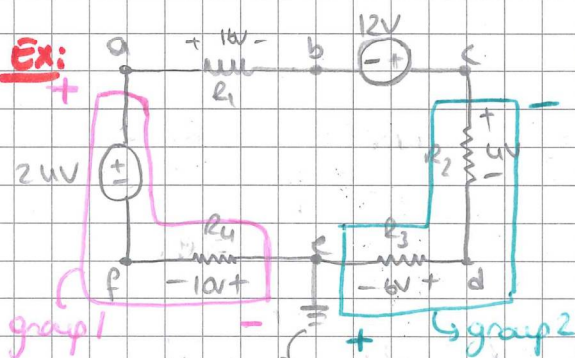

Write loop equation, find V_{ae} & V_{ec} .

1. way

$$1) V_{ae} = V_a - V_e$$

$$V_a = V_f + 2V = 1V$$

$$V_f = -10V$$

$$V_{ae} = V_a - V_e = 1V - 0 \Rightarrow \underline{V_{ae} = 1V}$$

$$2) V_{ec} = V_e - V_c$$

$$V_b = V_a - 16V = -2V$$

$$V_c = V_b + 12V = 10V$$

$$V_{ec} = V_e - V_c = 0 - 10V \Rightarrow \underline{V_{ec} = -10V}$$

2. way

KVL @ group 1

$$-V_{ae} + 16 - 12 + 4 + 6 = 0$$


$$\underline{V_{ae} = 1V}$$

KVL @ group 2

$$-V_{ec} + 10 - 2 + 16 - 12 = 0$$

$$\underline{V_{ec} = -10V}$$

Ex:

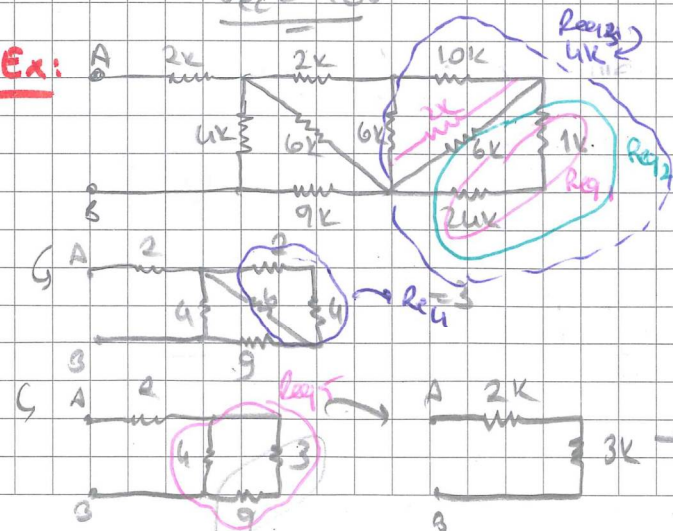


$R_{AB} = ?$

$$R_{eq1} = 1 + 2 = 3k\Omega \quad R_{eq2} = \frac{6 \times 3}{6 + 3} = 2k\Omega$$

$$R_{eq3} = \frac{6 \times 12}{12 + 6} = 4k\Omega$$

$$R_{eq4} = \frac{6 \times 6}{12} = 3k\Omega \quad R_{eq5} = \frac{4 \times 12}{12 + 4} = 3k\Omega$$
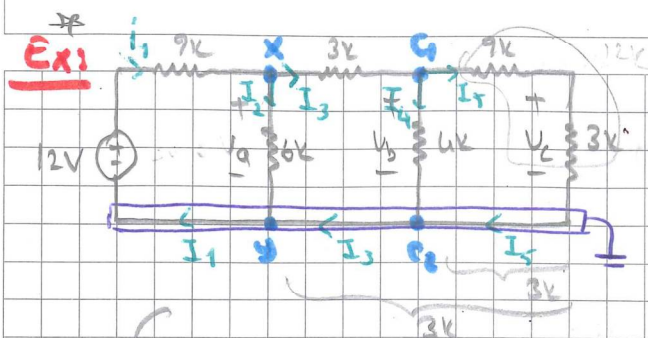
$$3k \rightarrow R_{AB} = 2 + 3 = \underline{5k\Omega}$$




Find the all currents and voltages.

$$9k + 3k = 12k$$

$$R_{eq1} = \frac{1}{\frac{1}{4} + \frac{1}{2}} = 3k$$

$$3k + 3k = 6k$$
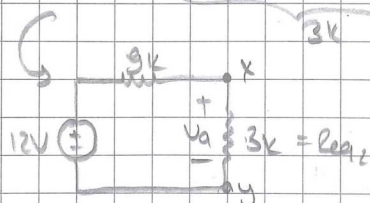
$$R_{eq2} = \frac{1}{\frac{1}{4} + \frac{1}{6}} = 3k$$



$$V_a = (12V) \cdot \frac{3k}{12k} = 3V$$

$$V_b = (3V) \cdot \frac{3k}{6k} = 1.5V$$

$$V_c = (1.5V) \cdot \frac{3k}{12k} = 0.375V$$

We use voltage division

$$I_1 = \frac{12-3}{9} = 1mA$$


$$I_2 = \frac{3-0}{6} = 0.5mA$$

$$I_3 = \frac{3-1.5}{3} = 0.5mA$$

$$I_4 = \frac{1.5-0}{4} = 0.375mA$$

$$I_5 = \frac{0.375-0}{3} = 0.125mA$$

* VOLTAGE DIVISION *

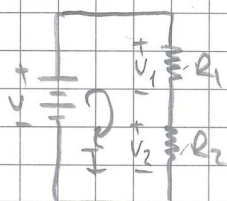

* All resistors in series and share same current.

By KVL & Ohm's law

$$0 = -V + V_1 + V_2 \rightarrow V = V_1 + V_2$$

$$V = IR_1 + IR_2 = I R_{eq}$$

$$V_1 = \frac{R_1}{R_1 + R_2} \cdot V$$

$$V_2 = \frac{R_2}{R_1 + R_2} \cdot V$$

* The source voltage V is divided among the resistors in direct proportion to their resistance.

* $\rightarrow$ the larger resistance has larger voltage drop.

* This called the principle of voltage division and the circuit is called a voltage divider circuit.

$$\nabla \text{ RULE } \Rightarrow V_n = \frac{R_n}{R_1 + R_2 + \dots + R_n} \cdot V_{\text{Total}} \Rightarrow$$


$$V_n = \left[\frac{R_n}{R_{eq}} \right] \cdot V_{\text{Total}}$$

Note: in real life red probe $\rightarrow +$ in circuits.
black probe $\rightarrow -$

AC voltage }
$$V = A \sin(2\pi f t + \phi)$$

$\downarrow$ magnitude $\nearrow$ frequency
 $\searrow$ phase

Ex:

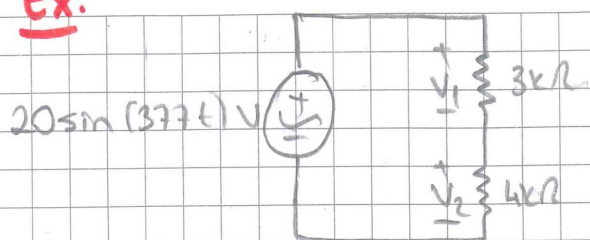


V_1 and $V_2 = ?$

$$V_1 = \frac{R_1}{R_1 + R_2} \cdot V_T = 8.57 \sin(377t) \text{ V}$$

$$V_2 = \frac{R_2}{R_1 + R_2} \cdot V_T = 11.4 \sin(377t) \text{ V}$$


Note:

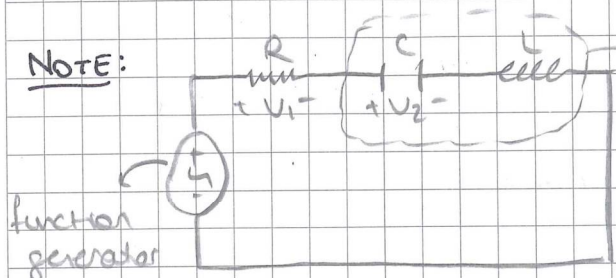

→ we will see the phase differences.

→ and these two elements energy storage in the circuit.

Ex:

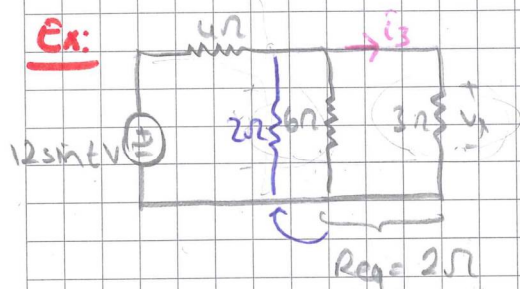


$V_x = ?$, $I_3 = ?$

$$V_x = \frac{2}{(4+2)} (12 \sin t) = 4 \sin t \text{ V}$$

$$I_3 = \frac{4 \sin t \text{ V}}{3} = 1.33 \sin t \text{ A}$$

* CURRENT DIVISION *

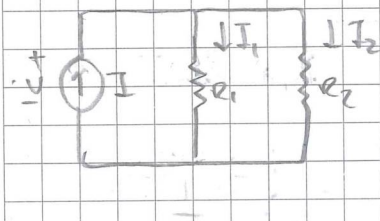

† All resistors in parallel and share the same voltage.

By KCL & Ohm's law

$$0 = -I + I_1 + I_2 \rightarrow I = I_1 + I_2$$

$$I_1 = \frac{R_2}{R_1 + R_2} \cdot I$$

$$I = \frac{V}{R_1} + \frac{V}{R_2}$$

$$I_2 = \frac{R_1}{R_1 + R_2} \cdot I$$


* The total current I is shared by resistors in inverse proportion to their resistors.

* → The smaller resistor has the larger current flow.

† This is called the principle of current division and the circuit is called current divider circuit.

! RULE $\Rightarrow I_n = \frac{1/R_n}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}} \cdot I_{\text{total}} \Rightarrow$
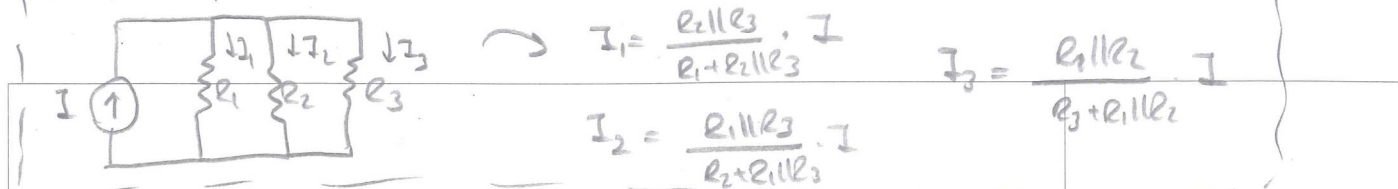
$$I_n = \left[\frac{R_{eq}}{R_n} \right] I_{\text{total}}$$




* If we can use conductance (G)

$$I_n = \frac{G_n}{G_1 + G_2 + \dots + G_n} \cdot I \Rightarrow \left[\frac{G_n}{G_{eq}} \right] \cdot I_{Total} = I_n$$

* the larger conductance value resistor has the larger current.

Ex:

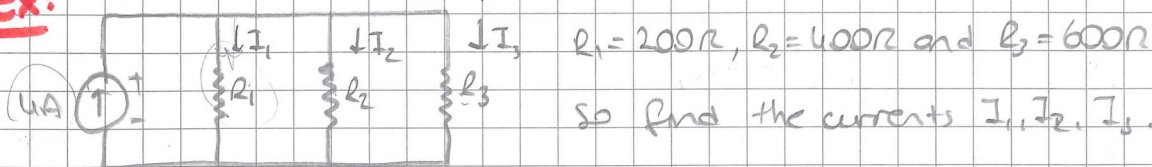


$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = 109\Omega$$

$$I_1 = \frac{109}{200} \cdot 4 = 2.18A$$

$$I_2 = \frac{109}{400} \cdot 4 = 1.09A$$


$$I_3 = \frac{109}{600} \cdot 4 = 0.722A$$

Ex:

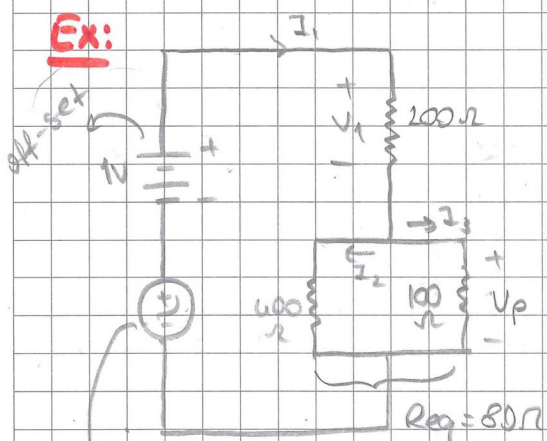

$$V_p, V_1, I_1, I_2, I_3 = ?$$
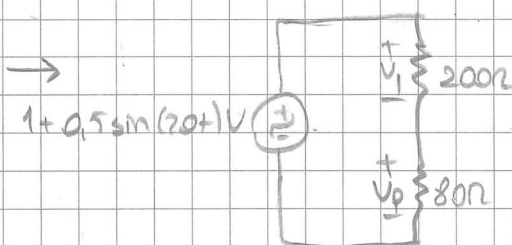
$$V_{tot} = 0.5 \sin(20t) + 1V \rightarrow \text{DC off-set voltage (DC Bias)}$$



$$I_1 = \frac{1 + 0.5 \sin(20t)}{280\Omega}$$

$$I_1 = 3.57 + 1.79 \sin(20t) \text{ mA}$$

DC term AC term

$0.5 \sin(20t) V$
(function generator)

$$V_1 = I_1 \cdot R_1$$

$$V_1 = (3.57 + 1.79 \sin(20t)) (200)$$

or by voltage divider

$$V_1 = 0.714 + 0.357 \sin(20t) V$$

$$V_1 = V_T \cdot \frac{200}{280}$$

$$V_p = \frac{V_T \cdot 80\Omega}{280\Omega} = 0.287 + 0.143 \sin(20t) V$$

$$I_3 = \frac{V_p}{100\Omega} = 2.86 + 1.43 \sin(20t) \text{ mA}$$



$$I_2 = \frac{V_p}{400\Omega} = 0.714 + 0.357 \sin(20t) \text{ mA}$$

or

$$I_2 = \frac{R_3}{R_2 + R_3} \cdot I_1$$

$$I_2 = I_1 - I_3$$

* WYE & DELTA NETWORK * (3 terminals)

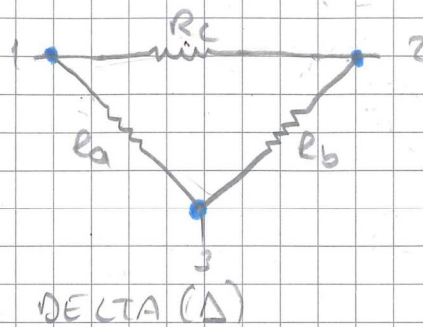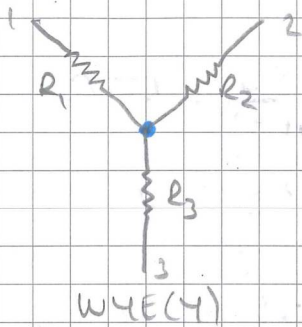

→ to transform $\Delta \rightarrow Y$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

→ to transform $Y \rightarrow \Delta$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$



$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

* if $R_1 = R_2 = R_3 = R \rightarrow R_a = R_b = R_c = 3R$


$R_a = R_b = R_c = R \rightarrow R_1 = R_2 = R_3 = 1/3R$

* T & Π NETWORKS * (4 terminals)

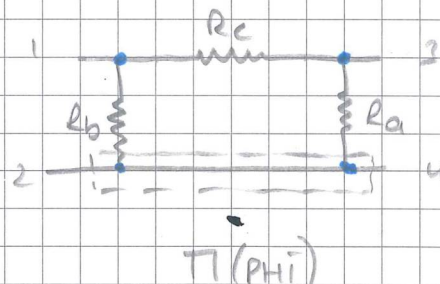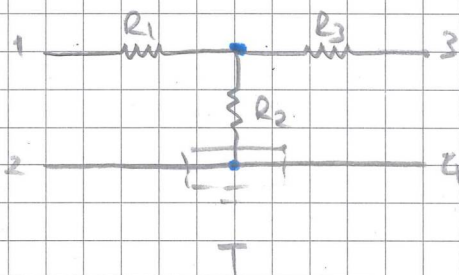


* we should use these transforms in distribution of power in stators and windings in motors/generators.

Ex:

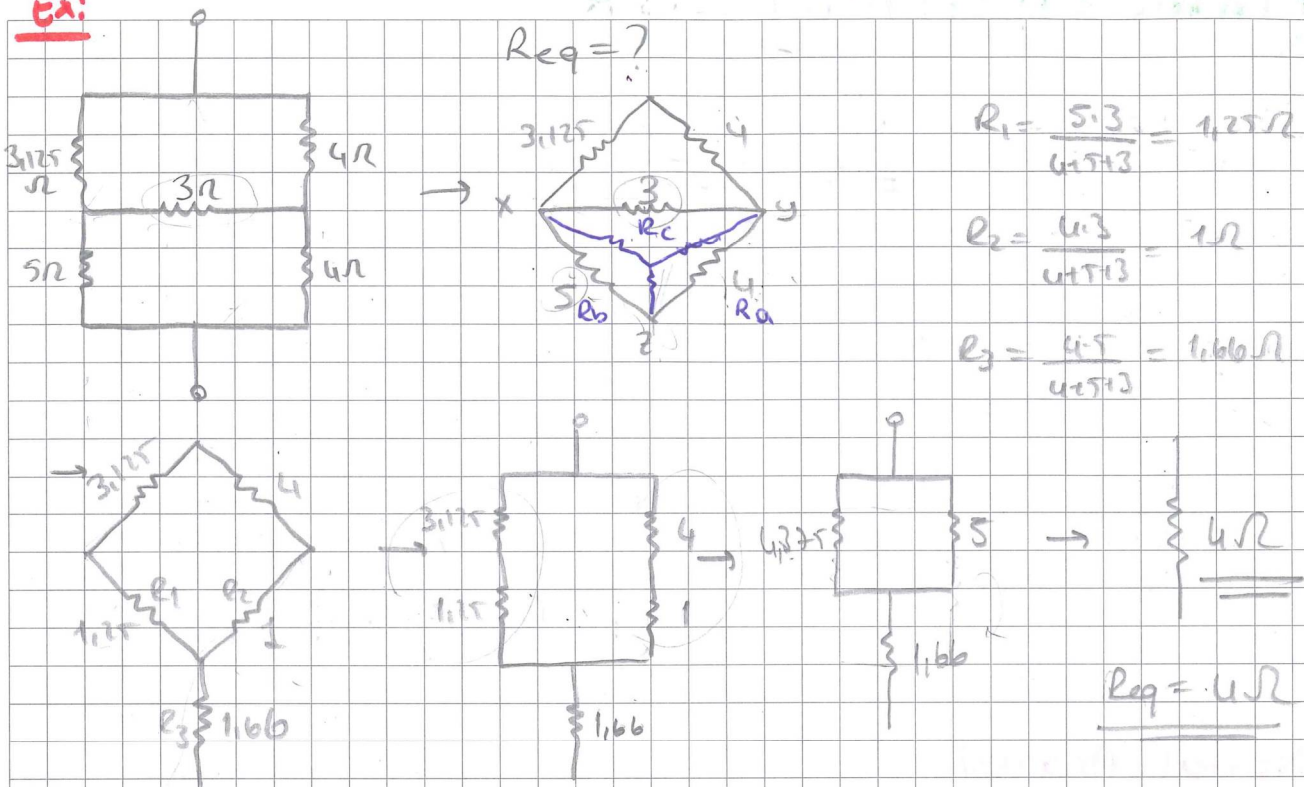

- # Distribution of power in stators and windings in motors/generators.
- Wye windings provide better torque at low rpm and delta windings generate better torque at high rpm.

* BRIDGE CIRCUITS *

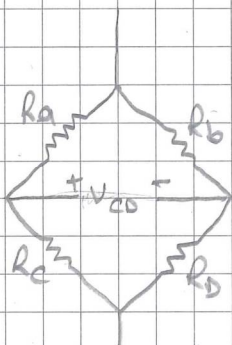


If $R_a = R_b = R_c = R_d$ then $V_{cd} = 0$

We can use this in sensing and full-wave rectifier circuits.

$$R_1 \cdot R_x = R_2 \cdot R_3$$

$$R_x = \frac{R_2 \cdot R_3}{R_1}$$

Wheatstone Bridge Circuit

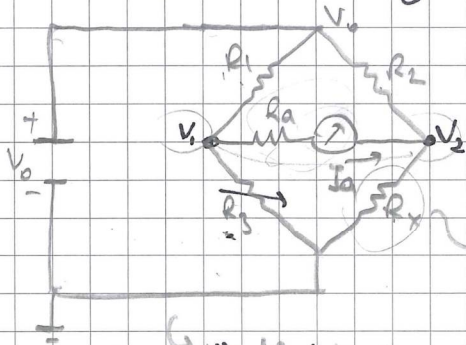

→ Measurement instrument based on differential measurement

* Balanced Condition; $I_d = 0$
 $V_1 = V_2$

$R_x = \left(\frac{R_2}{R_1} \right) R_3$ for balanced con.

(could be sensor and can be controlled by bridge)

If this is not balanced then you need to turn Δ / Y .

* NODAL & MESH ANALYSIS *

- Provide step-by-step instructions for nodal analysis, which is a method to calculate node voltages and currents that flow through component in circuit.
- Provide step-by-step instructions for mesh analysis, which is a method to calculate voltage drops and mesh currents that flow around loops in circuit.

! Remark: $a_1x + b_1y = c_1$
 $a_2x + b_2y = c_2$

→ Solution by Determinant

$$\begin{bmatrix} a_1 & b_1 \\ a_2 & b_2 \end{bmatrix} \begin{bmatrix} x \\ y \end{bmatrix} = \begin{bmatrix} c_1 \\ c_2 \end{bmatrix}$$


$$D = \begin{vmatrix} a_1 & b_1 \\ a_2 & b_2 \end{vmatrix} = a_1b_2 - a_2b_1$$

$$D_x = \begin{vmatrix} c_1 & b_1 \\ c_2 & b_2 \end{vmatrix}$$

$$D_y = \begin{vmatrix} a_1 & c_1 \\ a_2 & c_2 \end{vmatrix}$$

$$\left. \begin{array}{l} x = \frac{D_x}{D} \\ y = \frac{D_y}{D} \end{array} \right\}$$

→ Nodal Analysis

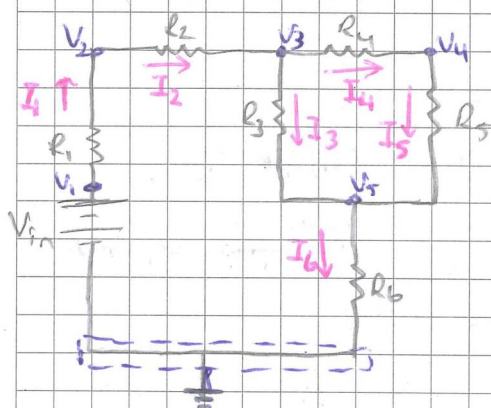


- 1) Define nodes and choose reference point.
- 2) Label the voltages at nodes
- 3) Label the currents flowing through at nodes
- 4) Use KCL
- 5) Use Ohm's Law to transform currents.
- 6) Solve equations.

* One or more of the node voltages may have a negative sign. This depends on which node you choose as your reference node.

* Node voltages must have a magnitude less than the sum of the voltage sources in the circuit.

→ Mesh Analysis


small loops in circuits

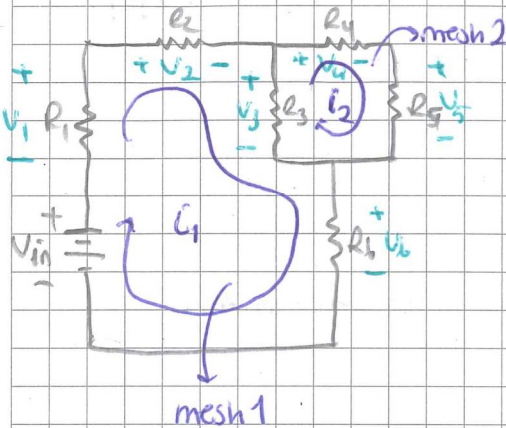

- 1) Define all meshes in the circuit.
- 2) label the current flowing in each mesh
- 3) label the voltage across each component
- 4) use KVL
- 5) use Ohm's law to transform voltages
- 6) Solve equations.

$$\left. \begin{array}{l} \text{Voltage } V_R \\ \text{Current } I_1 \\ \text{Current } I_2 \end{array} \right\} V_R = (I_1 + I_2)R$$

Ex:

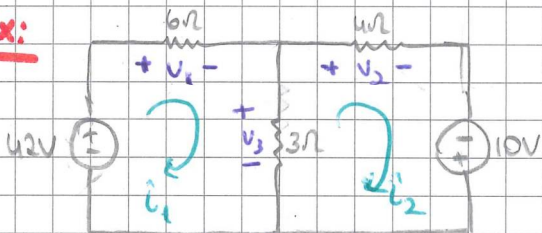

find the current flows on R_3 and V_3

$$\text{KVL @ 1st mesh} \rightarrow -42 + V_1 + V_3 = 0$$

$$\Rightarrow -42 + 6i_1 + (i_1 - i_2)3 = 0$$

$$9i_1 - 3i_2 = 42$$

$$i_1 = 6A$$

$$i_2 = 4A$$

$$i_{R_3} = i_1 - i_2$$

$$i_{R_3} = 2A \rightarrow V_3 = 2 \cdot 3 = 6V$$


KVL @ 2nd Mesh

$$\rightarrow -V_3 + V_2 - 10V = 0$$

$$\Rightarrow -(i_1 - i_2)3 + 4i_2 - 10 = 0$$

$$-3i_1 + i_2 = 10$$

Ex:

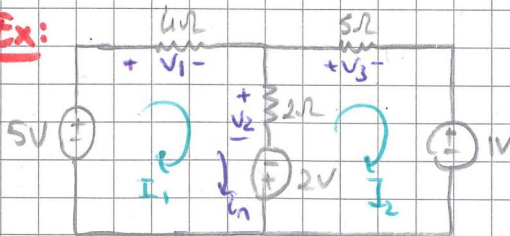

Determine the power supplied by the 2V source by using mesh analysis.

KVL @ 1st mesh

$$-5V + V_1 + V_2 - 2V = 0$$

$$-7V + 4i_1 + 2(i_1 - i_2) = 0$$

$$6i_1 - 2i_2 = 7V$$

KVL @ 2nd mesh

$$2V - V_2 + V_3 + 1V = 0$$

$$3V - 2(i_2 - i_1) + 5i_2 = 0$$

$$-2i_1 + 7i_2 = 3V$$


$$i_1 = 1.132A, i_2 = -0.1053A$$

$$I_n = (i_1 - i_2) = 1.23A$$


$$P_{2V} = (-)(2V)(1.23)$$

$$= -2.47W$$

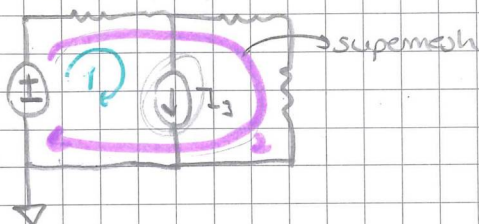Supermesh: A mesh that contains multiple meshes with a shared current source.



Ex:

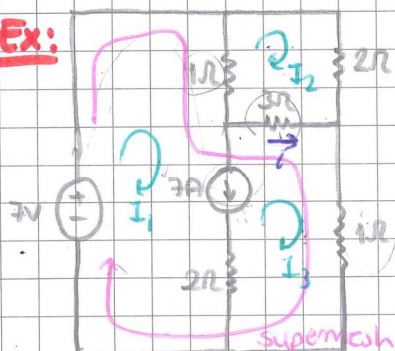

Determine the current i by using Mesh Analysis

KVL @ supermesh

$$-7 + (I_1 - I_2) + 3(I_3 - I_2) + (I_3) = 0$$

$$I_1 - 4I_2 + 4I_3 = 7 \quad (1)$$

KVL @ mesh 2

$$(I_2 - I_1) + 2I_2 + 3(I_2 - I_3) = 0$$

$$-I_1 + 6I_2 - 3I_3 = 0 \quad (2)$$

independent current source is related to mesh current

$$I_1 - I_3 = 7A \quad (3)$$

$$D = \begin{bmatrix} 1 & -4 & 4 \\ -1 & 6 & -3 \\ 1 & 0 & -1 \end{bmatrix} \cdot \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 7 \\ 0 \\ 7 \end{bmatrix} = -14$$

$$D_{I_1} = \begin{bmatrix} 7 & -4 & 4 \\ 0 & 6 & -3 \\ 7 & 0 & -1 \end{bmatrix} = -126$$

$$D_{I_2} = \begin{bmatrix} 1 & 7 & 4 \\ -1 & 0 & -3 \\ 1 & 7 & -1 \end{bmatrix} = -35$$

$$D_{I_3} = \begin{bmatrix} 1 & -4 & 7 \\ -1 & 6 & 0 \\ 1 & 0 & 7 \end{bmatrix} = -28$$

$$I_1 = \frac{D_{I_1}}{D} = 9A$$


$$I_2 = \frac{D_{I_2}}{D} = 2.5A$$

$$I_3 = \frac{D_{I_3}}{D} = 2A$$

$$i = I_3 - I_2$$

$$i = -0.5A$$

Ex:

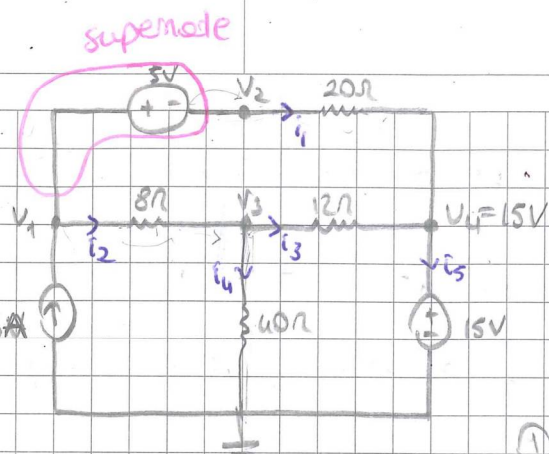

Find the V_1, V_2, V_3, V_4 by using Nodal Analysis.

KCL @ supernode

$$1.25A = i_1 + i_2$$

KCL @ V_3

$$i_2 = i_3 + i_4$$

$$1.25 = \frac{V_2 - 15}{20} + \frac{V_1 - V_3}{8}$$

$$\frac{V_1 - V_3}{8} = \frac{V_3 - 15}{12} + \frac{V_3}{40}$$

$$\textcircled{1} 5V_1 + 2V_2 - 5V_3 = 80$$

$$\textcircled{2} 15V_1 - 28V_3 = -150$$

By using the supernode

$$\textcircled{3} V_2 - V_1 = 5$$

$$\begin{bmatrix} 5 & 2 & -5 \\ 15 & 0 & -28 \\ -1 & 1 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 80 \\ -150 \\ 5 \end{bmatrix}$$

solve by matlab


$$V_1 = 22.4V$$

$$V_2 = 27.4V$$

$$V_3 = 17.4V$$

$$V_4 = 15V$$

Ex:

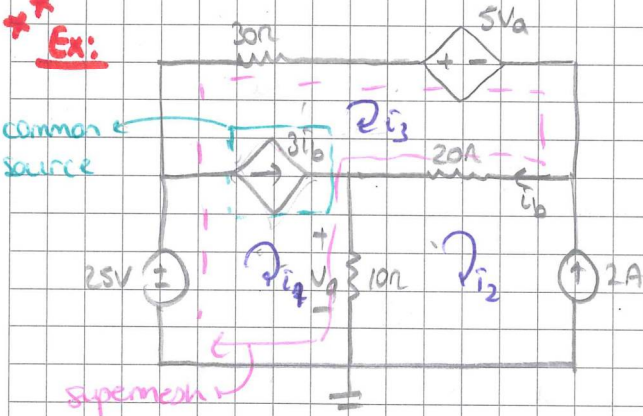

Find i_1, i_2, i_3 by using Mesh Analysis

KVL @ supernode

$$-25V + 30i_3 + 5V_a + 20(i_3 - i_2) + 10(i_1 - i_2) = 0$$

$$50i_3 + 60i_1 - 80i_2 = 25$$

$$60i_1 + 50i_3 = -135 \quad \textcircled{1}$$

$$V_a = 10(i_1 - i_2)$$

$$i_2 = -2A \quad \textcircled{3}$$

$$i_b = i_3 - i_2 = i_3 + 2$$

Use dependent current source

$$i_1 - i_3 = 3(i_b) \rightarrow i_1 - i_3 = 6$$

$$i_1 - 4i_3 = 6 \quad \textcircled{2}$$

if we solved $\textcircled{1}$ and $\textcircled{2}$ equations together

$$i_1 = 12.8A$$


$$i_2 = -2A$$

$$i_3 = -1.7A$$

→ Or if we want to solved by matrices

$$\begin{bmatrix} 60 & -80 & 50 \\ 1 & 0 & -4 \\ 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 25 \\ 6 \\ -2 \end{bmatrix}$$

* LINEAR SYSTEMS *

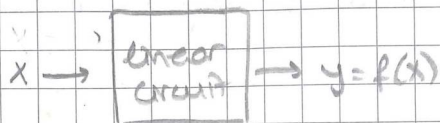

• if x is doubled $\rightarrow y = f(2x) = 2f(x)$

• if x is multiplied by a constant $a \rightarrow y = f(ax) = a f(x)$

• if $x = x_1 + x_2 \rightarrow y = f(x) = f(x_1 + x_2) = f(x_1) + f(x_2)$

then the system is linear

NOTE: $P = V \cdot I$


$$= I^2 R$$

$$= \frac{V^2}{R}$$

power has non-linear relation with current and voltage

linear components $\rightarrow$ resistor
 $\rightarrow$ capacitor
 $\rightarrow$ inductor
 $\rightarrow$ indep. sources

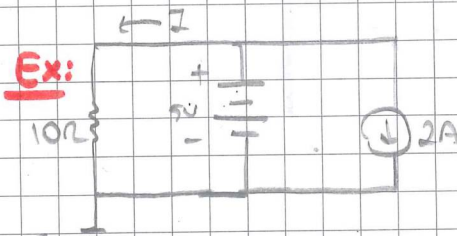
non-linear components $\rightarrow$ diodes
 $\rightarrow$ transistor
 $\rightarrow$ SCRs
 $\rightarrow$ magnetic switches



$I = ?$


* this circuit can be separated into two circuits and

$$I = I' + I''$$

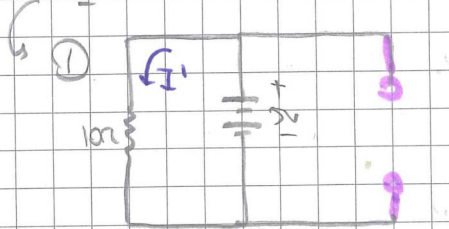


$$I' = 5V / 10\Omega = 0.5A$$

+

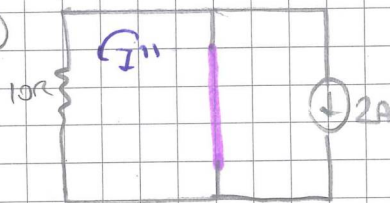

$$I'' = 0A \Rightarrow I = 0.5A$$

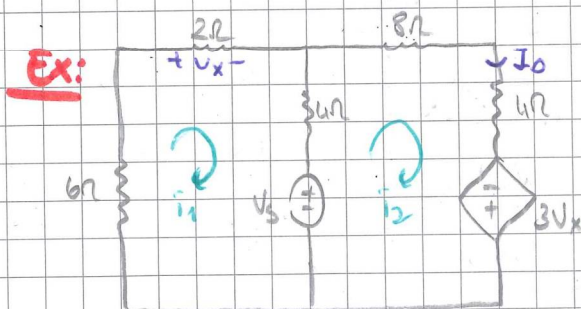

$I_o = ?$ when $V_s = 12$ & $V_s = 24V$

$\rightarrow$ By Mesh Analysis

KVL @ Mesh 1

$$6i_1 + 2i_1 + 4(i_1 - i_2) + V_s = 0$$

KVL @ Mesh 2

$$-V_s + 4(i_2 - i_1) + 6i_2 + 4i_2 - 3V_x = 0$$

$$i_1 = -6i_2$$

$$I_o = i_2, \quad i_2 = \frac{V_s}{76}$$

$$@ V_s = 12V \quad I_o = \frac{12}{76}$$

$$@ V_s = 24V \quad I_o = \frac{24}{76}$$

* this system is linear system because if we doubled input, the output doubled too.

* If your circuit is linear, your current sources addition must be equal to total current source.


* SUPERPOSITION *

→ Separating the contributions of the DC and AC independent sources.



① Voltage sources should be replaced with short circuits.

② Current sources should be replaced with open circuits.

Ex:

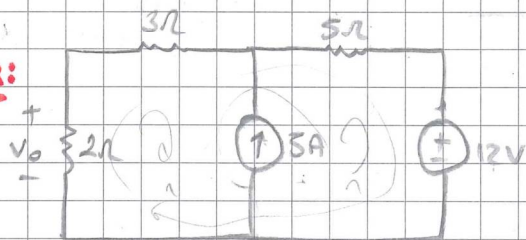

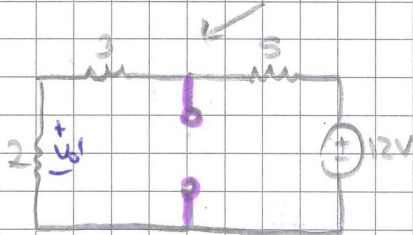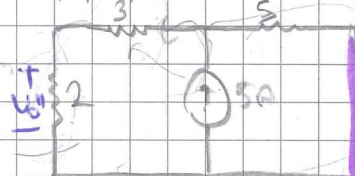Use the superposition theorem to find V_0 .



$$V_0' = (12) \left(\frac{2}{10} \right)$$


$$V_0' = 2.4V$$

$$V_0'' = I_0 \cdot 2 = \frac{5A \cdot 5\Omega}{10} \cdot 2 = 5V$$


$$I_0 = \frac{5 \cdot 5}{10}$$

$$V_0 = V_0' + V_0'' = \underline{\underline{7.4V}}$$

Ex:

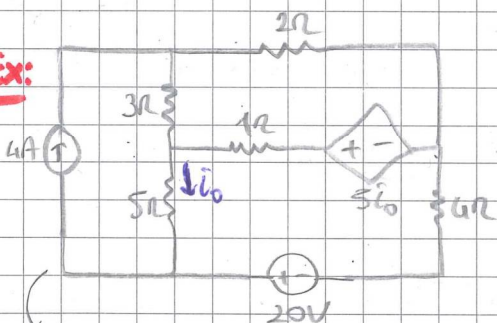

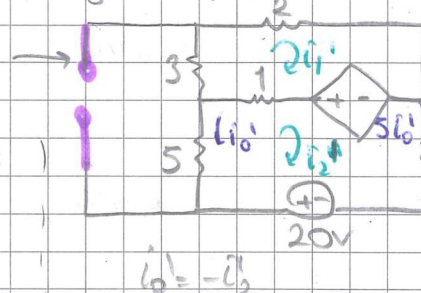Using the superposition theorem find I_0 .



$$3i_1' + 2i_1' - 5i_0' + (i_1' - i_2') = 0$$


$$6i_1' + 4i_2' = 0$$

$$-20 + 5i_1' + i_1' - i_1' + 5i_0' + 4i_2' = 0$$

$$-4i_1' + 5i_2' = 20$$

$$i_1' = 3.53A$$

$$i_0' = -3.53A$$

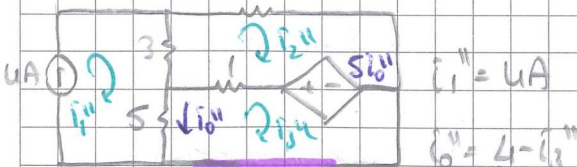

$$2i_2'' - 5i_0'' + i_2'' - i_2'' + 3(i_2'' - 4) = 0$$

$$6i_2'' + 4i_2'' = 32$$

$$i_2'' - i_2'' + 5i_0'' + 4i_2'' + 5(i_2'' - 4) = 0$$

$$5i_2'' - i_2'' = 0$$


$$i_2'' = 0.94A$$

$$i_0'' = 3.06A$$


$$I_0 = i_0' + i_0''$$

$$= \underline{\underline{-0.47A}}$$


Ex:

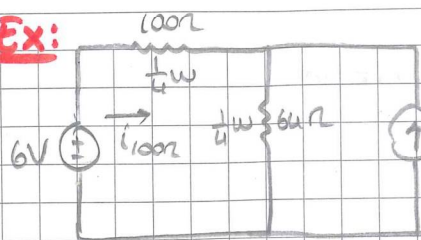

Find the maximum value of I_x

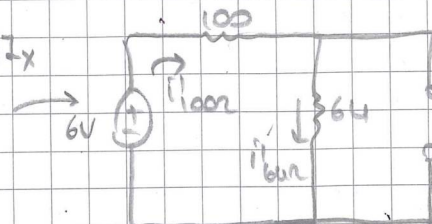
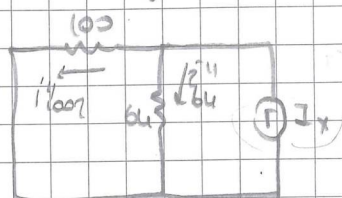
$$\left. \begin{array}{l} i_{100\Omega} \\ i_{64\Omega} \end{array} \right\} \text{same} = \frac{6}{164} = \underline{\underline{37\text{mA}}}$$



$$i_{100}'' = \frac{64\Omega}{164\Omega} I_x$$

$$i_{64}'' = \frac{100\Omega}{164\Omega} I_x$$

→ Power rate = $\frac{1}{4}W$ in the initial circuit;

$$i_{100} \leq \sqrt{\frac{0.25W}{100\Omega}} \Leftrightarrow P_{100\Omega} = (i_{100})^2 \cdot 100 \leq 0.25W$$

$$i_{64} \leq \sqrt{\frac{0.25W}{64\Omega}} \Leftrightarrow P_{64\Omega} = (i_{64})^2 \cdot 64 \leq 0.25W$$

a) The maximum power of $i_{100} \leq 50\text{mA}$

b) The maximum power of $i_{64} \leq 62.5\text{mA}$

In the original circuit; $i_{64} = i_{64}' + i_{64}''$

$$i_{100} = i_{100}'' - i_{100}'$$

$$\frac{64}{164} I_x$$

$$\rightarrow 37\text{mA}$$

because the direction of current flows

a-1) from eq a) $(i_{100}'' - i_{100}') \leq 50\text{mA} \Rightarrow I_x \leq (87\text{mA}) \frac{164}{64}$

b-1) from eq b) $(i_{64}' + i_{64}'') \leq 62.5\text{mA} \Rightarrow I_x \leq (25\text{mA}) \frac{164}{100}$

$$37\text{mA}$$

$$\frac{100}{164} I_x$$


a-1) $I_x \leq 222.9\text{mA}$ } It needs to satisfy both of them so:

b-1) $I_x \leq 41\text{mA}$


The final $I_x \leq 41\text{mA}$

* SOURCE TRANSFORMATION *

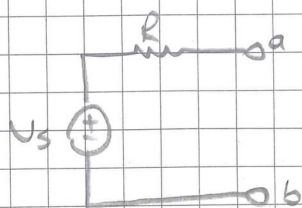→ is the process of replacing a voltage source V_s in series with a resistor R by a current source I_s in parallel with a resistor R , or vice versa.



$$V_s = I_s R$$

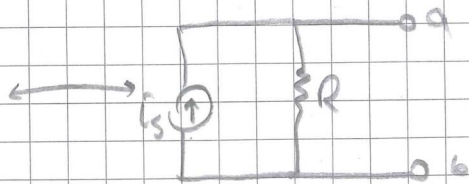

$$I_s = \frac{V_s}{R}$$

→ source transformation can apply on dependent sources.

for voltage sources

→ ideal: An ideal voltage source has no internal resistance

→ real: A real voltage source modeled as an ideal voltage source in series with a resistor. → (limiter)

for current sources

→ ideal: An ideal current source has no internal resistance.


→ real: A real current source is modeled as an ideal current source in parallel with a resistor. → (limiter)

Applied for both voltage and current sources

$$R = 0\Omega \rightarrow P = 0W$$

$$R = \infty\Omega \rightarrow P = 0W$$

Ex:

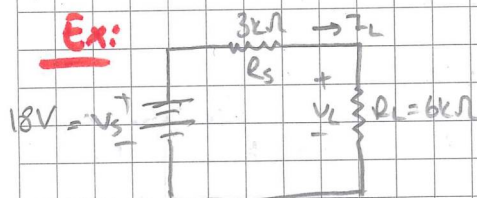


→ Find an equivalent current source to replace V_s and R_s in the circuit

→ Find I_L and V_L

$$V_L = \frac{R_L}{R_L + R_s} V_s$$
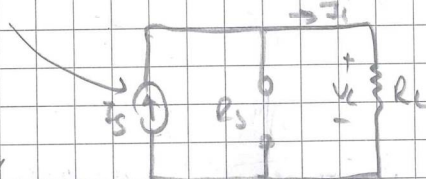
$$V_L = \frac{6k\Omega}{6k\Omega + 3k\Omega} 18 = 12V$$



$$I_s = I_L$$

$$V_L = 2mA(6k\Omega) = 12V$$

$$P_L = 12V \cdot 2mA = 24mW = P_{I_s}$$

$$I_L = V_L / R_L = 2mA$$

→ if $R_s = 20k\Omega$

$$P_{I_s} = P_L + P_{R_s} = 12 \cdot (2mA) + (18-12) \cdot (2mA) = 36mW$$

$$I_s = \frac{R_L + R_s}{R_s} I_L = 2.67mA$$

$$V_L = 12V \rightarrow P_{I_s} = 32mW$$

→ if $R_s = 3k\Omega$

→ if $R_s = 6k\Omega$

$$I_s = \frac{R_L + R_s}{R_s} I_L = 6mA$$

$$I_s = \frac{R_L + R_s}{R_s} I_L = 4mA$$

$$V_L = 12V \rightarrow P_{I_s} = 72mW$$


$$V_L = 12V \rightarrow P_{I_s} = 48mW$$

↓ R_s , ↑ P_{I_s}


→ but absorbed power is the same
(vaynaxan dola parla enaji kexyor oia
harcenar enaji ayin)

Ideal Source → @ $R_s = R_L$ condition

* THEVENIN and NORTON EQUIVALENT *

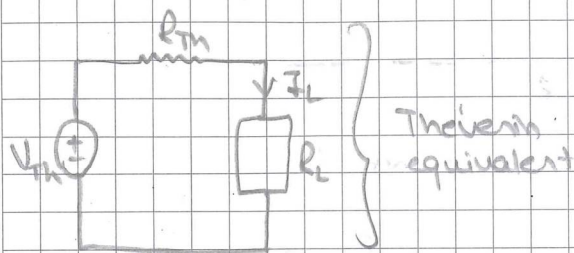

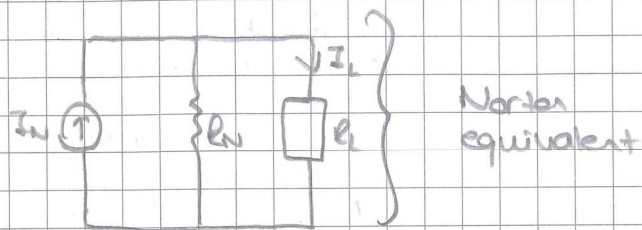
$$I_L = \frac{V_{th}}{R_{th} + R_L} \quad V_{th} = I_N \cdot R_{th}$$



$$I_N = \frac{V_{th}}{R_{th}} \quad R_N = R_{th}$$

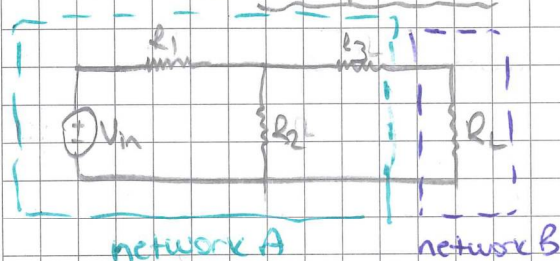→ We have 4 approaches to find Thevenin Equivalent.



1st approach: Use repeated source transformations to arrive at a single voltage source in series with a single series resistance.

2nd approach: Open the load and determine the open-circuit voltage (Voc), then short the load and determine short-circuit current (Isc).


3rd approach: Open the load and determine the open-circuit voltage (Voc) then deactive all independent sources and find the Req.

We use only dependent sources ←

4th approach: Open the load and determine the open-circuit voltage (Voc), then deactivate all independent sources and apply test source (Vt).




$$V_{th} = V_{oc} \quad V_t = R_{th} \cdot I_{test}$$

Ex:

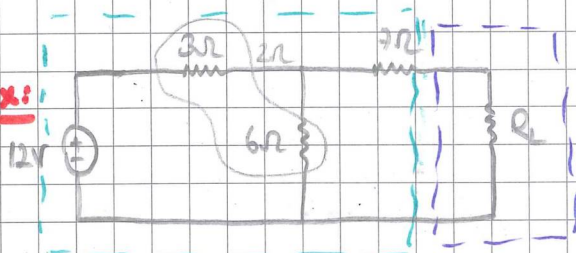

Find the Thevenin equivalent of this circuit, find the maximum power



→ by the 1st approach:

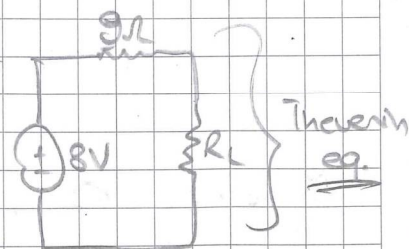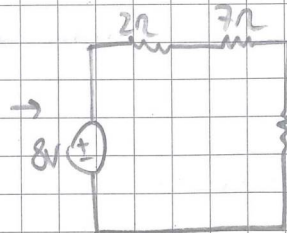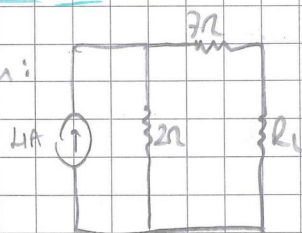

$$P_{max} \Rightarrow P_L = \left(\frac{8}{9 + R_L} \right)^2 R_L$$


$$8V = V_{th} \quad 9\Omega = R_{th}$$

→ by the 2nd approach:

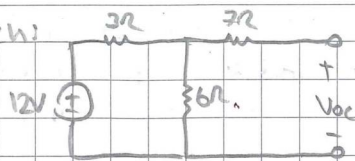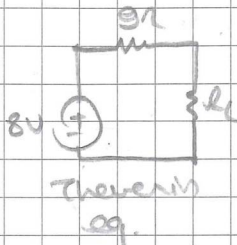

$$\begin{cases} V_{oc} = 12 \left(\frac{6}{3+6} \right) \\ V_{oc} = 8V = V_{Th} \end{cases}$$


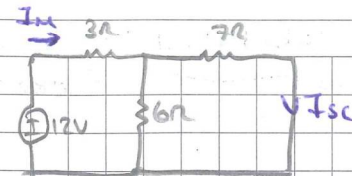
$$R_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{8}{0.89} = 9\Omega$$




$$I_{sc} = \frac{12}{3+7+6} = 1.92A \text{ (total I)}$$

$$I_{sc} = \frac{1.92 \times 6}{13} = 0.89A$$

→ by the 3th approach:

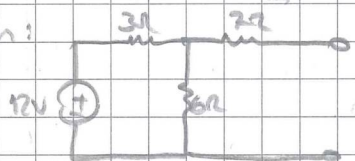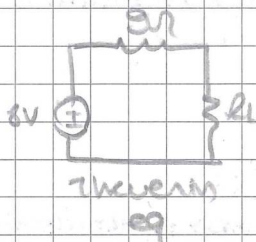


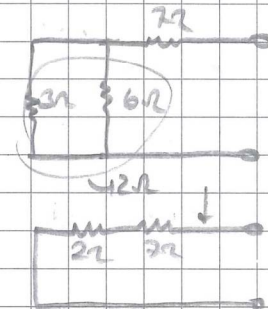
$$\begin{cases} V_{oc} = 12 \left(\frac{6}{3+6} \right) \\ V_{oc} = 8V = V_{Th} \end{cases}$$



$$R_{eq} = 12\Omega$$

$$R_{Th} = 9\Omega$$

→ by the 4th approach:

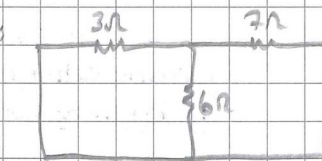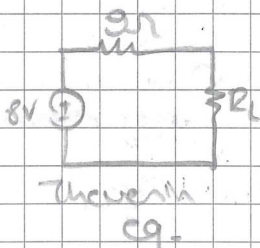


$$\begin{cases} V_{oc} = 12 \left(\frac{6}{3+6} \right) \\ V_{oc} = 8V = V_{Th} \end{cases}$$

test voltage ($V_t = 1V$)

$$I_{test} = \frac{1V}{9\Omega} = 0.11A$$

$$R_{test} = \frac{V_t}{I_t} = 9\Omega$$

Ex:

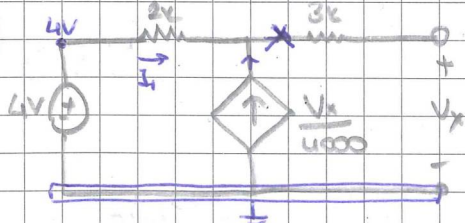


Find the V_x and thevenin equivalent of the circuit

by the 2nd approach → $V_{oc} = V_{Th} = V_x$


if we apply KCL

$$\frac{4V - V_x}{2000} + \frac{V_x}{4000} = 0 \rightarrow V_x = 8V$$

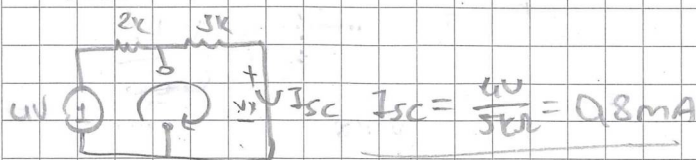
$$\begin{aligned} R_{Th} &= \frac{V_{oc}}{I_{sc}} \\ &= \frac{8V}{0.8mA} = 10k\Omega \end{aligned}$$



$$I_{sc} = \frac{4V}{5k\Omega} = 0.8mA$$

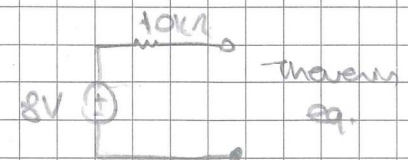


Ex:

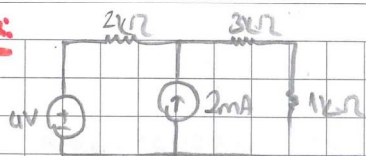


Determine the Thevenin and Norton eq. circuits for the network faced by the 1k resistor.

① → by the source transformation:

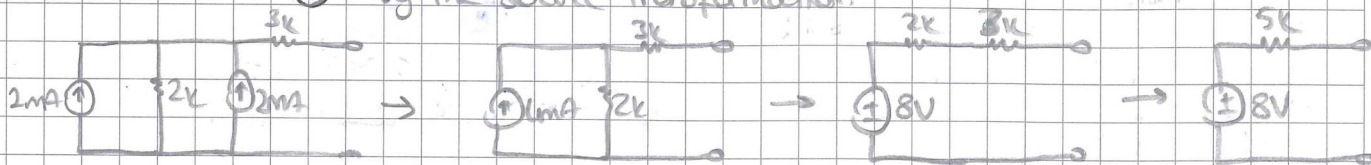

② → by the 3rd approach:

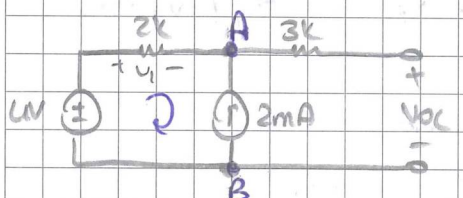→ find the V_{oc} , find R_{Th} , when all the indep. sources are killed




$$KVL \rightarrow -4V + V_1 + V_{oc} = 0$$

$$V_1 = -4V$$


$$V_{oc} = V_{AB} = V_{Th}$$

$$V_{oc} = 8V = V_{Th}$$

to find R_{Th}

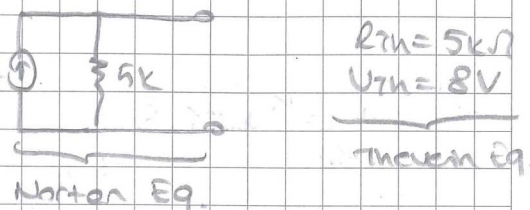


Thevenin Eq.

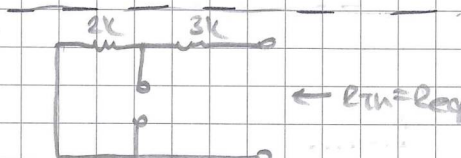

$$R_{eq} = 5k$$

Ex:

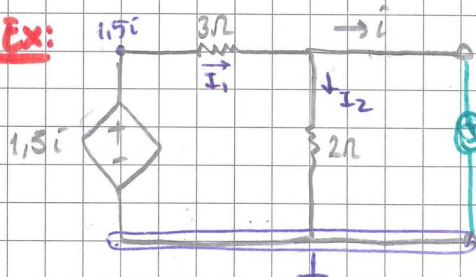

Find the thevenin equivalent of this circuit.

by the 1st approach $V_{Th} = 0 \rightarrow R_{Th}?$


$$I_1 = I_2 + i$$

$$R_{Th} = \frac{V_{Test}}{I_{Test}}$$

$$\frac{1.5i - 1}{3} = \frac{1}{2} + i \rightarrow i = -\frac{5}{3}A \quad I_{Test} = \frac{5}{3}A \quad R_{Th} = \frac{1}{5/3} = \frac{3}{5}$$

$$R_{Th} = 0.6\Omega$$

→ Power from a Practical Source :

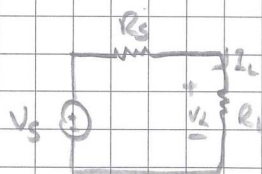

$$P_L = I_L \cdot V_L = \frac{V_s^2 R_L}{(R_s + R_L)^2}$$


→ Maximum power is delivered to the load when the load resistance (R_L) is equal to the Thevenin resistance (R_{Th}) of the circuit.

$$\text{if } R_L = R_s \rightarrow \frac{V_s^2}{4R_s}$$


$$\frac{d}{dR_L} P_L = 0 \rightarrow \text{for the max power}$$

(Maximum Power Transfer Theorem)

Ex:

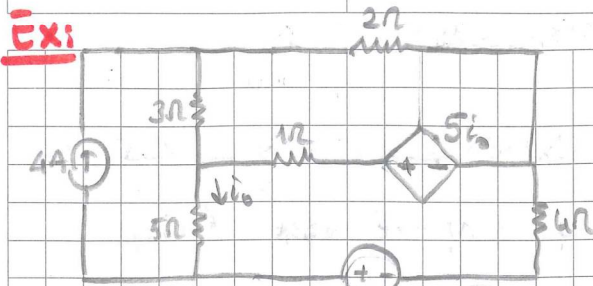

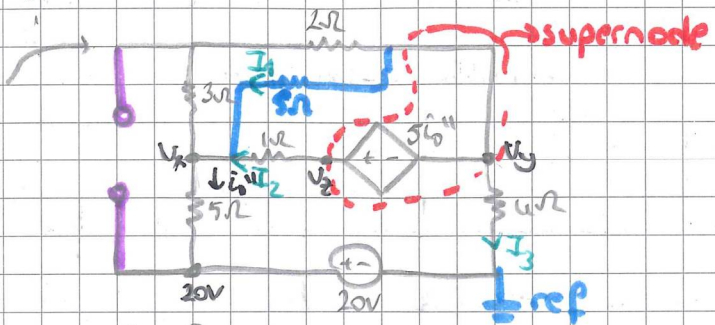Find i_o in the circuit with superposition



→ KCL @ V_x
 $i_1 + i_2 - i_o'' = 0$

$\frac{V_y - V_x}{5} + \frac{V_z - V_x}{1} = \frac{V_x - 20}{5} \rightarrow 7V_x - V_y - 5V_z = 20$ ①

→ KCL @ supernode

$i_1 + i_2 + i_3 = 0$

$\frac{V_y - V_x}{5} + \frac{V_z - V_x}{1} + \frac{V_y}{4} = 0 \rightarrow -2V_x + 9V_y + 20V_z = 0$ ②

→ @ supernode $V_z - V_y = 5i_o''$

$V_x + V_y - V_z = 20$ ③

$$\begin{bmatrix} 7 & -1 & -5 \\ -2 & 9 & 20 \\ 1 & 1 & -1 \end{bmatrix} \begin{bmatrix} V_x \\ V_y \\ V_z \end{bmatrix} = \begin{bmatrix} 20 \\ 0 \\ 20 \end{bmatrix}$$

$V_x = 2.35V$
 $V_y = 16.12V$
 $V_z = -3.53V$

$i_o'' = \frac{V_x - 20}{5} = -3.53A$

$i_o = i_o' + i_o'' = -0.67A$

→ by the Mesh Analysis

$i_1 = 4A$, $i_o = i_1 - i_3$

→ @ mesh 2

$3(i_2 - i_1) + 2i_2 - 5i_o' + (i_2 - i_3) = 0$

① $6i_2 + 4i_3 = 32$

→ @ mesh 3


$(i_3 - i_2) + 5i_o' + 4i_3 + 5(i_3 - i_1) = 0$

② $i_2 + 5i_3 = 0$


$i_2 = 4.7A$
 $i_3 = 0.94A$
 $i_1 = 4A$

$i_o' = i_1 - i_3 = 3.06A$

Ex:

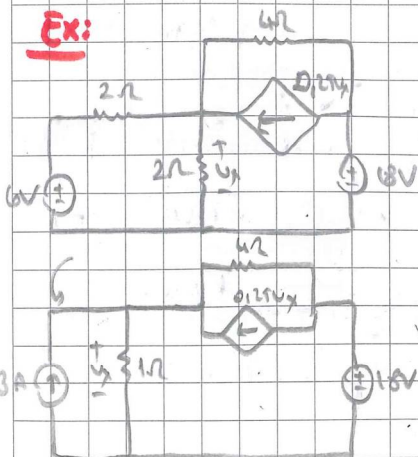

Find the V_x using source transformation

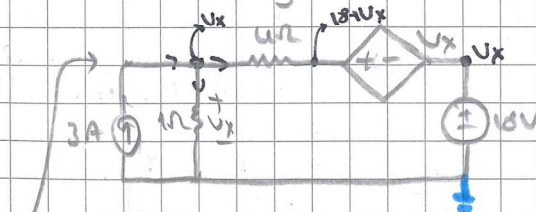


KCL @ V_x

$3A = \frac{V_x}{1} + \frac{(V_x - 18 - V_x)}{4}$

$V_x = 7.5V$

NOTE: Source transformation can apply only in series sources.

Ex:

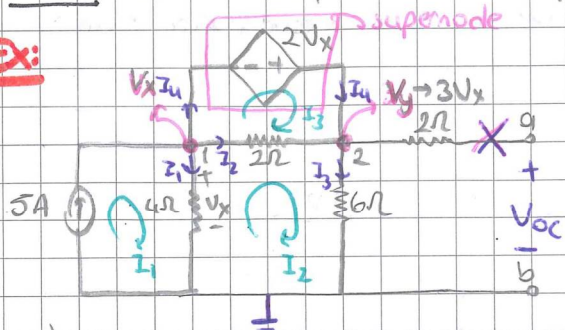

Find the Thevenin equivalent of this circuit.

1st way → by the Nodal Analysis

$$V_y = V_x + 2V_x \quad \text{@ supernode}$$

$$V_y = 3V_x$$

2nd way → by the Mesh Analysis

$$I_1 = 5A$$

@ 2nd Mesh

$$V_x = 4(I_1 - I_2)$$

$$4(I_2 - I_1) + 2(I_2 - I_3) + 6I_2 = 0$$

$$5A = I_1 + I_2 + I_4$$

$$5 = I_1 + I_3$$

KCL @ node 2

$$I_2 + I_4 = I_3$$

$$I_4 = I_3 - I_2$$

@ 3rd Mesh

$$-2V_x + 2(I_3 - I_2) = 0$$

$$\textcircled{2} \quad 6I_2 + 3I_3 = 40$$

$$\textcircled{1} \quad 12I_2 - 2I_3 = 20$$

$$I_2 = 3.3A$$

$$I_3 = 10A$$

$$5 = \frac{V_x}{4} + \frac{3V_x}{6}$$

$$V_x = \frac{20}{3}$$


$$V_{oc} = 3V_x$$

$$\underline{\underline{V_{oc} = 20V}}$$

$$V_{oc} = V_{Th} = V_{ab} = I_2 \cdot 6$$

$$\underline{\underline{V_{oc} = 20V}}$$

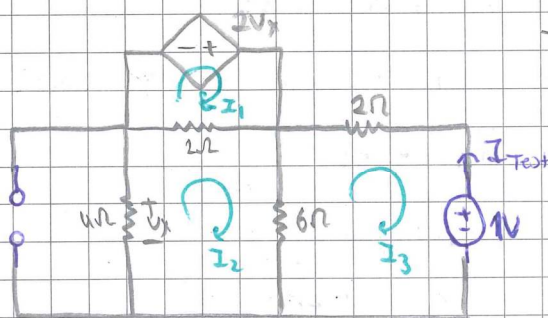after we find V_{oc} , by the u^{th} approach (adding test source)



→ we killed all the independent sources

by Mesh Analysis $V_x = -4I_2$

@ 1st Mesh

@ 2nd Mesh

$$-2V_x + 2(I_1 - I_2) = 0$$

$$V_x + 2(I_2 - I_1) + 6(I_2 - I_3) = 0$$

$$\textcircled{1} \quad 2I_1 + 6I_2 = 0$$

$$\textcircled{2} \quad -2I_1 + 12I_2 - 6I_3 = 0$$

@ 3rd Mesh

$$6(I_3 - I_2) + 2I_3 + 1 = 0$$


$$\textcircled{1} \quad -6I_2 + 8I_3 = -1$$

$$I_3 = -1/6A$$

$$I_{test} = -I_3$$


$$\underline{\underline{I_{test} = 1/6A}}$$
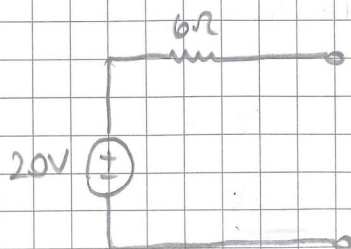
$$\begin{bmatrix} 2 & 6 & 0 \\ -2 & 12 & -6 \\ 0 & -6 & 8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ -1 \end{bmatrix}$$



Thevenin Equivalent
Circuit

Ex:


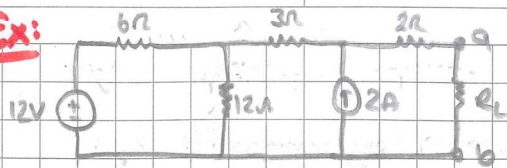


Find the value of R_L for max power transfer in the circuit, and find the maximum power.

for the max power, $R_L = R_{Th}$

→ by the 3rd approach (kill all dep. sources to find R_{Th})

→ Remove R_L and find V_{Th}

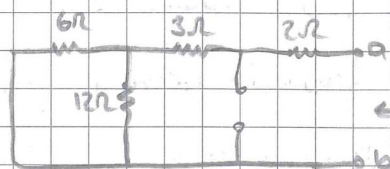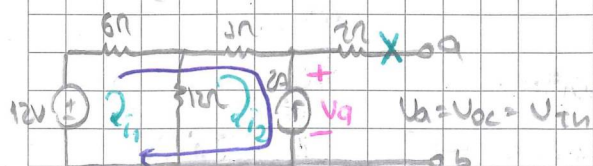

$R_{ab} = R_{Th} = 9\Omega$

by the Mesh Analysis $i_2 = -2A$

@ 1st mesh

KVL @ blue direction

$$-12 + 6i_1 + 12(i_1 - i_2) = 0$$

$$-12 + V_1 + V_2 + V_{ab} = 0$$

$$i_1 = -2/3 A$$


$$-12 + (6i_1) + 3i_2 + V_{ab} = 0$$

$$\underline{V_{ab} = 22V = V_{Th}}$$

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}}$$

$$P_{max} = \frac{22^2}{4 \cdot 9} = \underline{\underline{13.44W}}$$

* PROBLEM SOLVING PART 1 *

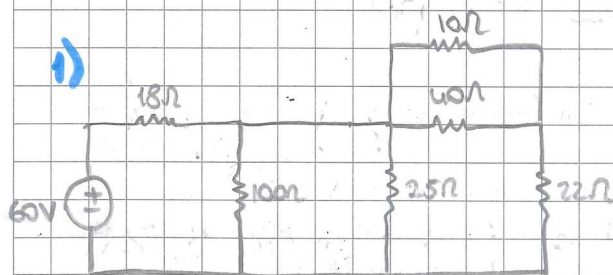

Look at the figure and,

a) Use voltage division to find the voltage drop across the 18Ω resistor positive at the left.

$$R_{eq} = 100\Omega \parallel 25\Omega \parallel 22\Omega + (10\Omega \parallel 40\Omega)$$

$$R_{eq} = 12\Omega$$

$$V_{18\Omega} = 60 \cdot \frac{18}{18+12} = \underline{\underline{36V}}$$

b) Find the current flowing in the 18Ω with using your result in (a).

$$I_{18\Omega} = \frac{36V}{18\Omega} = \underline{\underline{2A}}$$

d) Using your result in (c), find $V_{25\Omega}$


$$V_{25\Omega} = (0.96A) \cdot 25\Omega = \underline{\underline{24V}}$$

c) Starting with your result in (b) and use current division to find $I_{25\Omega}$.

$$I_{25\Omega} = (2A) \cdot \frac{100\Omega \parallel 25\Omega \parallel 30\Omega}{25\Omega} = \underline{\underline{0.96A}}$$

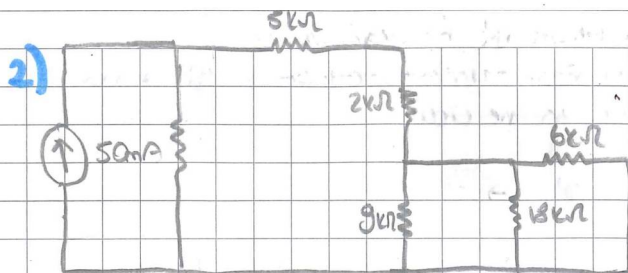e) find $V_{10\Omega}$ with voltage division.

$$V_{10\Omega} = (24V) \cdot \frac{8}{22 + (10 \parallel 40)} = \underline{\underline{6.4V}}$$



c) $V_{2k\Omega} = ?$ (by voltage division)

$$V_{2k\Omega} = (250) \frac{2k}{5k + 2k + 18k} = \underline{50V}$$

d) $I_{2k\Omega} = ?$

$$I_{2k\Omega} = \frac{50V}{2k\Omega} = \underline{25mA}$$

find the results according to figure

a) $I_{10k\Omega} = ?$ (by current division)

$$R_{eq} = 5k + 2k + (8k \parallel 18k \parallel 6k) = 10k\Omega$$


$$I_{10k\Omega} = (50mA) \frac{10k \parallel 10k}{10k} = \underline{25mA}$$

b) $V_{10k\Omega} = ?$

$$V_{10k\Omega} = (25mA)(10k\Omega) = \underline{250V}$$

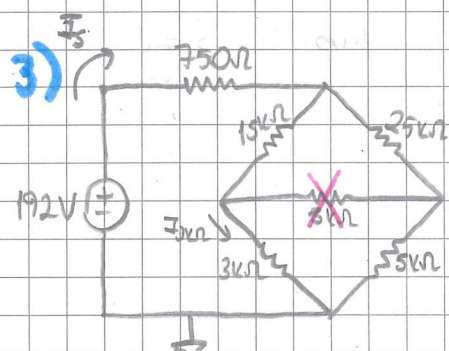e) $I_{18k\Omega} = ?$ (by current division)

$$I_{18k\Omega} = (25mA) \frac{(9k \parallel 18k \parallel 6k)}{18k} = \underline{4.167mA}$$



$15k\Omega \times 55k\Omega = 3k\Omega \times 25k\Omega$
 so we can cancel the 5kΩ


find the power dissipated in the $3k\Omega$ resistor in the circuit.

$$R_{eq} = 750 + 18k \parallel 30k = 12k\Omega$$

$$I_s = \frac{192V}{12k\Omega} = 16mA$$

$$I_{3k\Omega} = (16mA) \frac{18k \parallel 30k}{18k} = 10mA$$
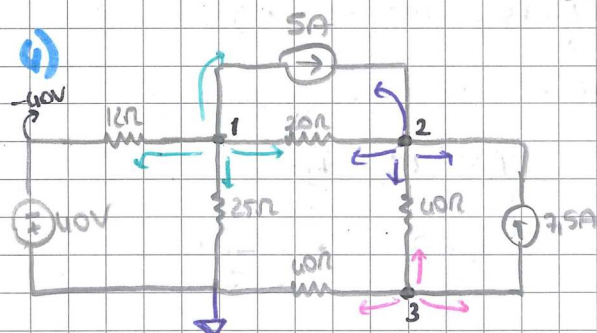
$$P_{3k\Omega} = i^2 R = (10mA)^2 (3k\Omega) = \underline{0.3W}$$



Use the node voltage method to find the total power dissipated in the circuit.

@ node 1 $\rightarrow \frac{V_1 - (-40)}{12} + \frac{V_1}{25} + 5A + \frac{V_1 - V_2}{20} = 0$

@ node 2 $\rightarrow -7.5A + \frac{V_2 - V_3}{40} + \frac{V_2 - V_1}{20} - 5A = 20$

@ node 3 $\rightarrow \frac{V_3}{40} + 7.5A + \frac{V_3 - V_2}{40} = 0$

$$V_1 = -10V, V_2 = 132V, V_3 = -84V$$

$$I_{40V} = \frac{-10 - 40}{12} = 2.5A$$

$$P_{12\Omega} = i^2 R = (2.5)^2 (12) = 75W \text{ diss.}$$


$$P_{25\Omega} = (-10V)^2 / 25 = 4W \text{ diss.}$$

$$P_{40V_{top}} = (-84)^2 / 40 = 176.4W \text{ diss}$$

$$P_{40V_{bot}} = (V_2 - V_3)^2 / R_{40} = 1166.4W \text{ diss}$$

$$P_{20\Omega} = (V_1 - V_2)^2 / R_{20} = 1008.2W \text{ diss}$$
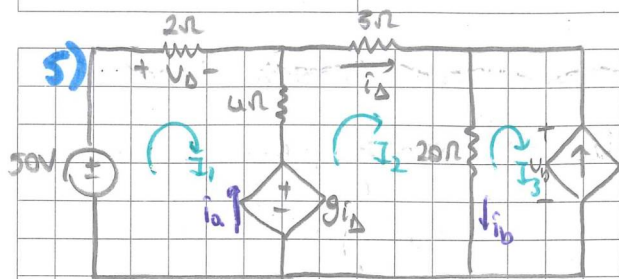
$$\rightarrow \Sigma P_{diss} = \underline{2430W}$$



a) Use the mesh current method to find which sources in the circuit are generating power.

@ 1st mesh $\rightarrow -5V + 2I_1 + 4(I_1 - I_2) + 9i_{\Delta} = 0$

$$6I_1 - 4I_2 + 9i_{\Delta} = 0$$

constraint equations: $i_{\Delta} = I_1$

@ 2nd mesh $\rightarrow -9i_{\Delta} + 4(I_2 - I_1) + 5I_2 + 20(I_2 - I_3) = 0$

$$-9i_{\Delta} + 28I_2 - 4I_1 - 20I_3 = 0$$

$$i_{\Delta} = I_1 - I_2 = 2 \text{ A}$$

$$i_{\Delta} = -1.7V_{\Delta}$$

$$i_{\Delta} = I_2 - I_3 = -1 \text{ A}$$

$$V_{\Delta} = 2I_1$$

$$V_{\Delta} = -20 \text{ V}$$

$$I_1 = -5 \text{ A}, I_2 = 16 \text{ A}, I_3 = 17 \text{ A}, V_{\Delta} = -50 \text{ V}, i_{\Delta} = 16 \text{ A}$$


$$P_{50V} = (-)(50)(-5 \text{ A}) = 250 \text{ W (absorbing)}$$

$$\rightarrow P_{9i_{\Delta}} = (-)(108)(2 \text{ A}) = -216 \text{ W (delivering/generating)}$$

$$\rightarrow P_{1.7V_{\Delta}} = (-)(-17)(-20) = -340 \text{ W (delivering/generating)}$$

These two sources are generating power in the circuit.

* PROBLEM SOLVING PART 2 *

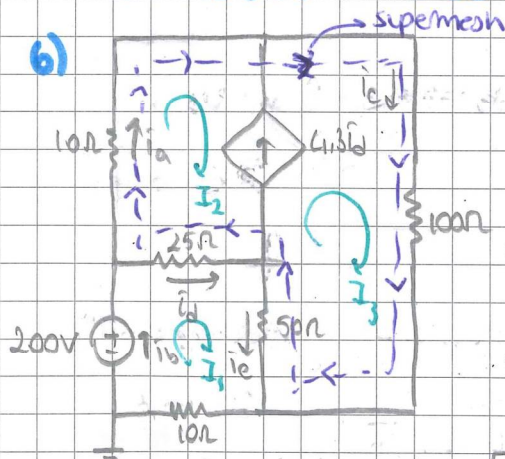

a) Use the mesh current method to find the branch currents in i_a to i_e in the circuit.

@ mesh 1 $\rightarrow -200 + 85I_1 - 25I_2 - 50I_3 = 0$ ①

@ supermesh $\rightarrow 150I_3 - 75I_1 + 35I_2 = 0$ ②

constraint eq: $4.13i_{\Delta} = I_3 - I_2$ $i_{\Delta} = I_1 - I_2$

$$4.13I_1 - 3.13I_2 - I_3 = 0$$
 ③

$$i_a = I_1 = 5.7 \text{ A}$$

$$i_b = I_1 = 4.16 \text{ A}$$

$$i_c = I_3 = 0.97 \text{ A}$$

$$i_d = I_1 - I_2 = -1.1 \text{ A}$$

$$i_e = I_1 - I_3 = 3.13 \text{ A}$$

$$\begin{bmatrix} 85 & -25 & -50 \\ -75 & 35 & 150 \\ 4.13 & -3.13 & -1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 200 \\ 0 \\ 0 \end{bmatrix}$$

$$I_1 = 4.16 \text{ A}$$

$$I_2 = 5.7 \text{ A}$$

$$I_3 = 0.97 \text{ A}$$

b) Show that $\sum P_{\text{diss}} = \sum P_{\text{gen}}$

$$P_{200V} = -920 \text{ W}$$

$$P_{4.13i_{\Delta}} = -399.68 \text{ W}$$

$$P_{10\Omega} = 324.9 \text{ W}$$

$$P_{100\Omega} = 94.09 \text{ W}$$

$$P_{50V} = 658.84 \text{ W}$$


$$P_{10\Omega} = 211.6 \text{ W}$$

$$P_{25\Omega} = 30.25 \text{ W}$$

$$\sum P_{\text{gen}} = -1319.68 \text{ W}$$

$$\sum P_{\text{diss}} = 1319.68 \text{ W}$$
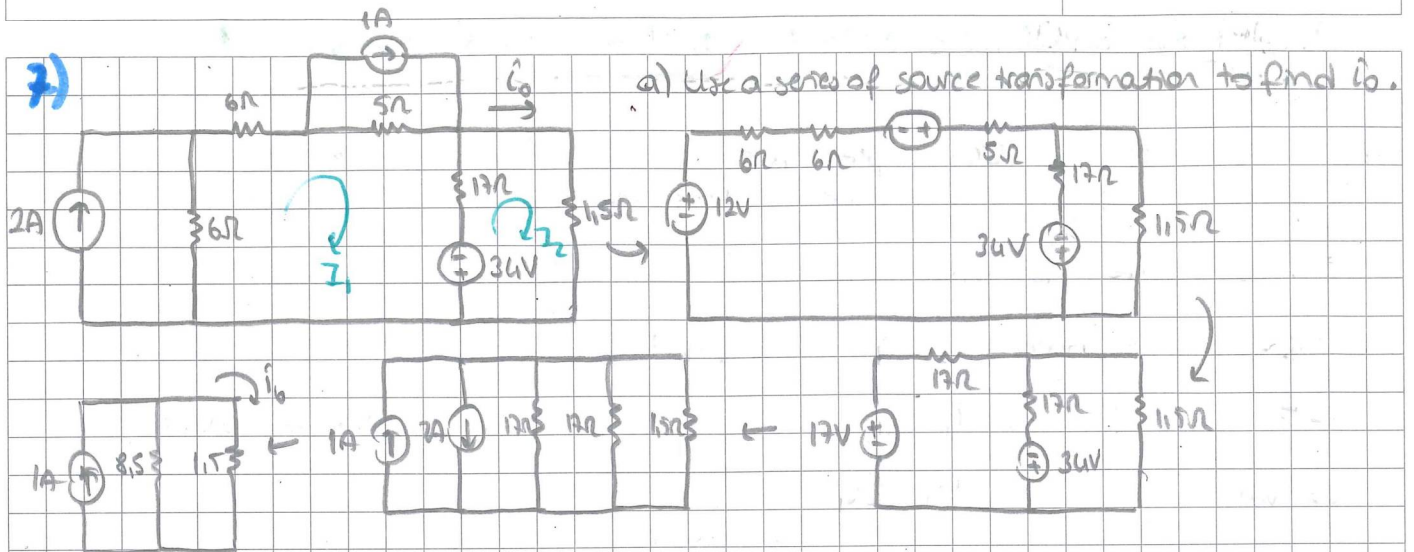
$$\sum P_{\text{diss}} = \sum P_{\text{gen}}$$






$$i_0 = (-1) \frac{8.5 \parallel 1.5}{1.5} = -0.85 \text{ A}$$

b) Verify your solution by using mesh analysis.

① mesh 1 $\rightarrow 34I_1 - 17I_2 = 51$ $I_1 = 1.07 \text{ A}$

② mesh 2 $\rightarrow -17I_1 + 16.5I_2 = -34$ $I_2 = -0.85 \text{ A} = i_0$
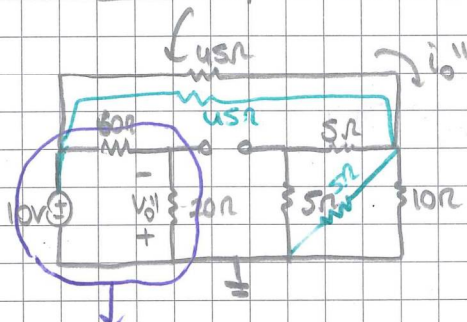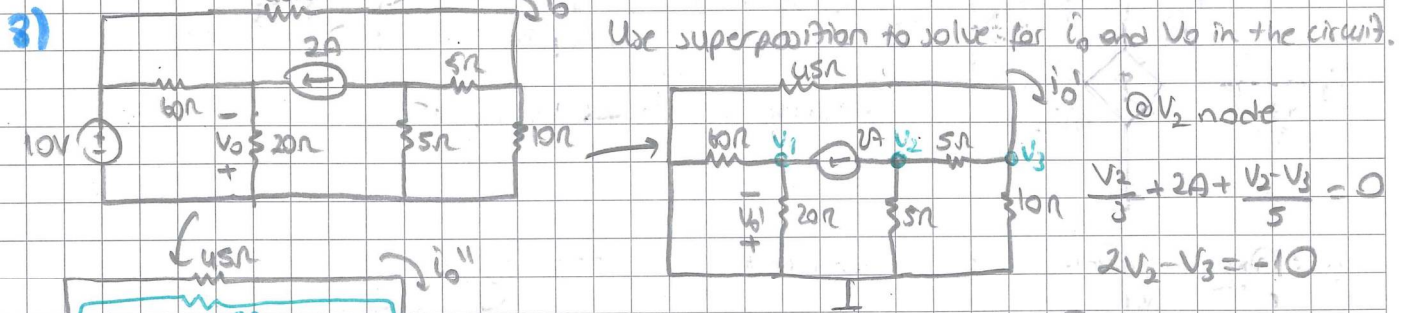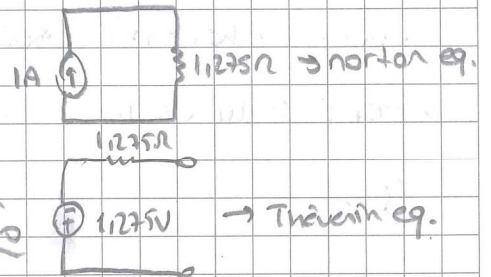
$$\begin{bmatrix} 34 & -17 \\ -17 & 16.5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 51 \\ -34 \end{bmatrix}$$



$$V_0' = (-0) \frac{20}{20+60} = -2.5 \text{ V}$$

$$i_0'' = \frac{10 \text{ V}}{5+5} = 0.2 \text{ A}$$

$$\begin{bmatrix} 2 & -1 \\ -18 & 29 \end{bmatrix} \begin{bmatrix} V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -10 \\ 0 \end{bmatrix}$$

$$V_2 = -7.25 \text{ V}$$

$$V_3 = -4.5 \text{ V}$$

$$i_0' = -V_3 / 5 = 0.1 \text{ A}$$

$$V_0' = 2 \cdot \frac{20 \parallel 60}{20} \cdot 20 = -30 \text{ V}$$


$$i_0 = i_0' + i_0'' = 0.3 \text{ A}$$

$$V_0 = V_0' + V_0'' = -32.5 \text{ V}$$

* OPERATIONAL AMPLIFIERS (OP-Amps) *

An Op-amps is a DC-coupled high-gain electronic voltage amplifier with a differential input and usually a single-ended output

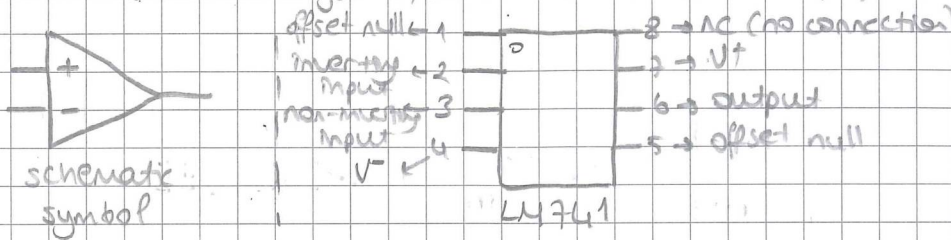→ In biomedical systems, we use instrumentation amplifiers.




* If we want to amplify voltage, we need to give energy.

* even we have no input, there will be an output.

* offset nulls use for finding output for no input, we should connect potentiometers.

* Op-Amps in Real Life *

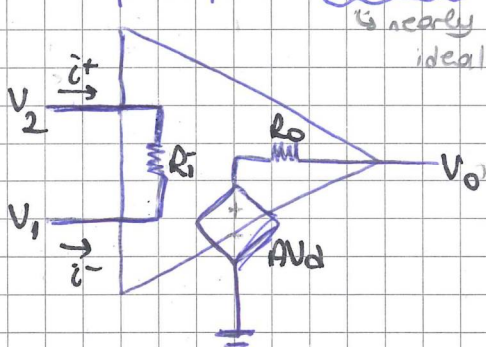

R_i → input resistor (very large)


R_o → output resistor (very small)

A → gain

V_d → voltage difference $V_d = V_2 - V_1$

V_o → output voltage

* Ideal Op-Amps *

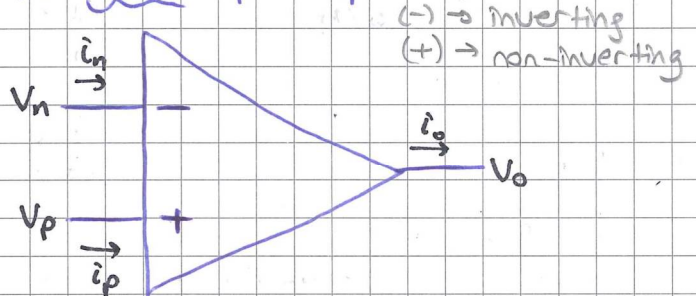

$$\rightarrow V^+ = V^- \quad V_n \approx V_p$$

$$\rightarrow i_n = i_p \approx 0 \quad (R_i = \infty)$$

$$A_v = \frac{V_o}{V_p - V_n}$$

we will assume that


* if we have no feedback resistor → open voltage gain

We use dB (decibels) → $10 \log (P/P_{ref})$, or $20 \log (V/V_{ref}) = x \text{ dB}$

Ex: $20 \log (V_o/V_{in}) = 20 \log (A) = 100 \text{ dB}$

$$A = 10^5$$

∇ A is frequency dependent ∇

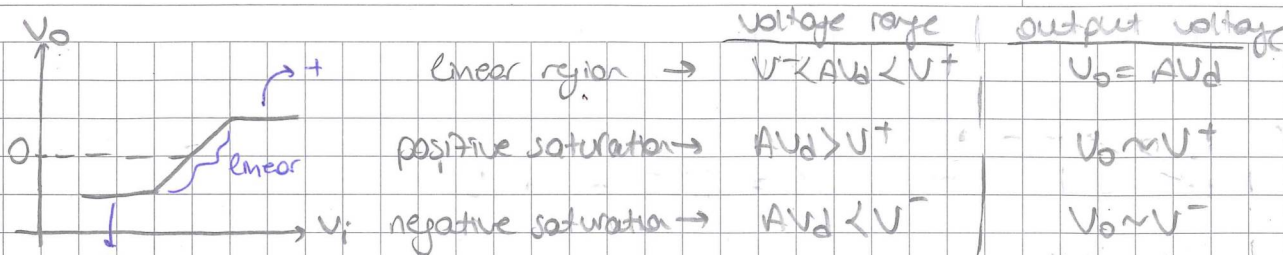

* Common Mode Rejection (rejects noises) *
(CMRR)

$$A_{cm} = \left| \frac{V_{ocm}}{V_{cm}} \right| \quad CMRR = \left| \frac{A}{A_{cm}} \right| \quad CMRR_{dB} = 20 \log \left| \frac{A}{A_{cm}} \right| dB$$

→ A is the differential gain, A_{cm} is the common mode gain

∇ if slew rate ↑, CMRR sensibility ↓


∇ if we choose $R_i = \infty$, $A = \infty$, $R_o = 0$ in real Op-Amps, we get ideal Op-Amps.

Ex: We want to build a sensor;

Temperature sensor → voltage

$T(^{\circ}C)$	$V(Volt)$
37.0	2.05
37.1	2.1
37.2	2.15
37.3	2.2
37.4	2.25
37.5	2.3

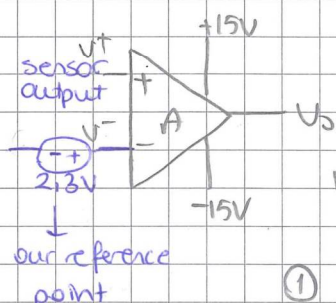If we have $37.5^{\circ}C$ and higher than this, we want to call doctor, and take $A=10^5$.



$$A(V^+ - V^-) = V_o$$

→ $2.3V$ our critical point

$$① V_o = (V_{so} - 2.3) 10^5$$

$$= (2.29 - 2.3) 10^5 = -1000V \rightarrow \text{negative saturates for all sensor outputs as;}$$


$$\underline{V_{so} < 2.3}$$

$$② V_o = (2.301 - 2.3) 10^5$$

$$= +100V \rightarrow \text{positive saturates for all sensor outputs as; } \underline{V_{so} > 2.3}$$


→ This types of circuits are called voltage comparator circuit.

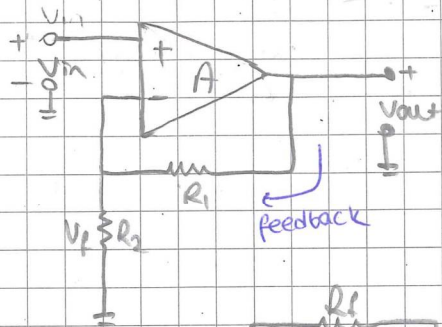* Feedback Mechanism (closed loop gain) *



$$G = \frac{V_{out}}{V_{in}} = 1 + \frac{R_1}{R_2}$$

Ex:

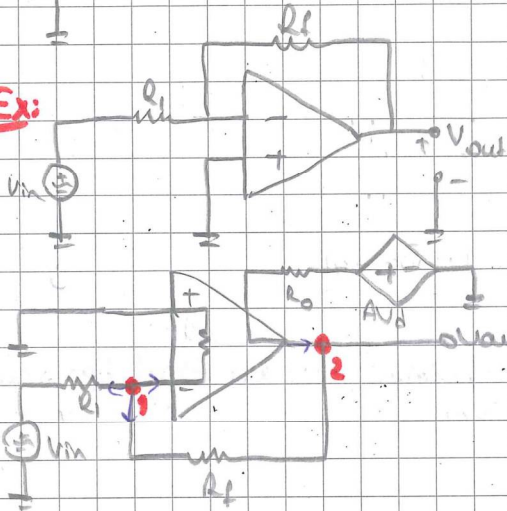

For a 741 Op-Amp ($A = 200,000$, $R_i = 2M\Omega$,

$R_o = 75\Omega$), $V_{in} = 5 \sin 3t \text{ mV}$, $V_{out} = ?$

$R_1 = 4.7k\Omega$

$R_f = 47k\Omega$

@ node 1

$$0 = \frac{-V_d - V_{in}}{R_1} + \frac{-V_d - V_{out}}{R_f} + \frac{-V_d}{R_i}$$


@ node 2

$$0 = \frac{V_{out} + V_d}{R_f} + \frac{V_{out} - A V_d}{R_o}$$

$$V_{out} = \left[\frac{R_o + R_f}{R_o - A R_f} \left(\frac{1}{R_1} + \frac{1}{R_f} + \frac{1}{R_i} \right) - \frac{1}{R_f} \right]^{-1} \frac{V_{in}}{R_1}$$

$$= -9.99 V_{in} = -49.99 \sin 3t \text{ mV}$$

① INVERTING AMPLIFIER

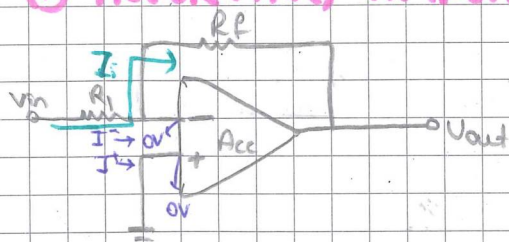


$$V_{out} = V_{in} \left(-\frac{R_f}{R_1} \right)$$

$$V^+ = V^- = 0$$

$$I^+ = I^- = 0$$

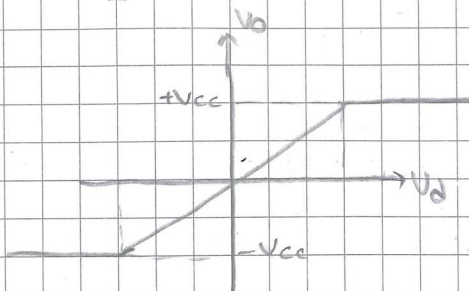
$$\frac{V_i - 0}{R_1} = \frac{0 - V_{out}}{R_f}$$



→ V_{cc}^+ / V_{cc}^- are the supplying voltages for work the Op-Amp.

→ There would be a phase difference with 180° .


③ NON-INVERTING AMPLIFIER

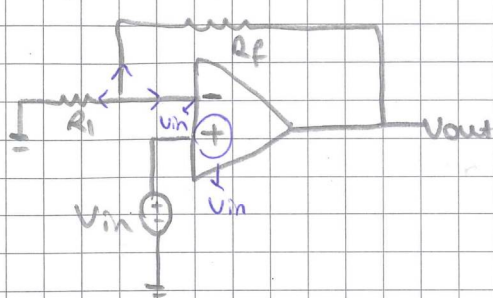

$$V_{out} = \left(\frac{R_f}{R_1} + 1 \right) V_{in}$$

$$\frac{V_{in} - 0}{R_1} + \frac{V_{in} - V_o}{R_f} = 0$$

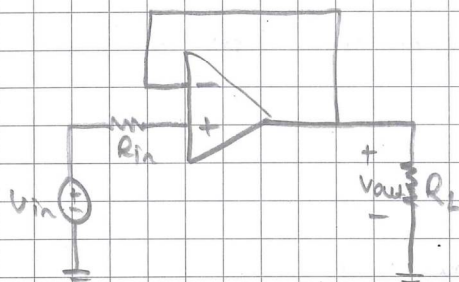④ VOLTAGE FOLLOWER (unity gain amplifier)




$$R_1 \rightarrow \infty, R_f \rightarrow 0, V_{out} = V_{in}$$

→ The input impedance of the Op-amp is very high, giving effective isolation at the output from the signal source.

Modulation → $M(t) + C(t) = S(t)$
 message signal carrier signal
 } we use in filters

⑤ SUMMING AMPLIFIER

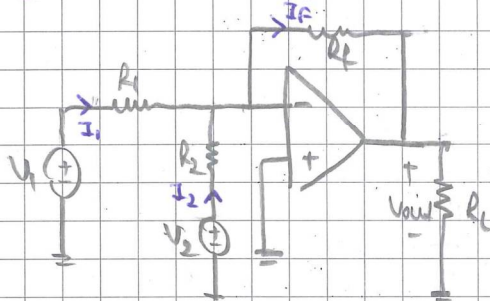


$$I_1 + I_2 = I_f$$

$$V_{out} = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 \right)$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{0 - V_o}{R_f}$$

⑥ DIFFERENCE AMPLIFIER

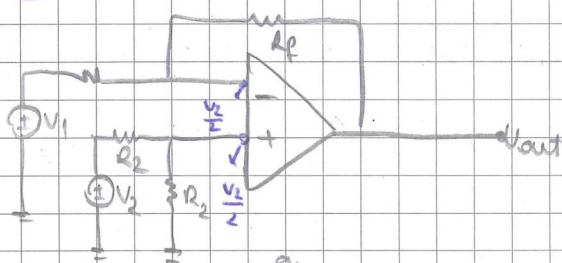


$$V_{out} = V_2 - V_1$$

$$\frac{V_1 - V_2}{2} = \frac{V_2 - V_o}{R_1}$$

$$V^+ = \frac{V_2 R_2}{2R_2} \Rightarrow V^+ = V^- = \frac{V_2}{2}$$

Ex:

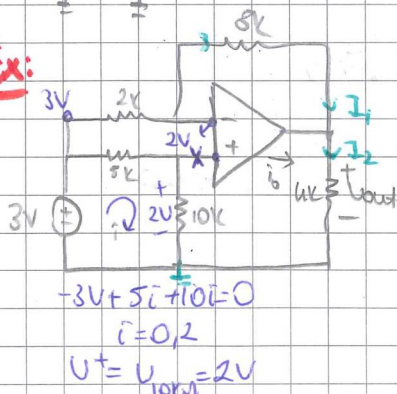

Find the i_o , V_{out} .

$$V^+ = V^- = 2V$$

$$KCL \rightarrow i_o + I_1 = I_2$$

$$\frac{3V - 2V}{2k} = \frac{2V - V_{out}}{8k}$$

$$i_o = \frac{-2V}{2k} = \frac{2V - (-2V)}{8k}$$


$$i_o = -1mA$$

$$V_{out} = -2V$$

* Cascading Op-Amps *

Op-Amps can be combined in stages to create the desired relationship between the outputs and inputs.

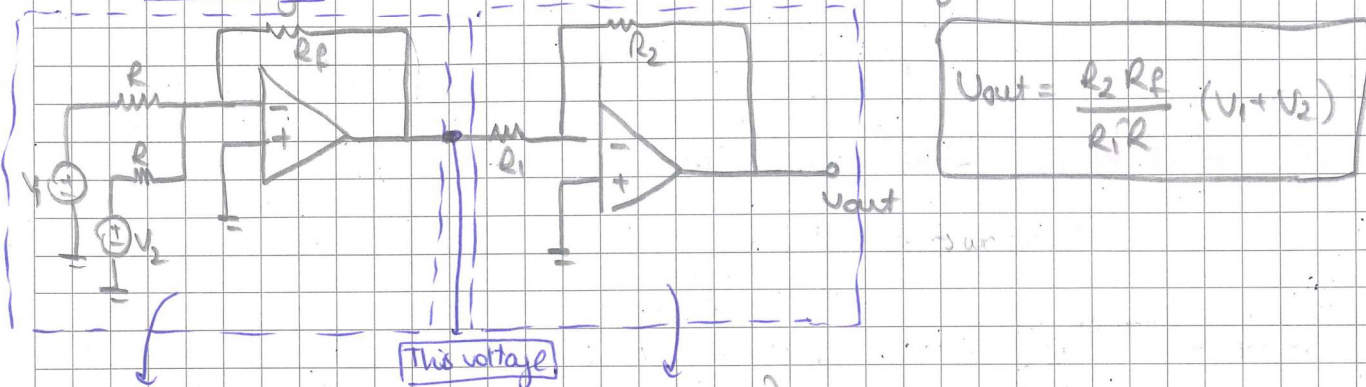→ The voltage is not affected by the circuit on the right.



$$V_{out} = \frac{R_2 R_f}{R_1 R} (V_1 + V_2)$$

$$V_{out} = \frac{R_f}{R} (V_1 + V_2)$$


(summing)

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

(inverting)

we can think like that
we multiply two gains.

Ex:

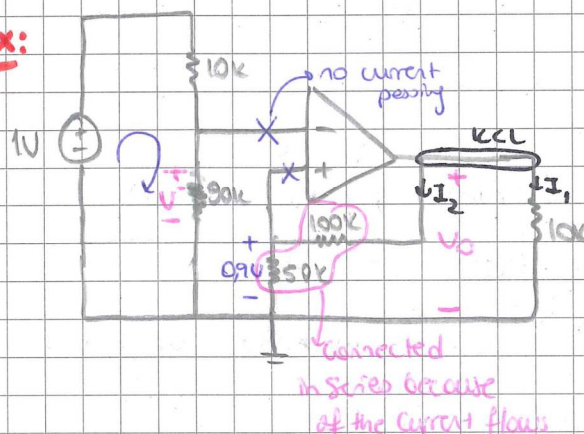

find the I_0 and V_0 .

we need to find $V^+ = V^- \rightarrow$ KCL @ node

$$V^- = 1V \cdot \frac{90k}{100k} = 0.9V$$

$$0.9V = V_0 \cdot \frac{50k}{150k}$$


$$V_0 = 2.7V$$

$$I_0 = I_1 + I_2$$

$$= \frac{2.7V}{10k} + \frac{2.7V}{150k}$$

$$I_0 = 0.28mA$$

Ex:

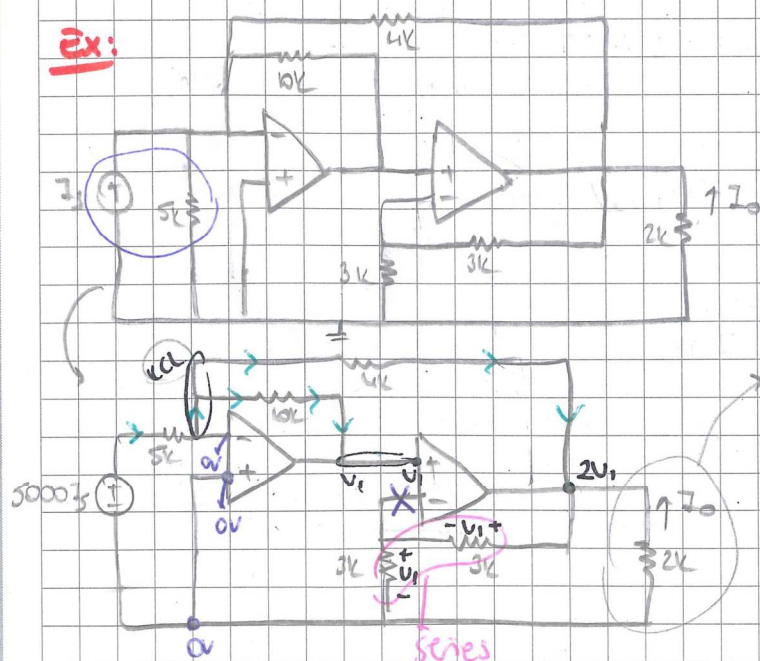

Find the current gain I_0/I_s .

KCL @ node

$$\frac{5000I_s - 0}{5k} = \frac{0 - V_1}{10k} + \frac{0 - 2V_1}{4k}$$


$$I_s = \frac{-12V_1}{20000}$$

$$I_0 = \frac{0 - 2V_1}{2k} \rightarrow I_0 = \frac{-2V_1}{2000}$$

$$\frac{I_0}{I_s} = \frac{-2V_1/2000}{-12V_1/20000} = \frac{5}{3}$$

Ex: Using only 2 op-amps, design a circuit to solve;
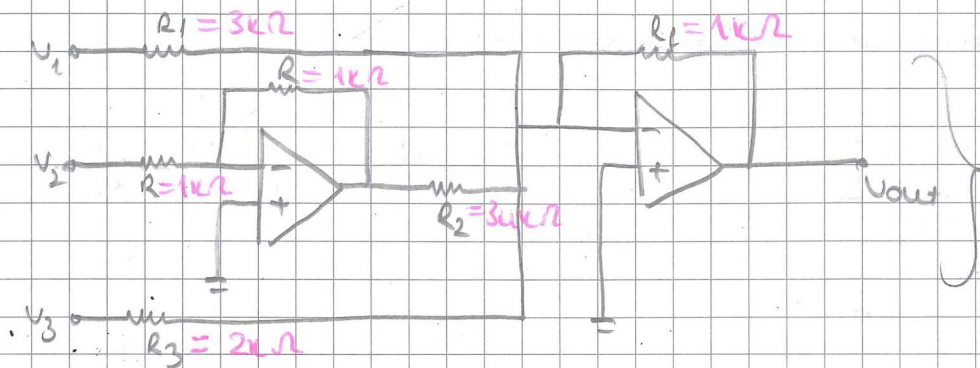
$$-V_{out} = \frac{V_1 - V_2}{3} + \frac{V_3}{2} \rightarrow -V_{out} = \frac{V_1}{3} - \frac{V_2}{3} + \frac{V_3}{2}$$



cascaded circuits

better
so,


$$R_1 = 3k\Omega$$

$$R_2 = 3k\Omega$$

$$R_3 = 2k\Omega$$

$$R = R = R_f = 1k\Omega$$

for solve 1st op-amp;

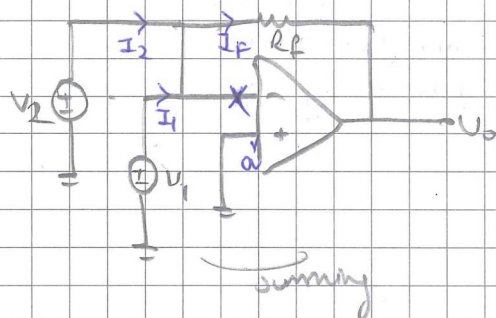


$$I_1 = I_2 = I_f$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{-V_0}{R_f}$$

$$-V_0 = \frac{R_f V_1}{R_1} + \frac{R_f V_2}{R_2}$$

summing

Ex:

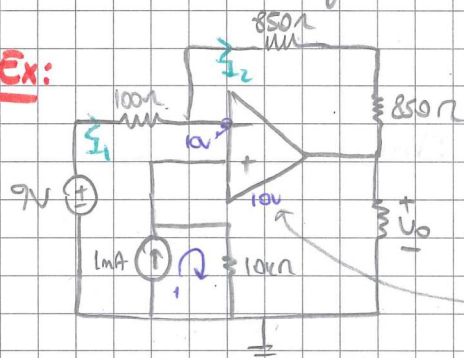

Determine the value of V_0 .


$$V^- = V^+, I^- = I^+ = 0$$

$$V^- = 1mA \times 10k\Omega = 10V \rightarrow \text{come from loop 1}$$

$$V^- = V^+ = 10V$$

$$I_1 = I_2 \rightarrow \frac{9V - 10V}{100k\Omega} = \frac{10V - V_0}{100k\Omega} \Rightarrow \underline{V_0 = 27V}$$

Ex:

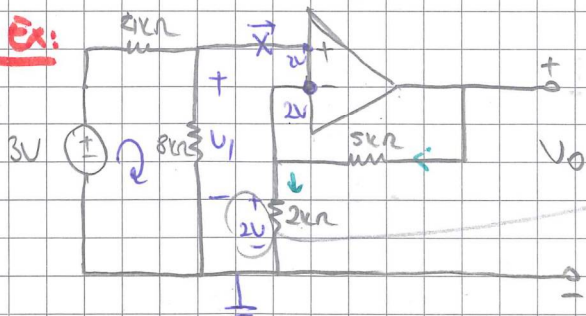

Calculate the V_0 .

$$V^- = V^+$$

$$V_1 = (3V) \cdot \frac{8k\Omega}{12k\Omega} = 2V$$

$$I^- = I^+ = 0$$

$$2V = V_0 \cdot \frac{2k\Omega}{7k\Omega} \Rightarrow \underline{V_0 = 7V}$$

* pico 10^{-12}
 nano 10^{-9} (n)
 micro 10^{-6} (H)


* ENERGY STORAGE ELEMENTS *

*** CAPACITORS:** A capacitor is a linear circuit element which stores energy in the electric field in the space between two conducting bodies occupied by a material with permittivity ϵ .

$$C = \epsilon \cdot \frac{A}{d}$$

$$C = \frac{Q}{V}$$

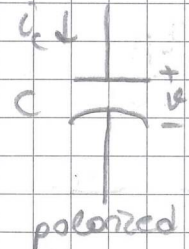$\epsilon = \epsilon_r \cdot \epsilon_0 \rightarrow$ vacuum permittivity.
 $\downarrow$
 relative dielectric constant



$$V(t) = \frac{1}{C} \left[\int_{t_0}^t i(t) dt + V(t_0) \right]$$

$$i_C(t) = C \cdot \frac{dV_C(t)}{dt}$$

$$P = CV \frac{dV}{dt}$$

$$W = \frac{1}{2} CV^2$$

charged: by applying current to its terminals

discharged: when it provides current from its terminals.


* When we give on the capacitor

! $\rightarrow$ DC voltage: 0 current (blocked) $\rightarrow$ acts like an open circuit


$\rightarrow$ AC voltage: $i_C(t) = C \cdot \frac{dV_C(t)}{dt}$

Current leads voltage, voltage lags current.

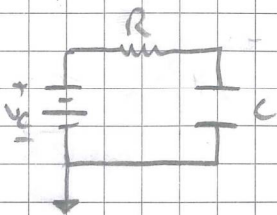
* Real capacitor: does dissipate energy due to leakage of charge through its insulator.



$\tau = RC$
 time constant

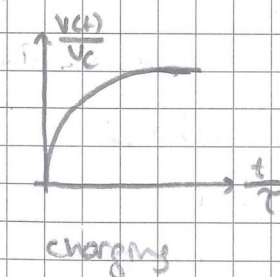


$$V(t) = V_C (1 - e^{-t/\tau})$$

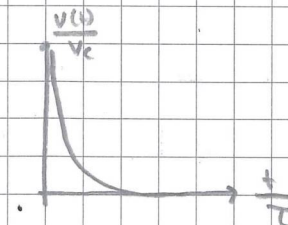

$$V(t) = V_C e^{-t/\tau}$$

Ex:

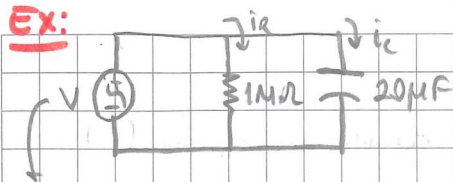

$$100 \sin 2\pi t$$

$$i_c = C \frac{dV}{dt}$$

$$= 20 \mu F \frac{d}{dt} (100 \sin(2\pi t))$$

$$= 4\pi \cos(2\pi t) \text{ mA}$$

$$i_c = \frac{V}{R} = \frac{100 \sin(2\pi t)}{10^6} = 0.1 \sin(2\pi t) \text{ mA}$$


Find the max energy stored in capacitor, at $0 < t < 0.5$

$$2\pi F \rightarrow 2 \cdot 0.5 = 1 \quad F = 1$$

$$W_c = \frac{1}{2} CV^2$$

$$= \frac{1}{2} (20 \mu F) ((100 \sin(2\pi t)) V)^2$$

$$= 100 \cdot 5m^2 (2\pi t) \text{ MJ}$$

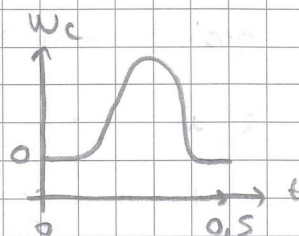

* the current of capacitors and voltage of capacitors has 90° of phase shift.

* source current and capacitor current has 180° of phase shift.

→ Capacitors in Parallel: $i_{in} = i_1 + i_2 + i_3 \dots$ $C_{eq} = C_1 + C_2 + C_3 \dots = \sum_{p=1}^P C_p$

$$i_{in} = C_{eq} \frac{dV}{dt}$$

$$V = V_1 = V_2 = V_3 \dots$$


→ Capacitors in Series: $V_{in} = V_1 + V_2 + V_3 \dots$ $C_{eq} = \left[\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \dots \right]^{-1} = \left[\sum_{s=1}^S \frac{1}{C_s} \right]^{-1}$

$$V_{in} = \frac{1}{C_{eq}} \int_0^t i_c dt$$

* The voltage across a capacitor must be a continuous function; the current flowing across a capacitor can be discontinuous.

* * An ideal capacitor act like an open circuits when a DC voltage or current has been applied for at least 5τ .


Ex:

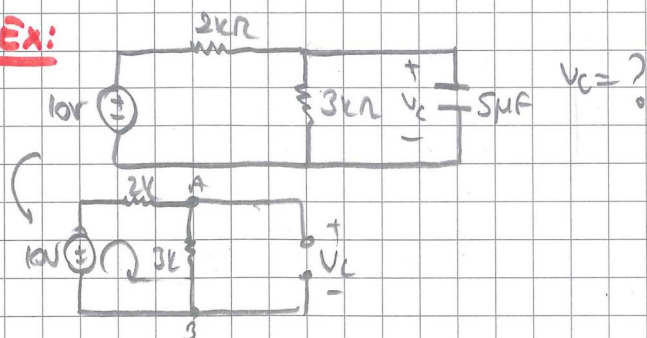

$$V_{AB} = 10 \cdot \frac{3}{5} = 6V = V_c$$

$$V_c = 6V$$


Ex:

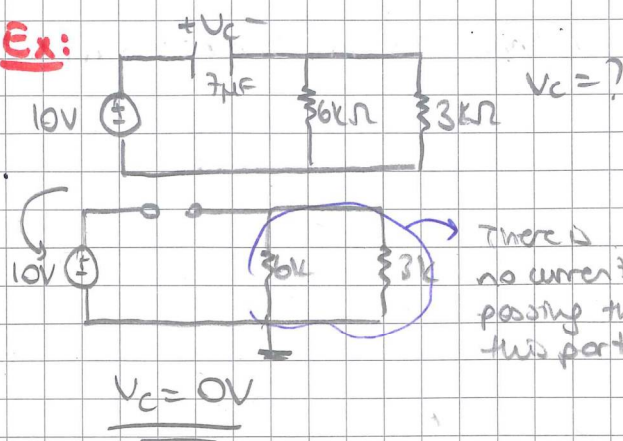

There is no current passing through this part.

$$V_c = 0V$$

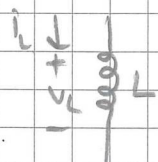*** INDUCTORS:** A component in an electric or electronic circuit which possesses inductance, also called a coil, choke or reactor is a passive two-terminal electrical component



$$i(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

$$v_L = L \frac{di(t)}{dt}$$

$$L = \mu \cdot \frac{N^2 A}{l}$$

$$W = \frac{1}{2} L i^2$$

* if we have decrease current $\rightarrow$ (-) voltage

constant current $\rightarrow$ 0 voltage

increase current $\rightarrow$ (+) voltage

* When we give an inductor

$\nabla \rightarrow$ DC voltage: acts like a short circuit

$\rightarrow$ AC voltage: $i(t) = \frac{1}{L} \int v(t) dt$

voltage "leads" current, current "lags" voltage.

* current must be continuous.


$\rightarrow$ Inductors in Parallel: $i_n = i_1 + i_2 + i_3 + \dots$ $L_{eq} = \left[\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots \right]^{-1} = \left[\sum_{p=1}^n \frac{1}{L_p} \right]^{-1}$

$$i_n = \frac{1}{L_{eq}} \int v(t) dt$$

$\rightarrow$ Inductors in Series: $V_{in} = V_1 + V_2 + V_3 + \dots$ $L_{eq} = L_1 + L_2 + L_3 + \dots = \sum_{p=1}^n L_p$

$$V_{in} = L_{eq} \frac{di(t)}{dt}$$

Ex!

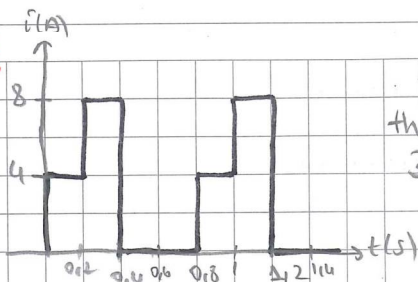

The current flowing through 33 mF capacitor is shown. Assume the passive sign convention, Compute the voltage at 300 ms , 600 ms and 1 s .

$$V_C(t) = \frac{1}{C} \int I_C(t) dt + V_C(t_0)$$

$$V_c(0.2s) = \frac{4.02}{33mf} = 24.2f$$

$$V_c(0,0) = \text{constant @ } 72.7V = 72.7V$$


$$V_c(0,45) = \frac{8 \cdot 0,2}{32\text{mF}} + 24,2 = 24,2 = 72,7\text{V}$$

$$V_C(1s) = \frac{4 \cdot 0,2}{33 \text{ mF}} + 72,7 \text{ V} = 97 \text{ V}$$

$$V_c(0,3s) = \frac{1}{2} [V(0,2) + V(0,4)] = \underline{\underline{48.5V}} \quad V_c(1,2) = \frac{8.012}{33mF} + 97V = 145.5V$$


$$V_c(1,1) = \frac{1}{2} [V(1,1) + V(1,2)] = \underline{\underline{121.2 \text{ V}}}$$

Ex:

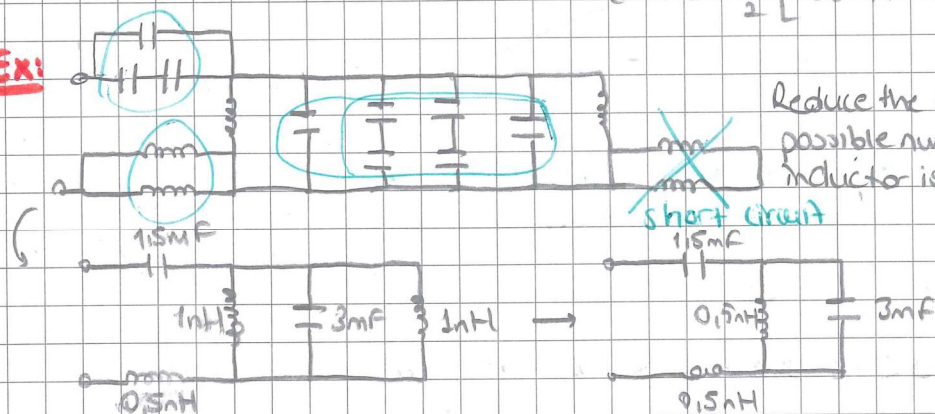

Reduce the network to the smallest possible number of components if each inductor is 1mH and capacitor is 1mF .

Ex:

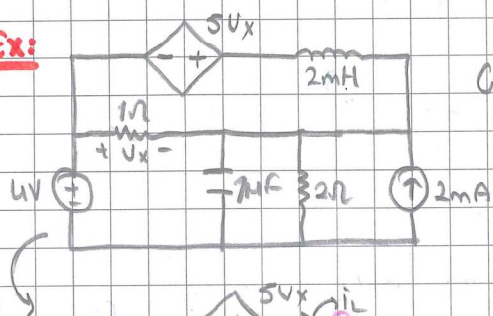

Calculate the energy stored in each energy storage element.

@ 1st mesh

$$-5V_x + 1(i_1 - i_2) = 0$$
$$6i_1 - 6i_2 = 0$$
$$i_1 = i_2$$

(a) 2nd mesh
 $-u + V_x + 2(i_2 - i_3) = 0$
 $-i_1 + 3i_2 = u - \underbrace{4 \cdot 10^{-3}}_{\text{can be negligible}}$

$$i_1 \cong 2A, i_2 \cong 2A$$

$$V_L = 2\Omega \times 2A = 4V$$


$$W_c = \frac{C V_c^2}{2}$$

$$= \frac{(1H)(4V)^2}{2} = \underline{\underline{8mJ}}$$

$$W_L = \frac{L \cdot I^2}{2} = \frac{(2m)(2A)^2}{2} = \underline{\underline{4mJ}}$$

Capacitor $\rightarrow$ open c.
Inductor $\rightarrow$ short c.


Ex:

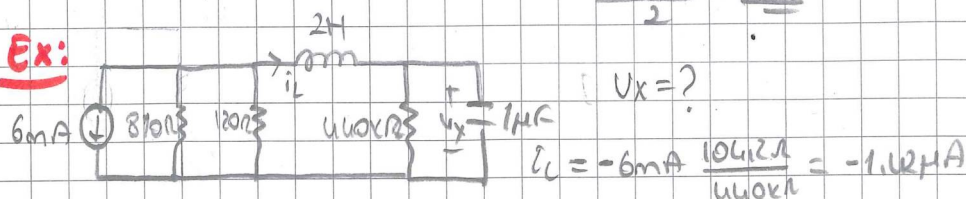

$$R_{eq} = \left[\frac{1}{810} + \frac{1}{120} + \frac{1}{40000} \right]^{-1} \quad V_x = i_L \times 400k\Omega = \underline{\underline{-624.8mV}}$$

$$= 104.2\Omega$$

Ex:

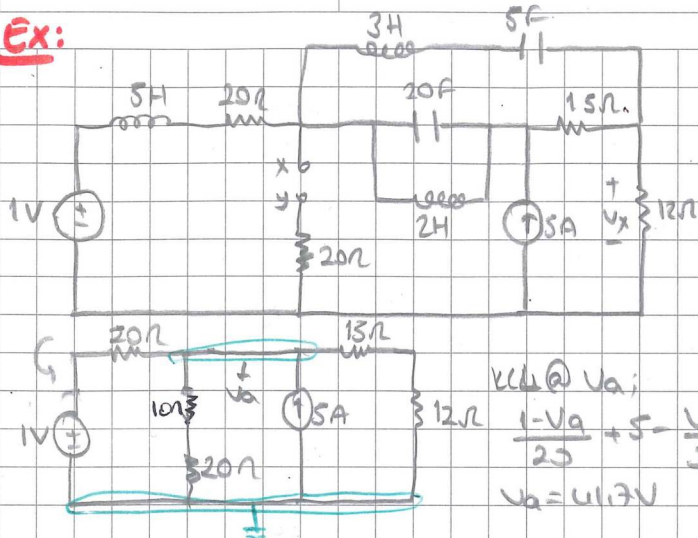

a) $x-y \rightarrow 10\Omega$ and determine V_x

b) $x-y \rightarrow 1H$ and determine V_x

c) $x-y \rightarrow 1F$ and determine V_x

$$b \rightarrow \frac{1-V_a}{20} + 5 - \frac{V_a}{20} - \frac{V_a}{12} = 0$$

$$V_a = 36.85V \quad V_x = \frac{V_a}{20} \cdot 12 = \underline{\underline{16.4V}}$$

KCL @ V_a :

$$\frac{1-V_a}{20} + 5 - \frac{V_a}{20} - \frac{V_a}{12} = 0$$

$$V_a = 41.7V$$

$$a \rightarrow V_x = \frac{V_a}{20} \cdot 12 = \underline{\underline{18.53V}}$$


$$c \rightarrow -5 + \frac{V_a}{20} + \frac{(V_a-1)}{20} = 0$$

$$V_a = 58.02V$$

$$V_x = \underline{\underline{25.8V}}$$

* 1st ORDER Op-AMP CIRCUITS *


* DIFFERENTIATOR:

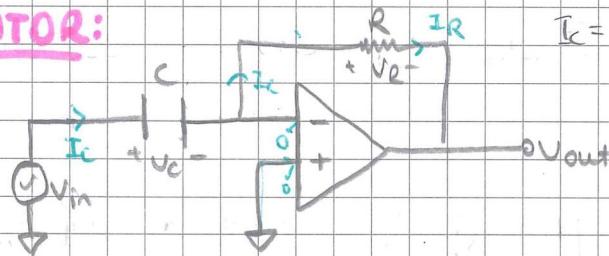

$$I_R = C \frac{dV_{in}}{dt} = \frac{0 - V_{out}}{R}$$

$$V_{out} = -RC \frac{dV_{in}}{dt}$$

Ex:

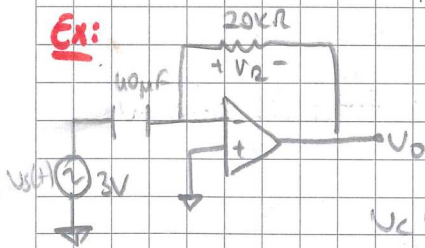

Suppose that $V_s(t) = 3V u(t-5s)$.


→ initial condition of $V_c = 0V$ when $t < 5s$,

→ final condition of $V_c = 3V$ when $t > 5s$,

$$V_c(t) = V_{c,ini} + (V_{c,final} - V_{c,ini}) e^{-(t-t_0)/\tau} \quad \tau = RC = 0.8$$

$$= 0 + (3V - 0V) e^{-(t-5s)/0.8} = \underline{\underline{3Ve^{-(t-5s)/0.8}}}$$

* INTEGRATOR:

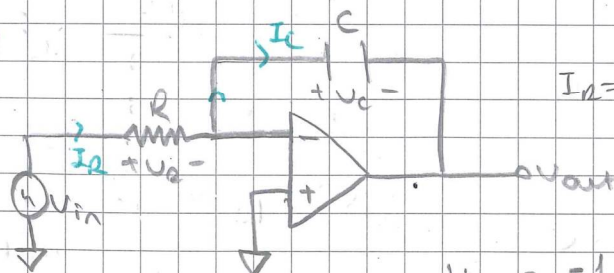

$$I_R = \frac{V_{in}}{R}$$

$$I_C = C \frac{dV_{in}}{dt}$$

$$V_{out} = -\frac{1}{RC} \int_{t_1}^{t_2} V_{in}(t) dt + V_o(t)$$

! differentiator → if our input voltage is sinusoid, output voltage lags input voltage.


integrator → if our input voltage is sinusoid, output voltage leads input voltage.

the output must be continuous.

* RC AND RL CIRCUITS *

* RC CIRCUITS *

① Natural Response:

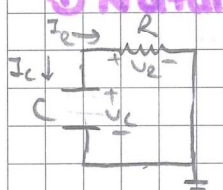

$$V_C = V_R \quad V_C(t) = V_0 e^{-t/\tau}$$

$$P_R(t) = \frac{V_0^2}{R} e^{-2t/\tau}$$

$$I_R(t) = -I_C(t) = \frac{V_0}{R} e^{-t/\tau} \quad W_C(t) = \frac{C V_0^2}{2} [1 - e^{-2t/\tau}]$$


$$\left. \begin{aligned} V_C &= A e^{st} \\ V_R &= \frac{1}{RC} A e^{st} \end{aligned} \right\} s = -\frac{1}{RC}$$

* @ $t=0$, the initial voltage $V(0) = V_0$ across the capacitor, capacitor acts like an open circuit.

* Capacitor stored energy at $t=0s$, released energy at $t>0s$.

* time constant $\tau = RC$


Ex:

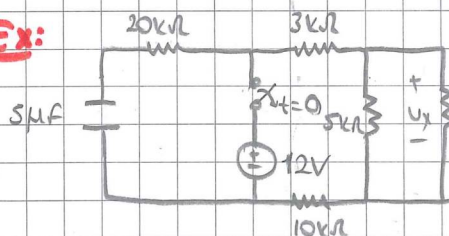

The switch above the 12V source in the circuit has been closed since just after the wheel was invented. It is finally thrown open at $t=0$.

a) compute the circuit's time constant.

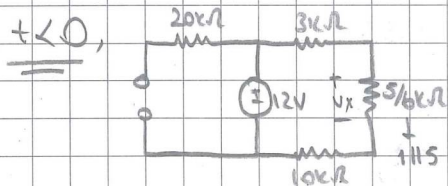b) Obtain an expression for $V_C(t)$ for $t>0$, calculate the energy stored in the capacitor 170ms after switch opened.




$$V_C(0^-) = 12V$$

$$V_x(0^-) = 12 \cdot \frac{5/6k\Omega}{(\frac{5}{6} + 3 + 10)k\Omega} = 723mV$$

$$\text{final condition} \rightarrow \begin{aligned} V_C(\infty) &= 0 \\ V_x(\infty) &= 0 \end{aligned}$$
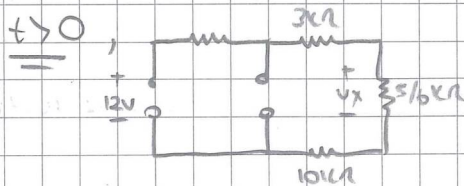
$$\begin{aligned} a) \tau &= R_{eq} C = (33.8k\Omega)(5\mu F) \\ &= \underline{\underline{169ms}} \end{aligned}$$




$$V_x(0^+) = 12 \cdot \frac{5/6k\Omega}{(\frac{5}{6} + 3 + 10 + 20)k\Omega} = 296mV$$

$$\begin{aligned} b) V_x(t) &= 296 e^{-5.9t} mV \\ V_C(t) &= 12 e^{-5.9t} V \end{aligned}$$

$$W_C = \frac{1}{2} C V^2 = \underline{\underline{360 e^{-11.8t} \mu J}}$$

③ Driven RC circuits:

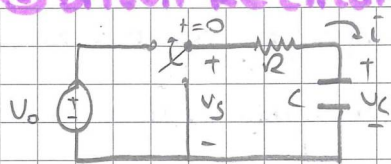

$V_S = 0, V_C(0^-) = 0 \rightarrow$ just before $t=0$


$V_S = V_0, V_C(0^+) = 0 \rightarrow$ just after $t=0$

* capacitor acts like an open circuit $\rightarrow V_C(\infty) = V_0$

$$* V_C(t) = V_C(\infty) + [V_C(0) - V_C(\infty)] e^{-t/\tau} \rightarrow V_C(t) = V_0(1 - e^{-t/\tau})$$

$$* I_C(t) = \frac{C}{\tau} [V_C(\infty) - V_C(0)] e^{-t/\tau} \quad \tau = RC$$


Ex:

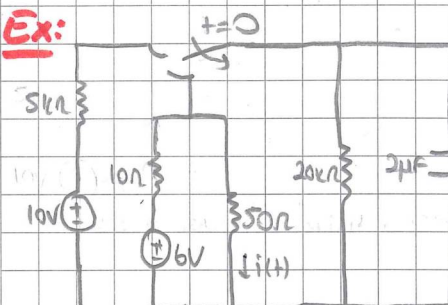

a) Obtain expression for $i(t)$ and $V_C(t)$ valid for all values of t .

b) Determine the energy remaining the capacitor at $t = 33 \mu s$.

$t < 0,$

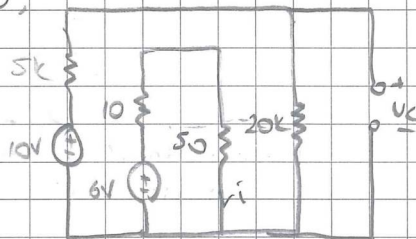

$$V_C(0^-) = 10 \cdot \frac{20k}{5k+10k} = 8V$$

$$* V_C(0^+) = V_C(0^-) \quad i(0^+) = \frac{8}{50} = 160mA$$

$$i(0) = \frac{6}{(10+50)k} = 100mA$$

$$a) R_{eq} = 10 || 50 || 20k = 8.3k$$

$$\tau = RC = 16.7 \mu s$$

$t \rightarrow \infty,$



$$V_C(\infty) = 6 \cdot \frac{50 || 20k}{10+50 || 20k} = 5V$$


$$b) V_C(33 \mu s) = 5 + 3e^{-60000(33 \cdot 10^{-6})} = 5.41V$$

$$W_C = \frac{1}{2} (2\mu)(5.41)^2 = 29.3 \mu J$$

$$i(\infty) = \frac{6}{60} = 100mA$$

* RL CIRCUITS:

① Natural Response:

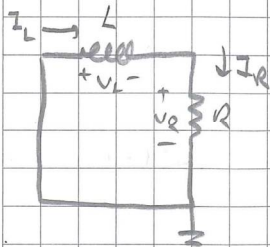

$$i_L(t) = I_0 e^{-t/\tau}$$

$$P_R(t) = R I_0^2 e^{-2t/\tau}$$


$$v_R(t) = -v_L(t) = R I_0 e^{-t/\tau} \quad w_L(t) = \frac{L I_0^2}{2} [1 - e^{-2t/\tau}]$$

* @ $t=0$ the initial current $i(0) = I_0$ through the inductor. Inductor acts like a short circuit

* Stored energy in inductor at $t=0$, released at $t>0$.



* time constant $\tau = \frac{L}{R}$

Ex:

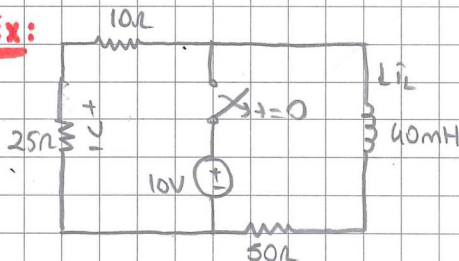

a) Obtain expressions for i_L and V which are valid for all $t \geq 0$.

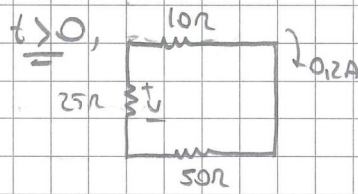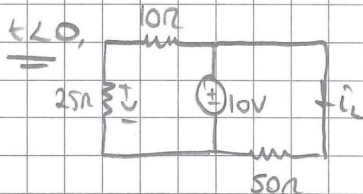b) Calculate $i_L(t)$ and $V(t)$ at $t = 470 \mu s$.



$$\tau = \frac{L}{R_{eq}} \quad R_{eq} = 85 \Omega$$

$$= \frac{40m}{85}$$

$$\tau = 471 \mu s$$

$$V(0^-) = 10 \cdot \frac{25}{35} = 7.14V$$

$$V(0^+) = -(25)(0.2) = -5V$$

$$i_L(0^-) = \frac{10}{50} = 0.2A$$

$$i_L(0^+) = i_L(0^-) = 0.2A$$

final condition $\rightarrow V(\infty) = 0, i_L(\infty) = 0$

a) $V(t) = -5e^{-2125t} V$


b) at $t = 470 \mu s$

$$i_L(t) = 200e^{-2125t} mA$$

$$V = -5/e = -1.8uV$$

$$i_L = 200/e = 74 mA$$

② Driven RL Circuits:

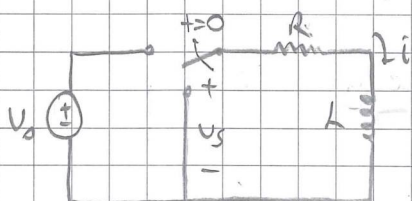

$V_s = 0, i_L(0^-) = 0 \rightarrow$ just before $t=0$

$V_s = V_0, i_L(0^+) = 0 \rightarrow$ just after $t=0$


* inductor acts like a short circuit.

$$* i_L(t) = I_L(\infty) + [I_L(0) - I_L(\infty)] e^{-t/\tau}$$


$$\tau = \frac{L}{R}$$

$$* v_L(t) = \frac{L}{\tau} [I_L(\infty) - I_L(0)] e^{-t/\tau}$$

Ex:

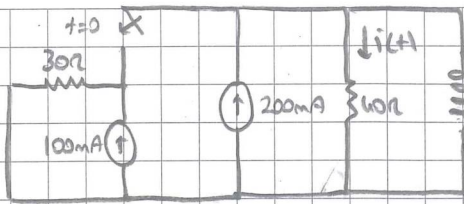

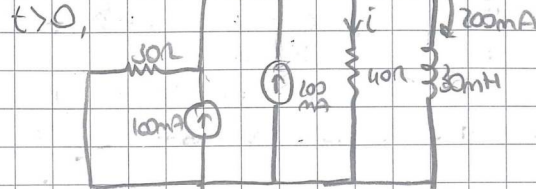Obtain an expression for $i(t)$ as labeled in the circuit, and determine the power dissipated in the 40Ω resistor at $t = 2.5\text{ms}$.



$$t \rightarrow \infty, i(\infty) = 0$$

$$\tau = \frac{L}{R_{eq}} = 1.75\text{ms}$$

$$i(0^-) = 0$$

$$i_L(0^-) = 200\text{mA}$$

$$i_L(0^+) = i_L(0^-) = 200\text{mA}$$

$$i(0^+) = 100 \cdot \frac{1/40}{1/40 + 1/30} = 42.9\text{mA}$$

$$i(t) = 42.9 e^{-t/1.75\text{ms}} = 42.9 e^{-571t} \text{ mA}$$

$$P = i^2 R$$


$$= [0.0429 e^{-571 \cdot 2.5\text{ms}}]^2 \cdot 40$$

$$= \underline{\underline{4.2\text{mW}}}$$

* RLC CIRCUITS *


→ A second order circuit is characterized by a second-order differential equation.

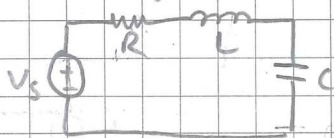→ The circuit will contain at least one resistor and the equivalent of two energy storage elements.



→ We use RLC circuits in analog filters.

* Parallel RLC Circuits:

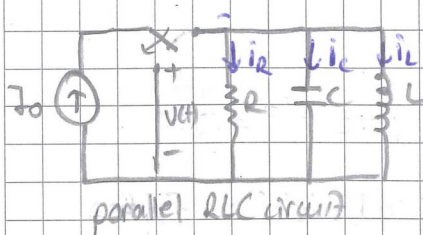

$$-I_0 + i_R + i_L + i_C = 0$$

$$I_0 + \frac{v(t)}{R} + \frac{1}{L} \int v(t) dt + C \frac{dv(t)}{dt} = 0$$

$$\frac{d^2}{dt^2} v(t) + 2\alpha \frac{d}{dt} v(t) + \omega_0^2 v(t) = 0$$


damping coefficient

resonant frequency

$$\alpha = \frac{1}{2RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

* Series RLC Circuits:

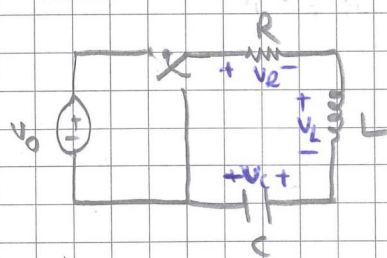

$$-V_0 + V_R(t) + V_L(t) + V_C(t) = 0$$

$$\text{derivative} \rightarrow -V_0 + R i(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int_{t_0}^t i(t) dt = 0$$

$$\frac{d^2}{dt^2} i(t) + 2\alpha \frac{d}{dt} i(t) + \omega_0^2 i(t) = 0$$

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

* General Solution: $x(t) = x_1 e^{s_1 t} + x_2 e^{s_2 t} + x_3$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$x(0^+) = x_1 + x_2 + x_3 \quad x(\infty) = x_3$$

$$\frac{dx}{dt}(0^+) = s_1 x_1 + s_2 x_2$$

* $\alpha > \omega_0 \rightarrow$ over-damped

$$\rightarrow x(t) = x_1 e^{s_1 t} + x_2 e^{s_2 t} + x_3$$

* $\alpha = \omega_0 \rightarrow$ critically-damped

$$\rightarrow x(t) = e^{-\alpha t} (x_1 + x_2) + x_3$$

* $\alpha < \omega_0 \rightarrow$ under-damped

$$\rightarrow x(t) = e^{-\alpha t} [x_1 \cos(\omega_d t) + x_2 \sin(\omega_d t)] + x_3$$

oscillation occurs

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} \quad (\text{natural resonant frequency})$$



Ex:

300n

Find an expression for $V_C(t)$ valid for $t > 0$ in the circuit.

150V

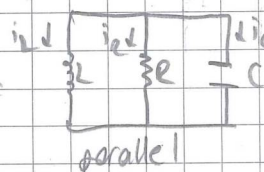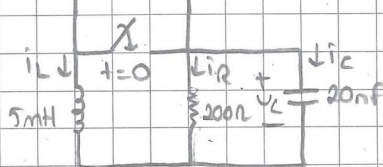* ① $t > 0$, we need to determine our RLC circuit type and find α, ω_0 .



$$\alpha = \frac{1}{2C} = \frac{1}{2 \cdot 200 \cdot 10^{-9}} = 0,125 \cdot 10^6 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 10^6 \text{ rad s}^{-1}$$


} $\alpha > \omega_0$ overdamped and no oscillation.

* ② We need to obtain $t = \infty$

$$V_C(t) = V_1 e^{s_1 t} + V_2 e^{s_2 t} + V_3$$

$$V_3(\infty) = 0 \rightarrow \text{no voltage on capacitor.}$$

* ④ $V_C(0^+), t < 0$

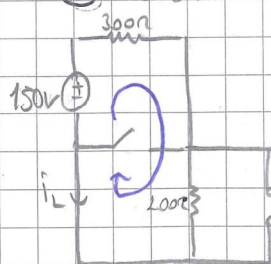

$$i_L(0^-) = -i_C(0^-)$$

$$i_L(0^-) = \frac{150}{200} = 0,3 \text{ A}$$

$$i_L(0^-) = i_C(0^-) = -0,3 \text{ A}$$

$$V_C(0^-) = V_C(0^+) = 200 \text{ nF} \times 0,3 \text{ A} = 60 \text{ V}$$

* ③ $V_C(0^+) = V_C(0^-)$, obtain $t = 0^+$

$$V_1 e^0 + V_2 e^0 + 0 = V_C(0^+)$$

$$V_1 + V_2 = V_C(0^+)$$

goes on

* ⑤ when we find $V_C(t)$ then,

$$V_C(t) = V_1 e^{s_1 t} + V_2 e^{s_2 t}$$

$$60 = V_1 + V_2 \quad (\text{our 1st eq})$$

* ⑥ if we take derivative

$$\frac{dV_C(t)}{dt} = V_1 s_1 e^{s_1 t} + V_2 s_2 e^{s_2 t}$$

$$\text{at } t=0^+ \rightarrow \frac{dV_C(0^+)}{dt} = \frac{I_C(0^+)}{C}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -50000$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -200000$$

* ⑧ if we solve 1st and 2nd equation,

$$\begin{cases} 60 = V_1 + V_2 \\ 0 = V_1 + 4V_2 \end{cases} \Rightarrow \underline{V_1 = 80V}, \underline{V_2 = -20V}$$

$$V_C(t) = 80 e^{-50000t} - 20 e^{-200000t} \quad \text{at } t > 0$$

* ⑦ we need to find $I_C(t)$, use KCL @ upper node at $t > 0^+$

$$i_C(0^+) + i_L(0^+) + i_R(0^+) = 0$$

$$i_C(0^+) = -i_L(0^+) - i_R(0^+) = -(-0,3) - \left(\frac{V_R(0^+)}{R}\right) \rightarrow V_R(0^+) = V_C(0^+)$$

$$= 0,3 - \frac{60}{200} = \underline{0A}$$

when we put $I_C(0^+)$,


$$\Rightarrow \frac{dV_C(0^+)}{dt} = 0 \rightarrow \frac{dV_C(0^+)}{dt} = V_1 s_1 e^{s_1 t} + V_2 s_2 e^{s_2 t} \rightarrow 0$$

$$\frac{dV_C(0^+)}{dt} = V_1 s_1 + V_2 s_2$$

$$0 = V_1(-50000) + V_2(-200000)$$


$$\underline{0 = V_1 + 4V_2} \quad (2^{\text{nd}} \text{ eq})$$

Ex:

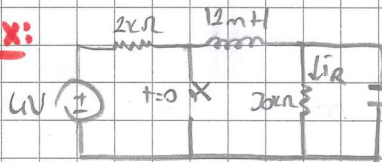

Find the i_R for all time intervals

* ① $t > 0$,

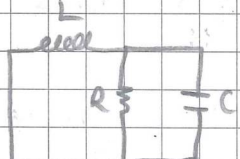

$$\alpha = \frac{1}{2RC} = 8,33 \cdot 10^6 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 6,45 \cdot 10^6 \text{ rad/s}$$

$$i_R(t) = \underbrace{I_1 e^{s_1 t} + I_2 e^{s_2 t}}_{\text{transient}} + \underbrace{I_3}_{\text{steady}}$$


$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -3,06 \cdot 10^6 \text{ s}^{-1}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -13,6 \cdot 10^6 \text{ s}^{-1}$$

$I_3 = 0 \rightarrow$ we have no energy

$$i_R(t) = I_1 e^{s_1 t} + I_2 e^{s_2 t}$$

* ② $t < 0$

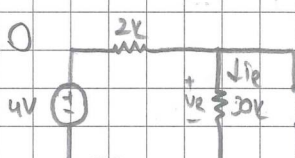

$$i_L(0^-) = i_R(0^-) = \frac{4V}{2k\Omega} = 125 \text{ mA}$$


$$V_C(0^-) = V_C(0^+) = i_R(0^-) \times 30k\Omega = 3,75V$$

$$i_L(0^+) = i_L(0^-) = 125 \text{ mA}$$

$$V_C(0^+) = V_C(0^-) = 3,75V$$

$$i_R(0^+) = \frac{V_C(0^+)}{30k\Omega} = 125 \text{ mA}$$

* ③ $t = 0^+$

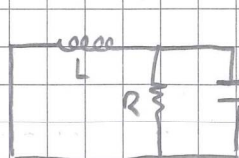

$$V_C = L \frac{di_L}{dt} \quad V_R = V_C$$

$$\frac{I_C(0^+)}{RC} = \frac{di_R}{dt}$$

$$I_1 e^{s_1 t} + I_2 e^{s_2 t} + 0 = i_R(t)$$

$$\underline{I_1 + I_2 = 125 \cdot 10^{-6} \text{ A}} \quad \text{①}$$

KCL @ upper node

$$i_L(0^+) = i_R(0^+) + i_C(0^+) = 0$$

$$\frac{di_R}{dt} = 0$$

$$I_1 s_1 + I_2 s_2 = 0$$

$$-3,06 \cdot 10^6 I_1 + 13,6 \cdot 10^6 I_2 = 0 \quad (2)$$


* (4) if we solve together 1 & 2

$$I_1 = 161,3 \mu A, \quad I_2 = -36,3 \mu A$$

$$I_L(t) = (161,3 e^{-3,06 \cdot 10^6 t} - 36,3 e^{-13,6 \cdot 10^6 t}) \mu A, \quad t > 0$$

$$I_L(t) = 125 \mu A, \quad t < 0$$

Ex:

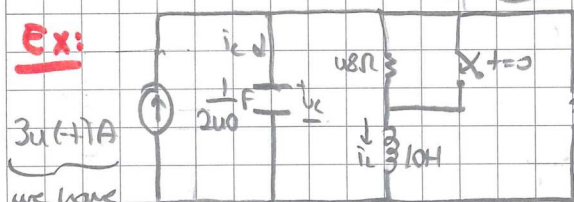

we have a source before $t=0$

determine $i_L(t)$ for the circuit and plot the wave form of your solution.


* (2) $t < 0$



$$i_L(0^-) = 3 A \cdot \frac{100 \Omega}{100 \Omega} = 2,02 A$$

$$V_C(0^-) = 48 \cdot 2,02 = 97,3 V$$

* (1) $t > 0$

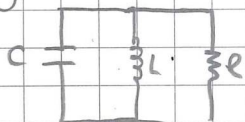

$$\alpha = 1/2RC = 1,25$$

$$\omega_0 = 1/\sqrt{LC} = 4,9 \text{ rad/s}$$

$\alpha < \omega_0 \rightarrow$ under-damped

$$i_L(t) = e^{-\alpha t} [I_1 \cos(\omega_d t) + I_2 \sin(\omega_d t)] + I_3$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 4,75 \text{ rad/s}$$

$$I_3 = 0 \text{ (we don't have source @ } t > 0)$$

* (3) $t = 0^+, i_L(0^+) = i_L(0^-)$

$$i_L(t) = e^0 [I_1 \cos(0) + I_2 \sin(0)] + 0$$

$$2,02 A = I_1$$

* (4) $\frac{d i_L(0^+)}{dt} = ?$

$$V_L = \frac{d i_L}{dt}$$

$$\frac{V_L(0^+)}{L} = \frac{d i_L(0^+)}{dt}$$

$$V_L(0^+) = V_C(0^+) = 97,3 V$$

$$\frac{d i_L(0^+)}{dt} = \frac{97,3}{10} = 9,73 A$$

* (5) $\frac{d i_L}{dt} = -\alpha e^{-\alpha t} [I_1 \cos(\omega_d t) + I_2 \sin(\omega_d t)] + [-\omega_d I_1 \sin(\omega_d t) + \omega_d I_2 \cos(\omega_d t)] e^{-\alpha t}$


@ $t = 0$

$$9,73 = (-1,2) (2,02) + 4,75 I_2$$

$$I_2 = 2,56 A$$

$$i_L(t) = e^{-1,2 t} [2,02 \cos(4,75 t) + 2,56 \sin(4,75 t)] A, \quad t > 0$$


$$i_L(t) = 2,02 A, \quad t < 0$$

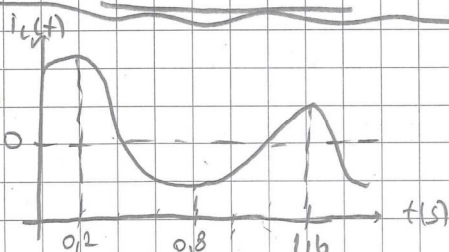



$$4,75 = 2\pi f$$

$$f = 0,75 \rightarrow T = 1/f = 1,33 \text{ sec}$$

Ex:

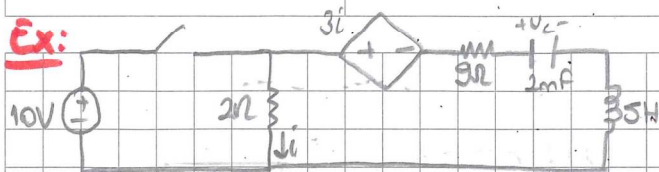

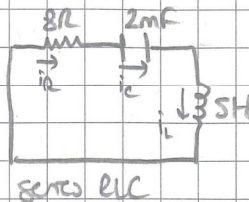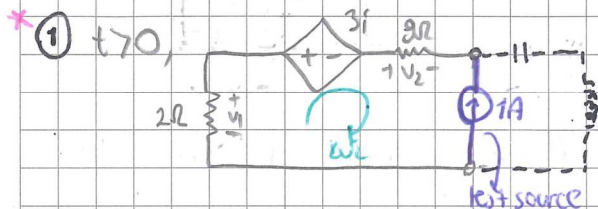Find an expression for $V_c(t)$ for $t > 0$.



$$\alpha = \frac{R}{2L} = 0.8 s^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 10 \text{ rad/s}$$

$\alpha < \omega_0 \rightarrow$ under-damped

$$V_c(t) = e^{-\alpha t} [V_1 \cos(\omega_d t) + V_2 \sin(\omega_d t)] + V_3$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 9.97 \text{ rad/s}$$

@ $t \rightarrow \infty$, $V_3 = 0$ because we have no source

we need to apply V_{th} approach to find $R_{eq} = 8\Omega$

$$-V_1 + 3i + V_2 + V_T = 0$$


$$-2i + 3i - 9i + V_T = 0$$

$$V_T = 8i$$

$$V_T = 8 \cdot 1A = 8V$$

$$R_{eq} = \frac{V_T}{1A} = 8\Omega$$

② $t < 0$, for find $V_c(0^-)$

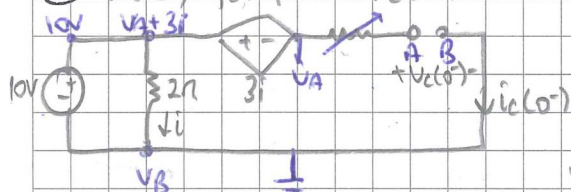

$i_c(0^-) = i_c(0^+) = 0A$ for open circuit

$$i = \frac{10V}{2\Omega} = 5A$$

$$V_c(0^-) = V_c(0^+) = V_1 - V_3 \rightarrow V_1 + 3i = 10V$$

$$V_c(0^-) = V_c(0^+) = -5V \quad \begin{cases} V_1 = 10V - 5V = -5V \\ V_3 = 0V \end{cases}$$

③ $t = 0^+$

$$-5V = e^0 [V_1 \cos 0 + V_2 \sin 0] + 0$$

$$-5V = V_1$$

$$\frac{dV_c(0^+)}{dt} \rightarrow i_c(t) = C \frac{dV_c(t)}{dt}$$

$$\frac{dV_c(0^+)}{dt} = i_c(0^+) \cdot C = 0$$

we take derivative $\rightarrow 0 = -0.8(-5V) + 9.97V_2$
and put α, V_1


$$V_2 = -0.4V$$

$$⑤ V_c(t) = e^{-\alpha t} [V_1 \cos(\omega_d t) + V_2 \sin(\omega_d t)] + V_3$$


$$V_c(t) = e^{-0.8t} [-5 \cos(9.97t) - 0.4 \sin(9.97t)], t > 0$$

$$V_c(t) = -5V, t < 0$$

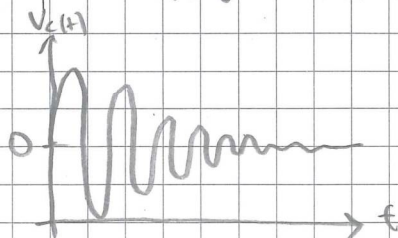
* for $\alpha < \omega_0$ and our circuit is under-damped, we have oscillation,



Ex:

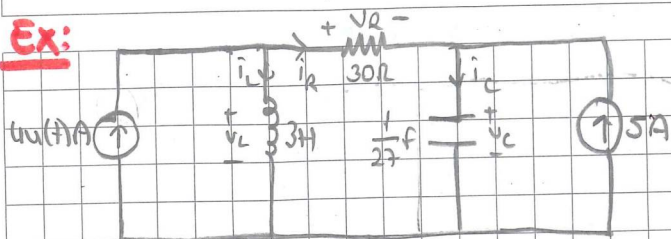

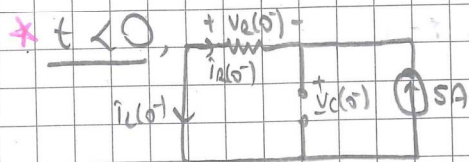Find i_R, i_L, i_C and v_R, v_L, v_C at $t=0^-$ and $t=0^+$.



$$v_R(0^-) = (30\Omega)(-5A) = -150V$$

$$v_L(0^-) = 0V$$


$$v_C(0^-) = 150V$$

$$* v_C(0^-) = v_C(0^+) \text{ and } i_L(0^-) = i_L(0^+)$$

$$i_R(0^-) = -5A$$

$$i_L(0^-) = 5A$$

$$i_C(0^-) = 0A$$

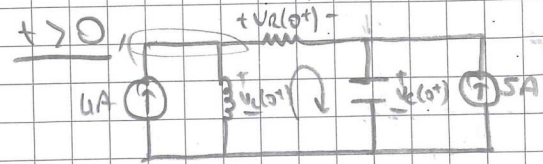

KCL @ upper left KCL @ upper right

$$4A = 5A + i_R(0^+)$$

$$i_R(0^+) + 5A = i_C(0^+)$$

$$i_R(0^+) = -1A$$

$$i_C(0^+) = 4A$$

$$v_R(0^+) = (30\Omega)(-1A) = -30V$$

$$v_C(0^+) = 150V$$

$$i_L(0^+) = 5A$$

$$\text{for find } v_L(0^+) \rightarrow -v_L + v_R + v_C = 0$$

$$v_L(0^+) = 120V$$

we can find derivatives at $t=0^+$,

$$\frac{d i_L(0^+)}{dt} \rightarrow v_L = L \frac{d i_L}{dt}$$

$$\frac{d i_L(0^+)}{dt} = \frac{v_L(0^+)}{L} \Rightarrow \frac{120V}{3H} = 40A/s$$

$$\frac{d i_R(0^+)}{dt} \rightarrow 4 - i_L - i_R = 0$$

$$\frac{d i_R(0^+)}{dt} = 0 - \frac{d i_L(0^+)}{dt} = -40A/s$$

$$\frac{d i_C(0^+)}{dt} \rightarrow i_C = C \frac{d v_C}{dt}$$

$$\frac{d i_C(0^+)}{dt} \rightarrow 5 + i_R = i_C$$

$$0 + \frac{d i_R(0^+)}{dt} = \frac{d i_C(0^+)}{dt} = -40A/s$$

$$\frac{d i_C(0^+)}{dt} = \frac{d v_C(0^+)}{dt} \Rightarrow \frac{4A}{1/25} = 108V/s$$

$$\frac{d v_R(0^+)}{dt} \rightarrow v = i \cdot R$$

$$\frac{d v_L(0^+)}{dt} \rightarrow -v_L + v_R + v_C = 0$$

$$\frac{d v_R(0^+)}{dt} = \frac{d i_R(0^+)}{dt} \cdot R = (-40A/s)(30) = -1200V/s$$

$$\frac{d v_L(0^+)}{dt} = \frac{d v_R(0^+)}{dt} + \frac{d v_C(0^+)}{dt}$$

$$\frac{d v_L(0^+)}{dt} = -1092V/s$$

$$\frac{d i_R(0^+)}{dt} = -40A/s$$

$$\frac{d v_R(0^+)}{dt} = -1200V/s$$


$$\frac{d i_L(0^+)}{dt} = 40A/s$$

$$\frac{d v_L(0^+)}{dt} = -1092V/s$$

$$\frac{d i_C(0^+)}{dt} = -40A/s$$

$$\frac{d v_C(0^+)}{dt} = 108V/s$$

* ALTERNATE CURRENT (AC) *

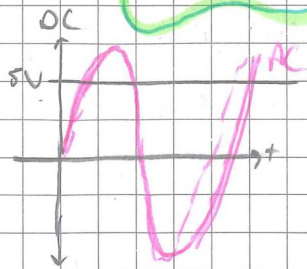

we can show that in circuits



AC notation

$$v(t) = V_A \sin(\omega t + \phi) = V_A \cos(\omega t + \phi + \pi/2)$$

angular freq.

$$\omega = 2\pi f$$


$$f = \frac{1}{T} \rightarrow \text{period}$$

phase


fourier transform $\rightarrow$ any signal can be transform to sum of the sinusoids.

$$v(t) = \sum_{n=-\infty}^{\infty} A_n \cos(\omega_n t + \theta_n), \quad \omega_n = 2\pi f_n$$

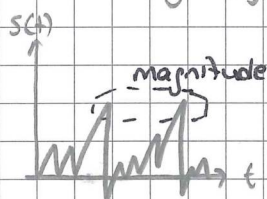* In AC analysis, your capacitor and inductor behaviors are changing by the frequency.



fourier

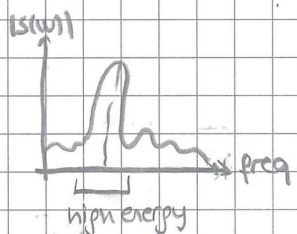



* input $\rightarrow$ output, magnitude and phase can be changed but the frequency must be the same.

$\rightarrow$ Complex Numbers: $j^2 = -1$ imaginary

$$x = a + bj$$

$$a = \text{Re}\{x\}, \quad b = \text{Im}\{x\}$$

rectangular form

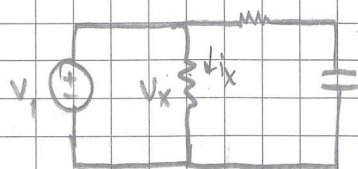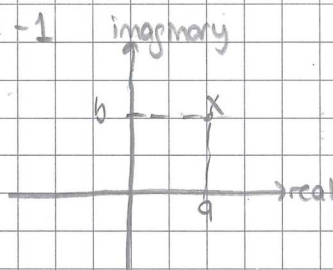

$$i_x = I_x \cos(2\pi f t + \phi)$$

$$v_i = A \cos(2\pi f t + \phi) \rightarrow v_x = A_x \cos(2\pi f t + \phi)$$

$$\text{Re} = \{A e^{j(2\pi f t + \phi)}\}$$

$$A e^{j\phi} = A \cos\phi + jA \sin\phi \quad (\text{euler's})$$

$$e^{j\phi} = \cos\phi + j\sin\phi \rightarrow |z|e^{j\phi} = a + bj$$

$$\begin{aligned} a &= |z|\cos\phi \\ b &= |z|\sin\phi \end{aligned} \quad |z| = \sqrt{a^2 + b^2}$$


$$\phi = \tan^{-1}\left(\frac{b}{a}\right)$$

$|z| \rightarrow$ magnitude of z

$\phi \rightarrow$ phase / angle of z

$$\star \quad \underbrace{z = a + bj}_{\text{rectangular form}} = \underbrace{|z|e^{j\phi}}_{\text{exponential form}} = \underbrace{|z|\angle\phi}_{\text{polar form}} \quad \nabla$$

Ex:

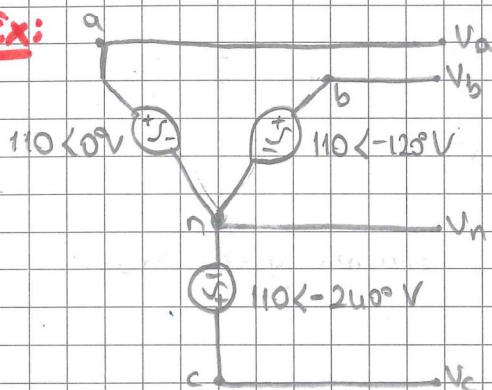

Determine the quantity $V_a - V_b$ in polar form if $V_n = 0$.

$$V_a - V_b = 110\angle 0^\circ - 110\angle -120^\circ$$

$$= [110\cos 0 + j110\sin 0] - [110\cos(-120) + j110\sin(-120)]$$

$$= [110 + j0] - [110(-1/2) + j110(-\sqrt{3}/2)]$$


$$= 165 + j55\sqrt{3}$$

$$|V_a - V_b| = \sqrt{(165)^2 + (55\sqrt{3})^2} \cdot \tan^{-1}(55\sqrt{3}/165)$$

$$= \underline{190.5\angle 30^\circ}$$

$$\star \quad \left. \begin{aligned} z_1 &= a_1 + bj = |z_1|e^{j\theta_1} \\ z_2 &= a_2 + bj = |z_2|e^{j\theta_2} \end{aligned} \right\} \begin{aligned} z_1 \cdot z_2 &= |z_1||z_2|\angle\theta_1 + \theta_2 \\ \frac{z_1}{z_2} &= \frac{|z_1|}{|z_2|}\angle\theta_1 - \theta_2 \end{aligned} \quad \nabla$$

Ex:

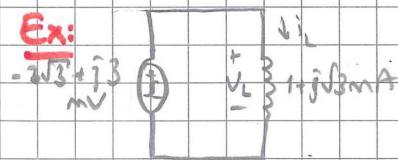


determine the ratio of V_L to i_L

$$\frac{V_L}{i_L} = \frac{|V_L|}{|i_L|}\angle\theta_{V_L} - \theta_{i_L}$$

$$= \frac{-2\sqrt{3} + j3 \text{ mV}}{1 + j\sqrt{3} \text{ mA}} = \frac{\sqrt{(3\sqrt{3})^2 + (3)^2} \angle \tan^{-1}(1/-\sqrt{3})}{\sqrt{1^2 + (\sqrt{3})^2} \angle \tan^{-1}(\sqrt{3})} = \frac{6\angle 150^\circ}{2\angle 60^\circ} = \underline{3\angle 90^\circ}$$

$\star$

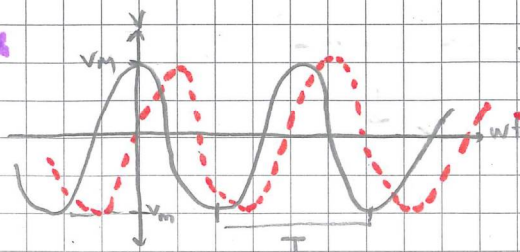

$$\left. \begin{aligned} V_1 &= V_m \sin(\omega t) \\ V_2 &= V_m \sin(\omega t + \phi) \end{aligned} \right\} \begin{aligned} V_1 &\text{ leads } V_2 \text{ by } \phi \\ V_2 &\text{ lags } V_1 \text{ by } \phi \end{aligned}$$

$$\omega = 2\pi f \quad T = \frac{1}{f}$$

→ to find phase difference (ϕ);


$$t_s = 0.2 \text{ s (phase diff)}$$

$$f_s = 0.5 \text{ Hz}$$

$$T = 1/0.5 = 2 \text{ s} \leftarrow \text{period}$$

$$\begin{array}{ccc} 1 \text{ cycle} & 2 \text{ sec} & 2\pi \\ 0.2 \text{ sec} & ? & \end{array}$$

$$? = 0.2 \cdot 2\pi = 0.4\pi$$

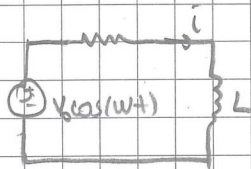

$$\frac{di(t)}{dt} + \frac{R}{L} i(t) = \frac{V_0}{L} \cos(\omega t) \rightarrow \text{oscillates forever}$$

$$i(t) = I_0 \cos(\omega t + \phi)$$

$$i(t) = \frac{V_0}{\sqrt{R^2 + \omega^2 L^2}} \cos \left\{ \omega t - \tan^{-1} \left(\frac{\omega L}{R} \right) \right\}$$

* Frequency (ω) is not changing.

* The RC / RL circuit's transient response is negligible after 5T.

* The RLC circuit's transient response is negligible after $T = T_s$.

* The remaining response is sinusoidal.

$$v(t) = V_m \cos(\omega t + \phi_1), \quad i(t) = I_m \cos(\omega t + \phi_2)$$

$$V_R(t) = I \cdot R$$

$$\phi_1 = \phi_2$$

→ V and I are in phase




$$V_L(t) = L \frac{di(t)}{dt}$$

$$\frac{V_m}{I_m} = \omega L$$

$$\phi_1 = \phi_2 + 90^\circ$$

→ V leads I by 90°

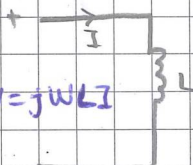


$$i_C(t) = C \frac{dV_C(t)}{dt}$$

$$\frac{I_m}{V_m} = \omega C$$

$$\phi_2 = \phi_1 + 90^\circ$$

→ I leads V by 90°

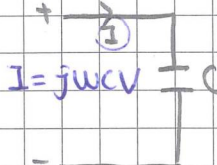

$$V_L = L j\omega \frac{e^{j(\omega t + \phi)}}{I_L} \rightarrow \frac{V_L}{I_L} = \omega L = Z = \text{impedance}$$

* Z (impedance):

$$Z_R = R$$


$$Z_L = j\omega L$$

$$Z_C = \frac{1}{j\omega C} \rightarrow -j \left(\frac{1}{\omega C} \right)$$

	High Frequency	Low Frequency
Inductor	large Z	small Z
Capacitor	small Z	large Z

* passive filters → R, L, C
active filters → Op-Amps

Ex:

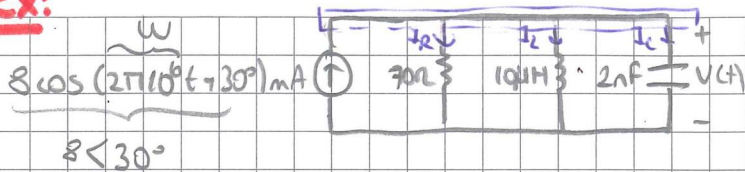

Determine $V(t)$.

$$I_s(t) = 8 \angle 30^\circ$$

$$Z_R = 70, \quad Z_L = j\omega L = j2\pi \cdot 10^6 \cdot 10 \cdot 10^{-6} = j20\pi$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j2\pi \cdot 10^6 \cdot 2 \cdot 10^{-9}} = -\frac{10^3}{j4\pi}$$

$$KVL \rightarrow 8 \angle 30^\circ = \frac{V}{70} + \frac{V}{j20\pi} + \frac{Vj4\pi}{10^3}$$

$$8 \angle 30^\circ = V \left[\frac{1}{70} + \frac{1}{j62.8} + j(0,012) \right]$$


$$8 \angle 30^\circ = V \left(0,0143 - 0,0033j \right)$$

$$0,0147 \angle -13^\circ$$

$$\rightarrow V = \frac{8 \angle 30^\circ}{0,0147 \angle -13^\circ} = 545 \angle 43^\circ \text{ mV}$$

$$V(t) = 545 \cos(2\pi 10^6 t + 43^\circ) \text{ mV}$$

Ex:

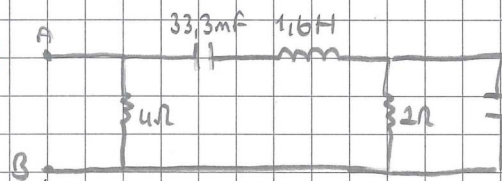


Determine the equivalent impedance of

the network at terminals A-B, if $\omega = 5 \text{ rad/s}$

$$Z_L = j\omega L = j \cdot 5 \cdot (1,6) = 8j$$

$$Z_{C1} = \frac{1}{j\omega C} = \frac{1}{j5(33,3 \cdot 10^{-3})} = -6j$$
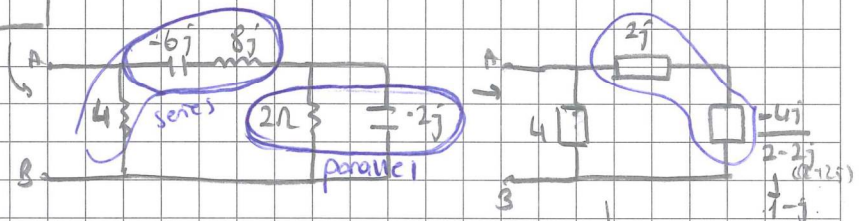
$$Z_{C2} = \frac{1}{j5(100 \cdot 10^{-3})} = -2j$$



$$Z_{eq} = 4 + 1 + j = \frac{4 + 4j}{5 + j} = \frac{24 + 16j}{26}$$

$$= 0,92 + j0,62 \rightarrow Z_{eq} = 1,1 \angle 33,9^\circ$$

* Reactance *

$$Z = \frac{V}{I} = R + j(X) \quad \text{imaginary part}$$

$$Z_R = R \rightarrow X = 0$$

$$Z_L = j\omega L \rightarrow X = \omega L$$

$$Z_C = \frac{1}{j\omega C} \rightarrow X = \frac{1}{\omega C}$$

* Admittance *

$$Y = \frac{1}{Z}$$


$$Y_R = \frac{1}{R}$$

$$Y_L = \frac{-j}{\omega L}$$

$$Y_C = j\omega C$$

NOTE: If we have two sources with two different frequency, we need to apply "superposition" theorem.

Ex:

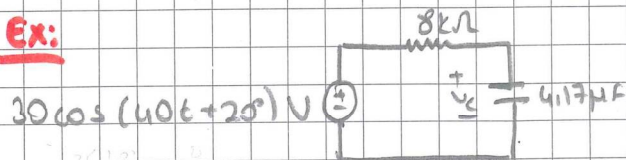


Determine $V_c(t)$ on time domain.

$$30 \cos(40t + 25^\circ) \rightarrow 30 \angle 25^\circ$$

$$Z_R = 8000$$
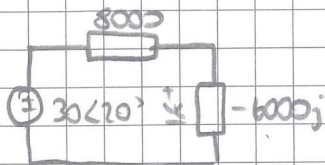
$$Z_C = \frac{1}{j \cdot 40 \cdot 4.17 \cdot 10^{-6}} = -6000j$$



$$V_c = \frac{(30 \angle 25^\circ)(-6000j)}{8000 - 6000j}$$

$$= \frac{(30 \angle 25^\circ)(6000 \angle -90^\circ)}{(10000 \angle -37^\circ)}$$

$$V_c = 18 \angle -33^\circ$$

$$\underline{V_c(t) = 18 \cos(40t - 33^\circ)}$$